

Module-2 : AC Circuits and Magnetic Circuits

① AC Circuit Analysis :-

- (i) Fundamentals of AC Circuit
- (ii) R, RL, RC, LC and RLC Circuits
- (iii) Series and Parallel Circuits
- (iv) Phasor Diagrams
- (v) Resonance in AC Circuit

② Magnetic Circuits :-

- (i) Analogy between electric and magnetic circuits
- (ii) Series and Parallel magnetic circuits
- (iii) Self and Mutual Inductance
- (iv) Magnetic circuit Applications


- DC motors
- Generators
- Transformers

Fundamentals of AC Circuit :-

DC





AC

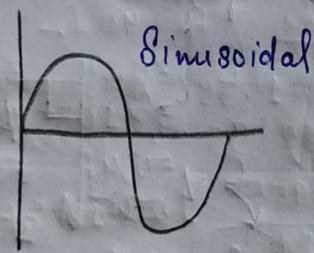

$f = 50 \text{ Hz}$ (standard Indian household)

$$T = \frac{s}{f} = \frac{s}{50} = 0.02 \text{ s}$$

Time Period

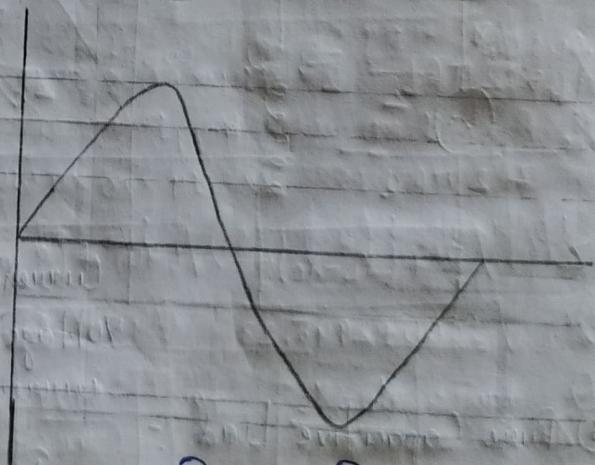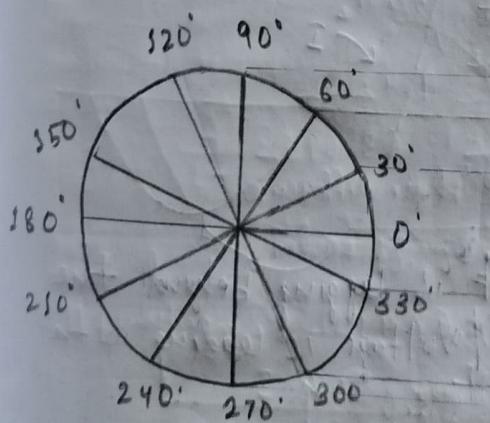

$$I_{\text{peak}} = I_{\text{max}} = I_{\text{rms}} \sqrt{2}$$

$$V_{\text{peak}} = V_{\text{max}} = V_{\text{rms}} \sqrt{2}$$

$$I_{\text{avg}} = \frac{2 \times I_{\text{max}}}{\pi} = 0.637 \times I_{\text{max}}$$

$$V_{\text{avg}} = \frac{2 \times V_{\text{max}}}{\pi} = 0.637 \times V_{\text{max}}$$

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}}$$

$$V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}}$$

$$\int \frac{2}{\pi} = 0.637$$

Power :-


- The first power is Active Power (useful power).
- The second power is Reactive Power (useless power).
- The third power is Apparent Power.

Mathematically,

$$\text{Reactive Power} (Q) = V \times I \times \sin \phi$$



$$\text{Apparent Power} (S) = \sqrt{P^2 + Q^2}$$
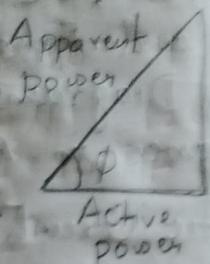
$$\text{Active Power} (P) = V \times I \times \cos \phi = I^2 R$$



AC Circuit : Types of Loads :-



① Pure Resistive Load :-

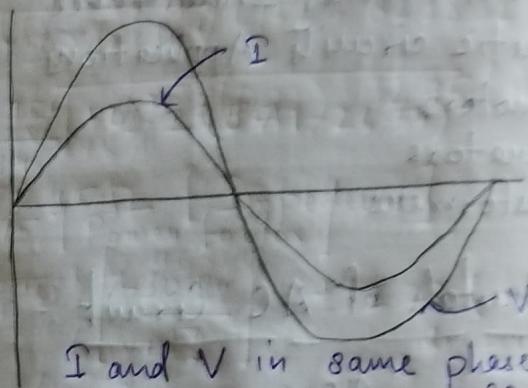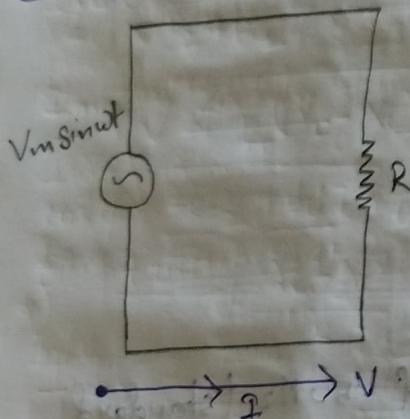

I and V in same phase
Magnitude can be different



$$\text{Power Factor (P.F)} = 1 \text{ (Unity)}$$

② Pure Inductive Load :-

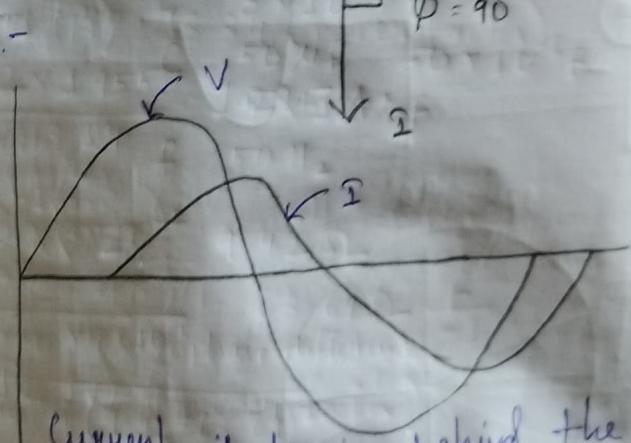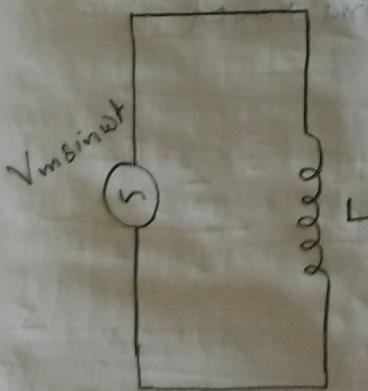

Current is lagging behind the voltage / Voltage is leading with current

③ Pure Capacitive Load :-

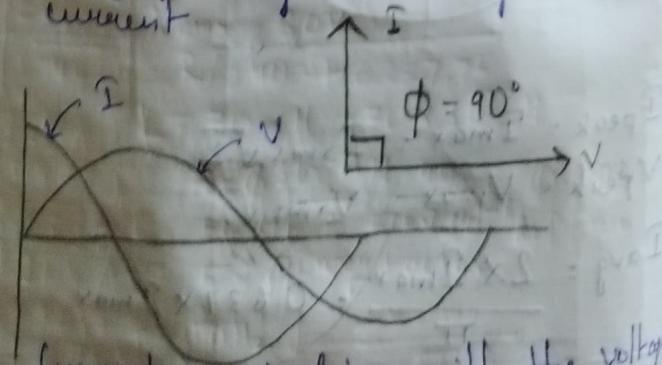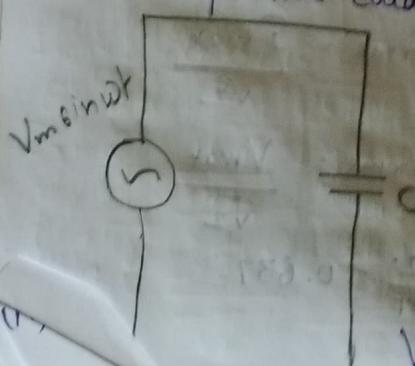

Current is leading with the voltage
Voltage is lagging behind current

- (4) Resistive - Inductive [RL-circuit] :-
Current lags with the voltage | Voltage leads with current
- (5) Resistive - Capacitive [RC-circuit] :-
Current leads with the voltage | Voltage lags with current
- (6) Resistive - Inductive - Capacitive [RLC-circuit] :-
- If $X_L > X_C$: Lagging power factor NOTE :-
If $X_C > X_L$: Leading power factor $I_{max} = \frac{V_{max}}{Z}$
- $X_L = \omega L = 2\pi f L$ } $\omega = 2\pi f$ $\cos \phi = \frac{R}{Z}$ = Power factor
 $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

(i) In R-L circuit :- (ii) In RC-circuit :- (iii) In RLC-circuit :-

$$Z \angle \theta = R + jX_L$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$\theta = \tan^{-1} \left[\frac{X_L}{R} \right]$$

$$Z \angle \theta = R - jX_C$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$\theta = \tan^{-1} \left[\frac{-X_C}{R} \right]$$

$$Z \angle \theta = R + j(X_L - X_C)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta = \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$$


In case of Parallel AC Circuit [RLC] :-

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}}$$

When the given AC circuit has resistors, inductors and capacitors parallelly connected.

RC-circuit : $Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_C}\right)^2}}$

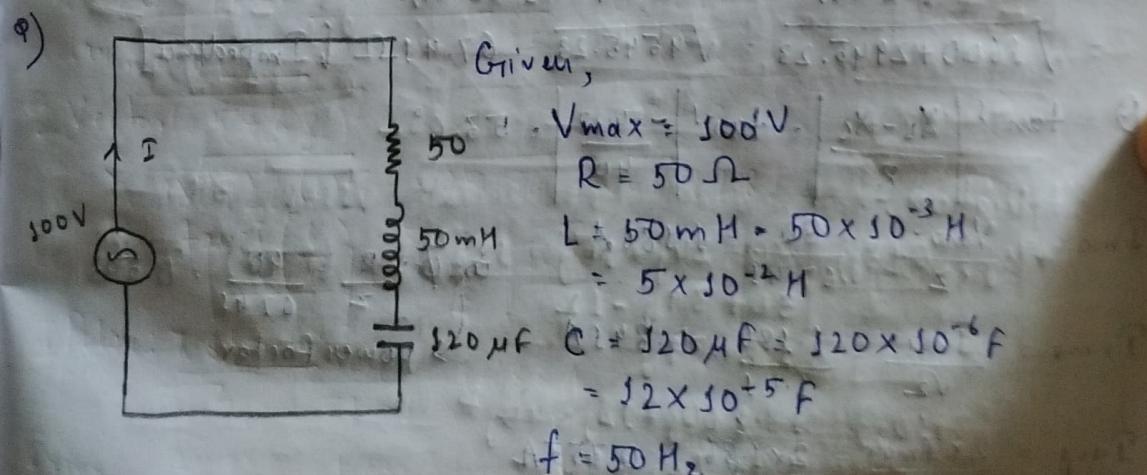RL-circuit : $Z = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L}\right)^2}$



$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 5 \times 10^{-4} = 15.7 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 12 \times 10^{-5}} = 26.54 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(50)^2 + (15.7 - 26.54)^2} = \sqrt{2500 + 1157.5} = 53.55 \Omega [Impedance]$$

$$\theta = \tan^{-1} \left| \frac{X_L - X_C}{R} \right| = \tan^{-1} \left| \frac{-10.84}{50} \right| = 52.23^\circ$$


$$I_{max} = \frac{V_{max}}{Z} = \frac{500}{53.55} = 9.55 A$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = \frac{9.55}{\sqrt{2}} = 6.886 A$$

$$I_{avg} = \frac{2 \times I_{max}}{\pi} = \frac{2 \times 9.55}{\pi} = 6.295 A$$

$$\cos \phi = \frac{R}{Z} = \frac{50}{53.55} = 0.9775 [Power factor]$$

Q)

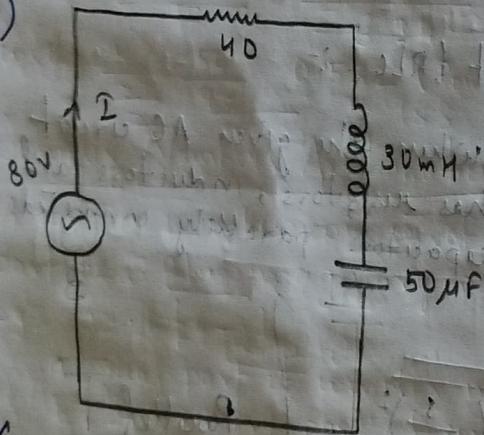

Given, $I_A = 1A$

$$V_{max} = 80V$$

$$R = 40 \Omega$$

$$L = 30mH = 30 \times 10^{-3} H$$

$$C = 50 \mu F = 50 \times 10^{-6} F$$

$$f = 50 Hz$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 3 \times 10^{-2} = 9.42 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 5 \times 10^{-6}} = 63.69 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(40)^2 + (9.42 - 63.69)^2}$$

$$= \sqrt{1600 + 2945.23} = \sqrt{4545.23} = 67.41 \Omega [Impedance]$$

$$I_{max} = \frac{V_{max}}{Z} = \frac{80}{67.41} = 1.186 A$$


$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = \frac{1.186}{\sqrt{2}} = 0.845 A$$

$$\cos \phi = \frac{R}{Z} = \frac{40}{67.41} = 0.593$$

power factor

$$I_{avg} = \frac{2 \times I_{max}}{\pi} = \frac{2 \times 1.186}{\pi} = 0.755 A$$

H.W. ⑥

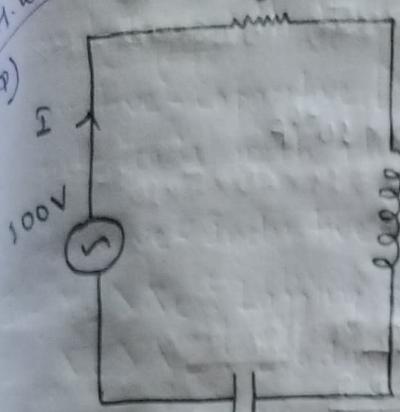

Given,

$$V_{max} = 100V$$

$$R = 30\Omega$$

$$L = 40\text{mH} = 40 \times 10^{-3}\text{H}$$

$$= 4 \times 10^{-2}\text{H}$$

$$C = 50\mu\text{F} = 50 \times 10^{-6}\text{F}$$

$$= 5 \times 10^{-5}\text{F}$$

$$f = 50\text{Hz}$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 4 \times 10^{-2} = 12.56\Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1 \times 10^5}{2 \times 3.14 \times 50 \times 5} = 63.69\Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(30)^2 + (12.56 - 63.69)^2}$$
$$= \sqrt{900 + 2634.27} = \sqrt{3534.27} = 59.28\Omega \quad [\text{Impedance}]$$

$$\theta = \tan^{-1} \left| \frac{X_L - X_C}{R} \right| = \tan^{-1} \left| \frac{-51.13}{40} \right| = 59.58^\circ$$


$$I_{max} = \frac{V_{max}}{Z} = \frac{100}{59.28} = 1.686\text{A}$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = \frac{1.686}{\sqrt{2}} = 1.195\text{A}$$

$$I_{avg} = \frac{2 \times I_{max}}{\pi} = \frac{2 \times 1.686}{3.14} = 1.073\text{A}$$

$$\cos\phi = \frac{R}{Z} = \frac{30}{59.28} = 0.506 \quad [\text{Power factor}]$$

Q)

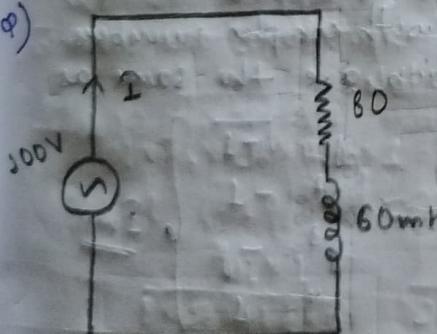

Given,

$$V_{max} = 100V$$

$$R = 80\Omega$$

$$L = 60\text{mH} = 60 \times 10^{-3}\text{H}$$

$$= 6 \times 10^{-2}\text{H}$$

$$f = 50\text{Hz}$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 6 \times 10^{-2} = 18.84\Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(80)^2 + (18.84)^2} = \sqrt{6755} = 82.18\Omega \quad [\text{Impedance}]$$

$$\theta = \tan^{-1} \left[\frac{X_L}{R} \right] = \tan^{-1} \left[\frac{18.84}{80} \right] = \tan^{-1} (0.23) = 13.295^\circ$$


$$I_{max} = \frac{V_{max}}{Z} = \frac{100}{82.18} = 1.216\text{A}$$

$$I_{avg} = \frac{2 \times I_{max}}{\pi} = \frac{2 \times 1.216}{3.14}$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = \frac{1.216}{\sqrt{2}} = 0.862\text{A}$$

$$I_{avg} = 0.774\text{A}$$
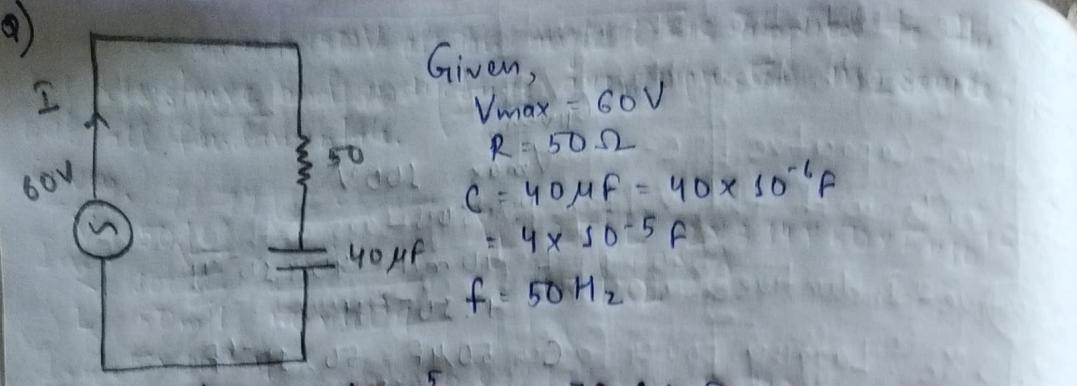
$$\cos\phi = \frac{R}{Z} = 0.9734 \quad (\text{power factor})$$



$$X_C = \frac{1}{2\pi f C} = \frac{1 \times 10^5}{2 \times 3.14 \times 50 \times 4} = 79.61\Omega$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(50)^2 + (79.61)^2} = \sqrt{8837.75} = 94 \quad (\text{Impedance})$$

$$\theta = \tan^{-1} \left[\frac{X_C}{R} \right] = \tan^{-1} \left[\frac{79.61}{50} \right] = \tan^{-1}(1.5922) = 57.868^\circ$$

$$I_{max} = \frac{V_{max}}{Z} = \frac{60}{94} = 0.6328\text{ A}$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = \frac{0.6328}{\sqrt{2}} = 0.448\text{ A}$$

$$I_{avg} = \frac{2 \times I_{max}}{\pi} = \frac{2 \times 0.6328}{\pi} = 0.403\text{ A}$$

$$\cos\phi = \frac{R}{Z} = \frac{50}{94} = 0.532 \quad (\text{Power factor})$$

Complex Numbers Arithmetics :-

A complex number consists of two parts namely, the real part and the imaginary part.

Eg :- $a+ib$ | $a-jb$

a = Real part of complex no.

b = Imaginary part of complex no.

All the operations can be performed with complex numbers. Among them, addition and subtraction are the same as in case of real numbers.

Addition :-

$$\begin{array}{r} 2 + 5i \\ 3 + 4i \\ \hline 5 + 9i \end{array}$$

Subtraction :-

$$\begin{array}{r} 5 + 5i \\ 2 + 2i \\ \hline 3 + 3i \end{array}$$

$$\left. \begin{array}{l} j = \sqrt{-1} \\ j^2 = -1 \\ j^3 = -j \\ j^4 = 1 \end{array} \right\} \text{Imp}$$

Multiplication :-

$$\begin{aligned} (5+4j)(6+3j) &= 30 + 24j + 15j + 12j^2 \\ &= 30 + 39j - 12 \\ &= 18 + 39j \end{aligned}$$

$$\begin{aligned} (6+4j)(3+10j) &= 18 + 60j + 12j + 40j^2 \\ &= 18 + 72j + 40j^2 \\ &= -22 + 72j \end{aligned}$$

$$a) \frac{6+4j}{3+50j} \times (3-50j) = \frac{(6+4j)(3-50j)}{9-2500} \\ = \frac{18-300j+12j-200}{9-2500} = \frac{18-288j-188}{9-2500} = \frac{58-48j}{109} = 0.5 - 0.4j$$

Vector to Polar form :-

$$\text{Vector} : 2+3j$$

$$\text{magnitude} = r = \sqrt{2^2 + 3^2} = \sqrt{4+9} = \sqrt{13} = 3.60$$

$$\theta = \tan^{-1}\left(\frac{3}{2}\right) = 56.30^\circ \quad [\text{Phase angle}]$$

$$\text{Polar} : 3.60 [56.30^\circ]$$

$$\text{Vector} : 5+6j$$

$$r = \sqrt{5^2 + 6^2} = \sqrt{25+36} = \sqrt{61} \approx 7.81$$

$$\theta = \tan^{-1}\left(\frac{6}{5}\right) = 50.59^\circ \quad \sin \theta \text{ +ve}$$

$$\text{Polar} : 7.81 [50.59^\circ]$$

Polar to Vector form

$$\text{Vector form} : a+jb$$

$$\text{Polar} : 5 [120^\circ]$$

$$\text{Magnitude } (a) = 5$$

$$\text{Phase angle } (\theta) = 120^\circ$$

$$a = r \cos \theta$$


$$= r \cos 120^\circ$$

$$= r \cos (180^\circ - 60^\circ)$$

$$= r (-\cos 60^\circ)$$

$$= 5 \times \frac{1}{2}$$

$$= 2.5$$

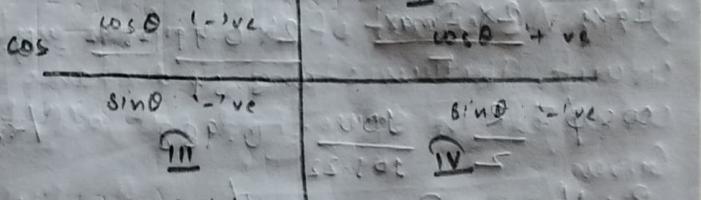

$$b = r \sin \theta$$

$$= r \sin 120^\circ$$

$$= r \sin (180^\circ - 60^\circ)$$

$$= r \sin 60^\circ$$

$$= 5 \times \frac{\sqrt{3}}{2}$$

$$= 4.33$$

$$\text{Vector} : 2.5 + 4.33j$$

$$\text{Polar} : 7.8 [50.59^\circ]$$

$$a = r \cos \theta$$

$$= r \cos (50.59^\circ)$$

$$= 7.8 \times 0.64$$

$$= 5$$

$$\text{Vector} : 5 + 6j$$

$$\text{Polar} : 7.8 [50.59^\circ]$$

$$a = r \cos \theta$$

$$= r \cos (56.3)$$

$$= 3.6 \times 0.554$$

$$= 2$$

$$b = r \sin \theta$$

$$= r \sin (56.3)$$

$$= 7.8 \times 0.768$$

$$6$$

$$b = r \sin \theta$$

$$= r \sin (56.3)$$

$$= 3.6 \times 0.832$$

$$= 3$$

$$\text{Vector} : 2 + 3j$$

An AC circuit 50V at an angle 0° is applied to the circuit. The resistance and inductance are connected in series. Find out all fundamentals.

Given,

$$V = 50 \angle 0^\circ$$

$$R = 500 \Omega$$

$$L = 50 \text{ mH} = 50 \times 10^{-3} \text{ H}$$

$$= 5 \times 10^{-2} \text{ H}$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(500)^2 + (55.7)^2} = 505.22 \Omega$$

$$\theta = \tan^{-1} \left(\frac{55.7}{500} \right) = 6.92^\circ$$

$$Z = 505.22 \angle 6.92^\circ [220]$$

$$I_{\max} = \frac{V}{Z} = \frac{50 \angle 0^\circ}{505.22 \angle 6.92} = 0.49 \angle 6.92 \text{ A}$$

$$I_{\text{rms}} = \frac{I_{\max}}{\sqrt{2}} = \frac{1}{\sqrt{2}} \times 0.49 \angle 6.92 = 0.347 \angle 6.92 \text{ A}$$

$$I_{\text{avg}} = \frac{2 \times I_{\max}}{\pi} = \frac{2 \times 0.49 \angle 6.92}{\pi} = 0.288 \angle 6.92 \text{ A}$$

$$\cos \phi = \frac{R}{Z} = \frac{500}{505.22} = 0.988$$

$$V_{\text{rms}} = \frac{V_{\max}}{\sqrt{2}} = \frac{50 \angle 0^\circ}{\sqrt{2}}$$

$$P = V_{\text{rms}} \times I_{\text{rms}} \times \cos \phi$$

$$V_{\text{rms}} = 35.46 \angle 0^\circ \text{ V}$$

$$= 35.46 \angle 0^\circ \times 0.347 \angle 6.92 \times 0.988$$

$$= 12.3 \angle 6.92 \times 0.988$$

$$= 12.1524 \angle 6.92 \text{ W}$$

a) An AC circuit of 500V at an angle 0° is applied to the circuit. The resistance, inductance and capacitance are connected in series. Find out all the fundamentals.

Given,

$$R = 20 \Omega$$

$$V = 500 \angle 0^\circ$$

$$L = 25 \text{ mH} = 25 \times 10^{-3} \text{ H}$$

$$C = 90 \text{ HF} = 90 \times 10^{-6} \text{ F}$$

$$= 9 \times 10^{-5} \text{ F}$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 25 \times 10^{-3}$$

$$= 7.85 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 9 \times 10^{-5}}$$

$$= 35.38 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(20)^2 + (7.85 - 35.38)^2} = \sqrt{1558} = 34 \Omega$$

$$\theta = \tan^{-1} \left| \frac{X_L - X_C}{R} \right| = \tan^{-1} \left| \frac{7.85 - 35.38}{20} \right| = \tan^{-1} (3.3755) = 53.9^\circ$$

$$Z \angle \theta = 34 \angle 53.9^\circ \Omega$$

$$I_{\max} = \frac{V}{Z} = \frac{500 \angle 0^\circ}{34 \angle 53.9^\circ} = 2.943 \angle -53.9^\circ \text{ A}$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = \frac{5}{\sqrt{2}} \times 2.945 |+53.9^\circ| = 2.085 |+53.9^\circ| A$$

$$I_{avg} = \frac{2 \times I_{max}}{\pi} = \frac{2 \times 2.945}{3.14} |+53.9^\circ| = 1.873 |+53.9^\circ| A$$

$$\cos \phi = \frac{R}{Z} = \frac{20}{34} = 0.588 \quad V_{rms} = \frac{V_{max}}{\sqrt{2}} = \frac{5}{\sqrt{2}} \times 100 |0^\circ|$$

$$P = V_{rms} \times I_{rms} \times \cos \phi \quad V_{rms} = 71 |0^\circ| V$$

$$= 71 |0^\circ| \times 2.085 |+53.9^\circ| \times 0.588$$

$$= 548.035 |+53.9^\circ| \times 0.588$$

$$= 87.04458 |+53.9^\circ| W$$

H.W ①

- (a) An AC circuit 80V at an angle 0° is applied to the circuit. The resistance and capacitance are connected in series. Find out all fundamentals.

Given,

$$V = 80 |0^\circ|$$

$$R = 80 \Omega$$

$$C = 500 \mu F = 500 \times 10^{-6} F$$

$$= 33.333333333333336 \times 10^{-6} F$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{(80)^2 + (33.333333333333336 \times 10^{-6})^2} = 86.5 \Omega$$

$$\theta = \tan^{-1} \left(\frac{-X_C}{R} \right) = \tan^{-1} \left(\frac{33.333333333333336 \times 10^{-6}}{80} \right) = \tan^{-1} (0.398) = -25.7^\circ$$

$$Z \angle \theta = 86.5 | -25.7^\circ | \Omega$$

$$I_{max} = \frac{V}{Z} = \frac{80 |0^\circ|}{86.5 | -25.7^\circ |} = 0.929 |+25.7^\circ| A$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}} = \frac{1}{\sqrt{2}} \times 0.929 |+25.7^\circ| = 0.658 |+25.7^\circ| A$$

$$I_{avg} = \frac{2 \times I_{max}}{\pi} = \frac{2 \times 0.929}{3.14} |+25.7^\circ| = 0.595 |+25.7^\circ| A$$

$$\cos \phi = \frac{R}{Z} = \frac{80}{86.5} = 0.929 \quad V_{rms} = \frac{V_{max}}{\sqrt{2}} = \frac{80 |0^\circ|}{\sqrt{2}}$$

$$P = V_{rms} \times I_{rms} \times \cos \phi \quad V_{rms} = 56.73 |0^\circ|$$

$$= 56.73 |0^\circ| \times 0.658 |+25.7^\circ| \times 0.929$$

$$= 34.678 |+25.7^\circ| W$$

- (b) An AC circuit 60V at an angle 30° is applied to the circuit. The resistance and inductance are connected in series. Find out all fundamentals.

Given,

$$V = 60 |30^\circ|$$

$$R = 70 \Omega$$

$$L = 50 mH = 50 \times 10^{-3} H = 5 \times 10^{-2} H$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 5 \times 10^{-2}$$

$$= 314 \times 5 \times 10^{-2} = 15.7 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(70)^2 + (15.7)^2} = \sqrt{5146.5} = 73.74 \Omega$$

$$\theta = \tan^{-1} \left[\frac{X_L}{R} \right] = \tan^{-1} \left(\frac{15.7}{70} \right) = \tan^{-1}(0.224) = 12.62^\circ$$

$$Z \angle \theta = 73.74 [12.62^\circ] \Omega$$

$$I_{\text{max}} = \frac{V}{Z} = \frac{60 [30^\circ]}{73.74 [12.62^\circ]} = 0.836 [17.38^\circ] A$$

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} = \frac{1}{\sqrt{2}} \times 0.836 [17.38^\circ] = 0.593 [57.38^\circ] A$$

$$I_{\text{avg}} = \frac{2 \times I_{\text{max}}}{\pi} = \frac{2 \times 0.836}{3.14} [17.38^\circ] = 0.532 [17.38^\circ] A$$

$$\cos \phi = \frac{R}{Z} = \frac{70}{73.74} = 0.975 \quad V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}} = \frac{1}{\sqrt{2}} \times 60 [30^\circ]$$

$$P = I_{\text{rms}} \times V_{\text{rms}} \times \cos \phi \quad V_{\text{rms}} = 42.55 [30^\circ]$$

$$= 0.593 [17.38^\circ] \times 42.55 [30^\circ] \times 0.975$$

$$= 25.23 [47.38^\circ] \times 0.975$$

$$= 24.6 [47.38^\circ] W$$

Q) An AC circuit of 300V at an angle 45° is applied to the circuit. The resistance, inductance and capacitance are connected in series. Find out all the fundamentals.

Given,

$$V = 300 [45^\circ]$$

$$R = 80 \Omega$$

$$L = 40 \text{ mH} = 40 \times 10^{-3} \text{ H} = 4 \times 10^{-2} \text{ H}$$

$$C = 120 \text{ MF} = 120 \times 10^{-6} \text{ F} = 12 \times 10^{-5} \text{ F}$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 4 \times 10^{-2} = 52.56 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1 \times 10^5}{2 \times 3.14 \times 50 \times 12 \times 10^{-5}} = \frac{1 \times 10^5}{3768} = 26.54 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(60)^2 + (52.56 - 26.54)^2} = \sqrt{3795.44} = 61.6 \Omega$$

$$\theta = \tan^{-1} \left| \frac{X_L - X_C}{R} \right| = \tan^{-1} \left| \frac{52.56 - 26.54}{60} \right| = \tan^{-1}(0.233) = 13.11^\circ$$

$$Z \angle \theta = 61.6 [13.11^\circ] \Omega$$

$$I_{\text{max}} = \frac{V}{Z} = \frac{300 [45^\circ]}{61.6 [13.11^\circ]} = 4.823 [33.89^\circ] A$$

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} = \frac{1}{\sqrt{2}} \times 4.823 [33.89^\circ] = 3.455 [33.89^\circ] A$$

$$I_{\text{avg}} = \frac{2 \times I_{\text{max}}}{\pi} = \frac{2 \times 4.823}{3.14} [33.89^\circ] = 0.733 [33.89^\circ] A$$

$$\cos \phi = \frac{R}{Z} = \frac{60}{61.6} = 0.974$$


$$V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}} = \frac{1}{\sqrt{2}} \times 300 [45^\circ]$$

$$V_{\text{rms}} = 70.92 [45^\circ]$$

$$\begin{aligned}
 P &= V_{rms} \times I_{rms} \times \cos \theta \\
 &= 70.92 \text{ } 145^\circ \times 1.581 \text{ } 121.89^\circ \times 0.974 \\
 &= 83.63 \text{ } 170.89^\circ \times 0.974 \\
 &= 79.5 \text{ } 118.89^\circ \text{ W}
 \end{aligned}$$

AC - Parallel Circuits

① RL Circuit

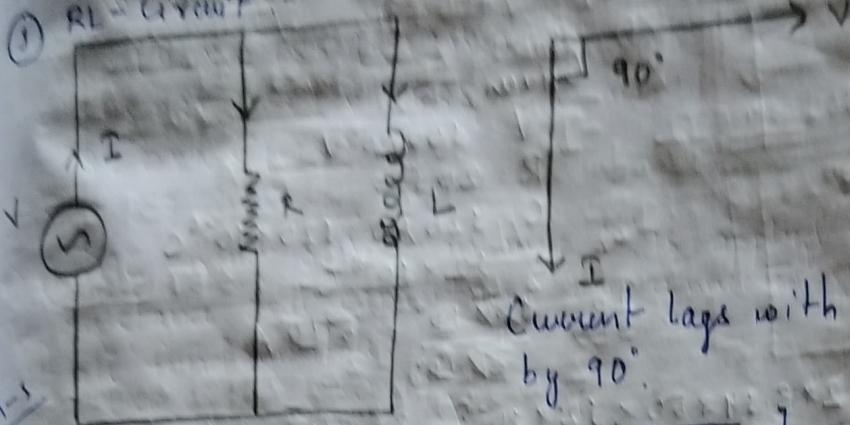


Current lags with the voltage by 90°.

$$\begin{aligned}
 I_{L0} &= I_R + I_L \\
 I_{L0} &= I_R - j I_{XL}
 \end{aligned}
 \quad \left. \begin{aligned}
 I &= \sqrt{I_R^2 + (-I_{XL})^2} \\
 I &= \sqrt{I_R^2 + I_{XL}^2}
 \end{aligned} \right\} \theta = \tan^{-1} \left[\frac{-I_{XL}}{I_R} \right]$$

M-2

$$Z = \frac{z_1 z_2}{z_1 + z_2} = \text{Impedance} \left[Z = \frac{V}{I} \right]$$

NOTE: Voltage always remains at 0°.

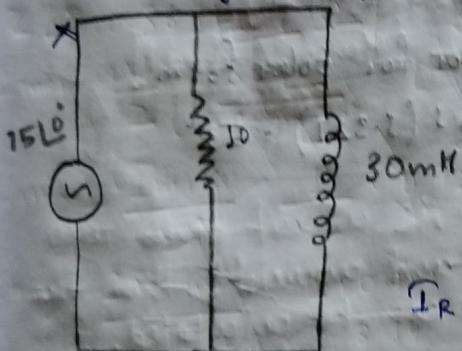

Given,

$$V = 75 \text{ } 10^\circ \text{ V}$$

$$R = 10 \Omega$$

$$L = 30 \text{ mH} = 30 \times 10^{-3} \text{ H} \\ = 3 \times 10^{-2} \text{ H}$$

$$I_R = \frac{V L 0}{R L 0} = \frac{75 \text{ } 10^\circ}{10 \text{ } 10^\circ} = 7.5 \text{ } 10^\circ \text{ A}$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 50 \times 3 \times 10^{-2} = 9.42 \Omega$$

$$I_{XL} = \frac{I_R}{X_L} = \frac{V}{X_L} = \frac{75 \text{ } 10^\circ}{9.42 \text{ } 190^\circ} = 7.96 \text{ } 1790^\circ \text{ A} \quad [\text{Current lags by } 90^\circ]$$

$$I = \sqrt{I_R^2 + I_{XL}^2}$$

$$= \sqrt{(7.5 \text{ } 10^\circ)^2 + (7.96 \text{ } 190^\circ)^2}$$

$$= \sqrt{56.25 \text{ } 100 + 63.36 \text{ } 180^\circ}$$

$$= \sqrt{56.25 - 63.36} \quad [\text{Vector form}]$$

$$= \sqrt{-7.51} = 7.51 \text{ A} \quad [\text{Polar form}]$$

$$a + b_j \quad | \quad a' + b'_j$$

$$a = 56.25 \cos 0^\circ; \quad b = 56.25 \sin 0^\circ$$

$$a = 56.25; \quad b = 0$$

$$a' = 63.36 \cos \pi$$

$$a' = -63.36; \quad b' = 81 \pi = 0$$

$$\sqrt{(-7.51)^2 + 0^2} = 7.51 \quad (\text{positive value taken})$$


$$\tan^{-1} \left(-\frac{X_L}{R} \right) = \tan^{-1} \left(-\frac{-9.42}{20} \right) = \tan^{-1} (-0.471) = -43.29^\circ$$

$$I_{LO} = 7.11 |43.29^\circ A$$

$$Z = \frac{V_{LO}}{I_{LO}} = \frac{75 \angle 0^\circ}{7.11 \angle 43.29^\circ} = \frac{75}{7.11} \angle 0 + 43.29^\circ = 30.55 \angle 43.29^\circ \Omega$$

Total Impedance of the circuit.

② RLC-Circuit :-

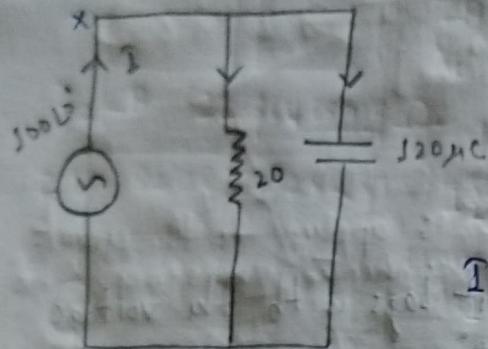

Given,

$$V = 500 \angle 0^\circ V$$

$$R = 20 \Omega$$

$$C = 120 \mu F = 120 \times 10^{-6} F$$

$$= 12 \times 10^{-5} F$$

$$I_R = \frac{500 \angle 0^\circ}{20 \angle 0^\circ} = 5 \angle 0^\circ A$$

$$X_C = 2\pi f C = 2 \times 3.14 \times 50 \times 120 \times 10^{-6} = 26.54 \Omega$$

$$I_{XC} = \frac{V}{X_C} = \frac{500 \angle 0^\circ}{26.54 \angle 90^\circ} = 3.76 \angle -90^\circ$$

[Current leads by 90°]

$$I = \sqrt{I_R^2 + I_{XC}^2}$$

$$= \sqrt{(5 \angle 0^\circ)^2 + (3.76 \angle -90^\circ)^2}$$

$$= \sqrt{25 \angle 0^\circ + 14.13 \angle -180^\circ}$$

$$= \sqrt{25 - 14.13} \quad [\text{Vector form}]$$

$$= \sqrt{10.87} = 3.297 A$$

$$a + b_j / a' + b'_j$$

$$a = 25 \cos 0^\circ = 25; b = 25 \sin 0^\circ = 0$$

$$a' = 34.33 \cos \pi = -34.33;$$

$$b' = -34.33 \sin \pi = 0$$


Same answer for polar form.

$$\theta = \tan^{-1} \left(\frac{X_C}{R} \right) = \tan^{-1} \left(\frac{26.54}{20} \right) = \tan^{-1} (1.327) = 53^\circ$$

$$I_{LO} = 3.297 \angle 53^\circ A$$

$$Z = \frac{V_{LO}}{I_{LO}} = \frac{500 \angle 0^\circ}{3.297 \angle 53^\circ} = 22.748 \angle -53^\circ \Omega$$

Q)

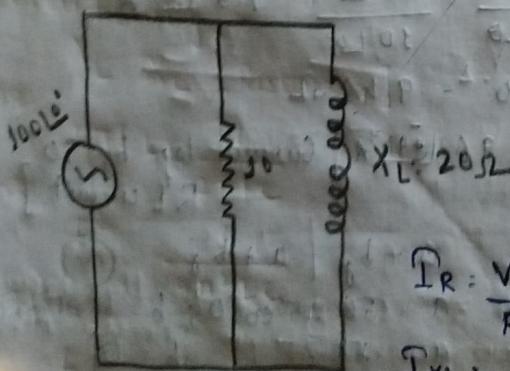

Given,

$$V = 500 \angle 0^\circ V$$

$$R = 10 \Omega$$

$$X_L = 20 \Omega$$

$$I_R = \frac{V_{LO}}{R_{LO}} = \frac{500 \angle 0^\circ}{10 \angle 0^\circ} = 50 A$$

$$I_{XL} = \frac{V}{X_L} = \frac{500 \angle 0^\circ}{20 \angle 90^\circ} = 5 \angle -90^\circ A$$

$$\angle LO = I_R - j I_{XL}$$

= $50 \angle 0^\circ - 5 \angle 90^\circ$ [Magnitude in case of RL-circuit]

$$I = \sqrt{(50)^2 + (5)^2} = \sqrt{525} = 22.91 A$$

$$\theta = \tan^{-1} \left(-\frac{5}{10} \right) = \tan^{-1} \left(-\frac{1}{2} \right) = \tan^{-1} (0.5) = -26.56^\circ$$

$$\cos \theta = \cos (-26.56^\circ) = \cos (26.56^\circ) = 0.89 \text{ [Power factor]}$$


$$Z = \frac{V_{LD}}{I_{LD}} = \frac{100 \angle 0^\circ}{15.18 \angle -26.56^\circ} = 8.94 \angle 26.56^\circ \Omega$$

$$Z_1 = 50 \angle 0^\circ; Z_2 = 20 \angle 90^\circ$$

[Verified!]

$$Z = \frac{Z_1 Z_2}{Z_1 + j Z_2} = \frac{50 \angle 0^\circ \times 20 \angle 90^\circ}{10 + (0 + j 20)} = \frac{200 \angle 90^\circ}{50 + j 20} = \frac{200 \angle 90^\circ}{22.36 \angle 63.4^\circ} = 8.94 \angle 26.56^\circ$$

Q)

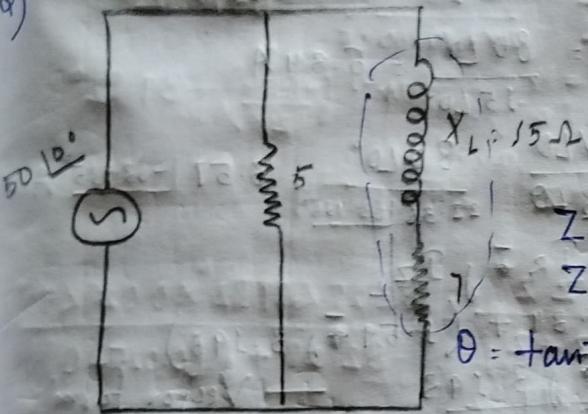

Given,

$$V = 50 \angle 0^\circ V$$

$$X_L = 15 \Omega$$

$$Z_2 = \sqrt{R^2 + (X_L)^2} = \sqrt{7^2 + 15^2}$$

$$Z_2 = \sqrt{49 + 225} = \sqrt{274} = 16.55 \Omega$$

$$\theta = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{15}{7} \right) = 64.9^\circ$$

$$Z_2 = 16.55 \angle 64.9^\circ \Omega$$

$$I_R = \frac{50 \angle 0^\circ}{8 \angle 0^\circ} = 50 A$$

$$I_{Z_2} = \frac{V_{LD}}{Z_2 \angle 0^\circ} = \frac{50 \angle 0^\circ}{16.55 \angle 64.9^\circ} = 3.02 \angle -64.9^\circ$$

$$I_{Z_2} = 1.28 - j 2.7 \text{ [Vector form]}$$

$$I_{LD} = I_R + j I_{Z_2} (G_R)$$

$$= 50 + j 1.28 - j 2.7$$

$$= 55.28 - j 2.7$$

$$I = \sqrt{(55.28)^2 + (2.7)^2} = \sqrt{3072.2384 + 7.29} = \sqrt{3184.5284} = 55.59 A$$

$$\theta = \tan^{-1} \left(\frac{-2.7}{55.28} \right) = -53.46^\circ$$

$$I_{LD} = 55.59 \angle -13.46^\circ A$$

$$Z = \frac{V_{LD}}{I_{LD}} = \frac{50 \angle 0^\circ}{55.59 \angle -13.46^\circ} = 4.81 \angle 13.46^\circ \Omega$$

$$Z = \frac{Z_1 Z_2}{Z_1 + j Z_2} = \frac{5 \angle 0^\circ \times 16.55 \angle 64.9^\circ}{5 + (0 + j 15)} = \frac{82.75 \angle 64.9^\circ}{52 + j 15}$$

$$= \frac{82.75 \angle 64.9^\circ}{59.2 \angle 15.94^\circ} = 4.31 \angle 13.46^\circ \Omega \text{ [Hence Verified!]}$$

GIVEN.

$$V = 80 \text{ LD}^\circ \text{ V}$$

$$X_L = 20 \Omega$$

$$Z_2 = \sqrt{R^2 + X_L^2} = \sqrt{(20)^2 + (10)^2}$$

$$Z_2 = \sqrt{400 + 100} = \sqrt{500} = 22.36 \Omega$$

$$\theta = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left(\frac{10}{20} \right) = 63.43^\circ$$

$$Z_2 \angle 9^\circ = 22.36 [63.43^\circ] \Omega \quad I_R = \frac{80 \text{ LD}^\circ}{15 \Omega} = 5.34 \text{ A}$$

$$T_{22} \cdot \frac{VLD}{Z_2 \angle 9^\circ} = \frac{80 \text{ LD}^\circ}{22.36 [63.43^\circ]} = 3.57 [-63.43^\circ] \text{ A}$$

$$Z_2 \angle 9^\circ = I_R + j T_{22}$$

$$= 5.34 + (3.57 + j 3.593)$$

$$= 6.93 + j 3.593 \quad \text{--- Vector form}$$

$$T = \sqrt{(6.93)^2 + (3.593)^2} = 7.63; \theta = \tan^{-1} \left(\frac{3.593}{6.93} \right) = -29.73^\circ$$

$$TLD = 7.63 \angle -29.73^\circ \text{ A} \quad [\text{Again converted to polar}]$$

$$Z = \frac{VLD}{TLD} = \frac{80 \text{ LD}^\circ}{7.63 \angle -29.73^\circ} = \frac{80}{7.63} \text{ LD}^\circ - (-29.73^\circ) = 10.48 \angle 24.73^\circ \Omega$$

$$Z = \frac{Z_1 Z_2}{Z_1 + j Z_2} = \frac{15 \text{ LD}^\circ \times 22.36 [63.43^\circ]}{15 + (50 + 20j)} = \frac{335.4 [63.43^\circ]}{25 + 20j}$$

$$= \frac{335.4 [63.43^\circ]}{32.055 [38.66^\circ]} = 10.48 \angle 24.73^\circ \Omega \quad [\text{Hence Verified!}]$$

Resonance :-

When the input frequency of the AC circuit gives zero phase difference between voltage and current, then the resonance of the given AC circuit can be calculated.

Conditionally,

$$X_L = X_C \quad [\text{Resonance}]$$


$$\text{OR, } 2\pi f L = \frac{1}{2\pi f C}$$

$$\text{OR, } f^2 = \frac{1}{4\pi^2 LC}$$

Thus,

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ rad} \quad [\text{In radians}]$$
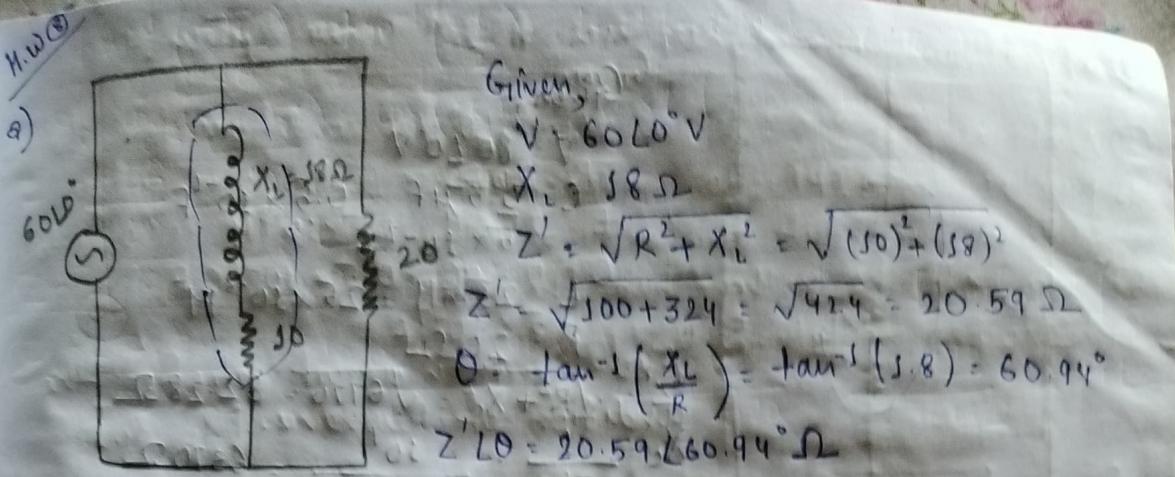
$$f = \frac{1}{\sqrt{LC}} \text{ Hz} \quad [\text{In Hz}]$$



$I_R = \frac{60 L 0^\circ}{20 L 0^\circ} = 3 \text{ A}$; $I_{2'} = \frac{60 L 0^\circ}{20.59 L 60.94^\circ} = 2.914 L - 0.94^\circ \text{ A}$

$I_{L0} = I_R - j I_{2'} \quad [\text{Inductor representation}]$

$$= 3 + (j.45 - 2.54j)$$

$$= 4.45 - 2.54j$$

$$I = \sqrt{(4.45)^2 + (2.54)^2} = \sqrt{39.44 + 6.45} = \sqrt{25.89} = 5.08 \text{ A}$$

$\theta = \tan^{-1}\left(\frac{-2.54}{4.45}\right) = \tan^{-1}(-0.576) = -29.94^\circ$; $I_{L0} = 5.08 L -29.94^\circ \text{ A}$

$$Z = \frac{V_{L0}}{I_{L0}} = \frac{60 L 0^\circ}{5.08 L -29.94^\circ} = 11.81 L +29.94^\circ \Omega$$

a)

Given,

$$V = 50 L 0^\circ \text{ V}$$

$$X_L = 50 \Omega$$

$$Z' = \sqrt{R^2 + X_L^2} = \sqrt{(20)^2 + (50)^2} = \sqrt{400 + 2500} = 25.49 \Omega$$

$$Z = \sqrt{650} = 25.49 \Omega$$

$$\theta = \tan^{-1}\left(\frac{-X_C}{R}\right) = \tan^{-1}\left(\frac{-50}{20}\right) = -68.19^\circ$$

$$Z' L \theta = 25.49 L -68.19^\circ \Omega$$

$I_R = \frac{50 L 0^\circ}{20 L 0^\circ} = 5 \text{ A}$; $I_{2'} = \frac{50 L 0^\circ}{25.49 L -68.19^\circ} = 1.96 L 68.19^\circ \text{ A}$

$I_{L0} = I_R + j I_{2'}$

$$= 5 + (0.72 + j 1.82)$$

$$= 5.72 + j 1.82$$

$$I = \sqrt{(5.72)^2 + (1.82)^2} = \sqrt{32.71 + 3.31} = 5.72 \text{ A}$$

$$I = \sqrt{36.02} = 6 \text{ A (Approx.)}$$

$\theta = \tan^{-1}\left(\frac{1.82}{5.72}\right) = \tan^{-1}(0.31) = 17.22^\circ$


$I_{L0} = 6 L 17.22^\circ$

$$Z = \frac{V_{L0}}{I_{L0}} = \frac{50 L 0^\circ}{6 L 17.22^\circ} = 8.34 L -17.22^\circ \Omega$$

Natural and forced Responses in 2nd Order System :-


① Natural Response : When certain initial conditions for the input is set. It is a system response with some initial conditions, without any external force and $x(t)$ is set to be zero. $y(t)$ is nothing but the input.

Symbolic Representation : $y_n(t)$

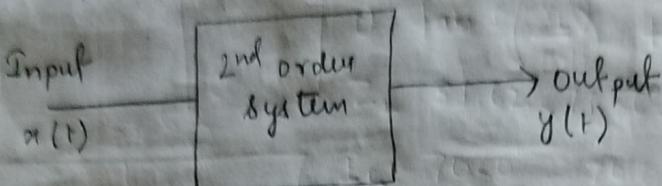

② Forced Response : It is a system response with some external force ($y_p(t)$) with all the initial condition set to be zero.

Symbolic Representation : $y_f(t)$

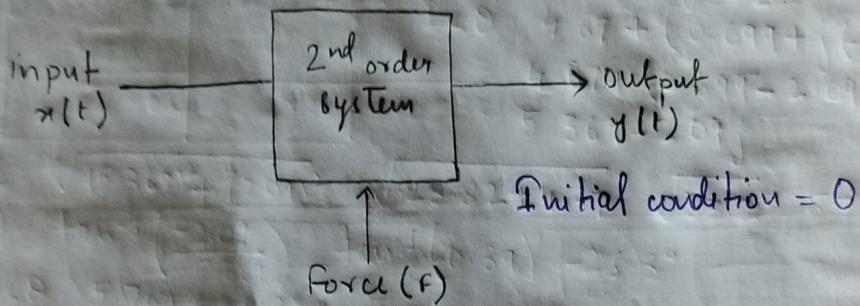


③ Total Response : Natural Response + Forced Response

Symbolic Representation : $y_t(t)$

$$y_t(t) = y_n(t) + y_f(t)$$

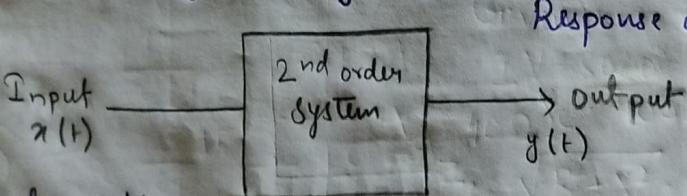Addition of Natural Response and forced Response.



Initial condition $\neq 0$

$y_p(t)$ [External force]

$$\frac{d^2}{dt^2} y(t) + 5 \frac{d}{dt} y(t) + 6 y(t) = -\frac{d}{dt} x(t) + y_p(t)$$

$$x(t) = e^{-t} u(t)$$

unit response = 1

(i) Natural Response :-

$$y(0) = 3 ; \frac{d}{dt} y(0) = 0$$

$$(1+2)(1+3) = 0$$

$$\frac{d^2}{dt^2} y(t) + 5 \frac{d}{dt} y(t) + 6 y(t) = 0$$

$$\lambda = -2 \mid \lambda = -3$$

$$\lambda^2 + 5\lambda + 6 = 0 \quad [y(t) = \lambda]$$

$$\lambda^2 + 3\lambda + 2\lambda + 6 = 0$$

$$\lambda(\lambda+3) + 2(\lambda+3) = 0$$

Homogeneous solutions :-

$$y_n(t) = C_1 e^{-2t} + C_2 e^{-3t}$$

$$y(0) = 3 \Rightarrow C_1 + C_2 = 0 \quad \text{--- (i)}$$

$$\frac{dy}{dt}(0) = 0 \Rightarrow -2C_1 - 3C_2 = 0$$

$$2C_1 + 3C_2 = 0 \quad \text{--- (ii)}$$

Solving eqn (i) and (ii) we get,

$$C_1 = 9 \text{ and } C_2 = -6$$

(iii) Forced Response :-

$$x(t) = e^{-t} (s) = e^{-t} \text{ [Given]}$$

$$y_p(t) = ke^{-t} \text{ [External force acting]}$$

$$\frac{d}{dt} y_p(t) = -ke^{-t}; \quad \frac{d^2}{dt^2} y_p(t) = ke^{-t}$$

$$\frac{d}{dt} x(t) = -e^{-t}$$

$$ke^{-t} + 5(-ke^{-t}) + G(ke^{-t}) = -e^{-t} + 4e^{-t}$$

$$ke^{-t} - 5ke^{-t} + 6ke^{-t} = 3e^{-t}$$

$$2ke^{-t} = 3e^{-t}$$

$$k = \frac{3}{2} = 1.5$$

Forced Response : $y_n(t) + y_p(t)$

$$= C_1 e^{-2t} + C_2 e^{-3t} + 1.5e^{-t}$$

$$y(0) = 0 \Rightarrow \frac{dy}{dt}(0) = 0$$

$$\text{Thus, } C_1 + C_2 + 1.5 = 0 \quad \text{--- (iii)}$$

Now,

$$\frac{dy}{dt} = -2e^{-2t} C_1 - 3e^{-3t} C_2 = 1.5e^{-t}$$

$$\frac{d}{dt} y(0) = -2C_1 - 3C_2 + 1.5 = 0 \quad \text{--- (iv)}$$

Solving eqn (iii) and (iv), we get,

$$C_1 = -3 \text{ and } C_2 = 1.5$$

$$y_F(t) = -3e^{-2t} + 1.5e^{-3t} + 1.5e^{-t}$$



$$\text{And, } y_F(t) = y_n(t) + y_F(t)$$

$$= 9e^{-2t} - 6e^{-3t} - 3e^{-2t} + 1.5e^{-3t} + 1.5e^{-t}$$



$$= 6e^{-2t} - 4.5e^{-3t} + 1.5e^{-t} \text{ [Total Response]}$$

$$(22.16 + 0.5e^{-3t}) + 1.5e^{-2t} - 8e^{-t}$$

$$8.5e^{-2t} + 1.5e^{-t}$$

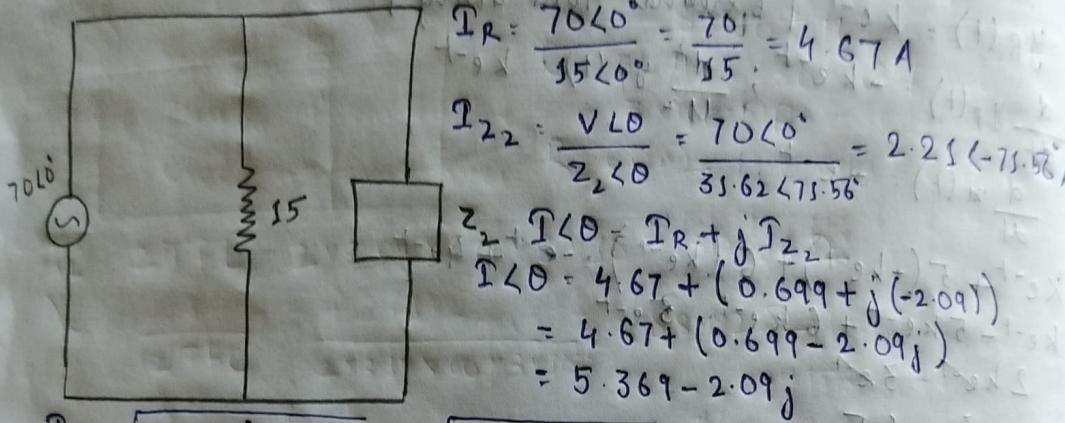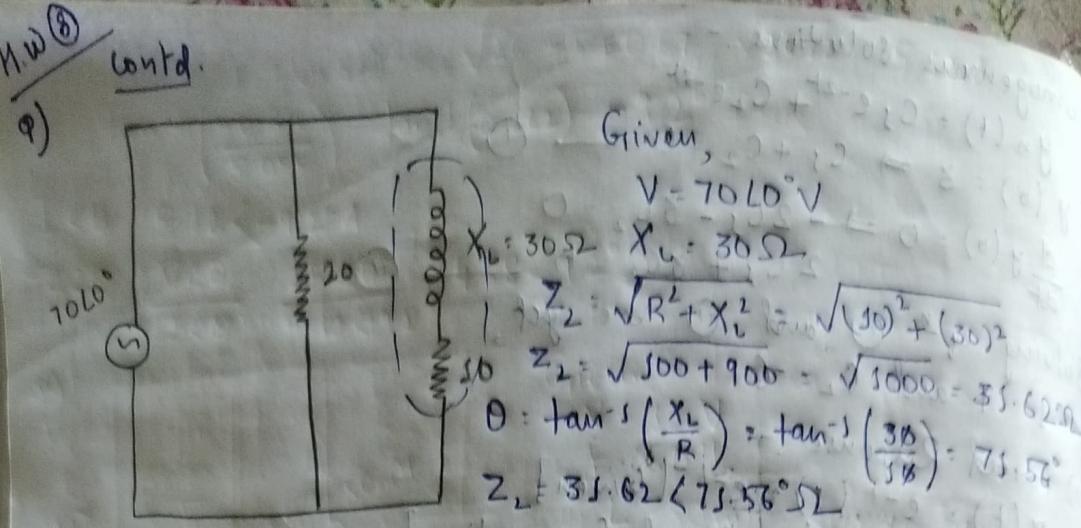

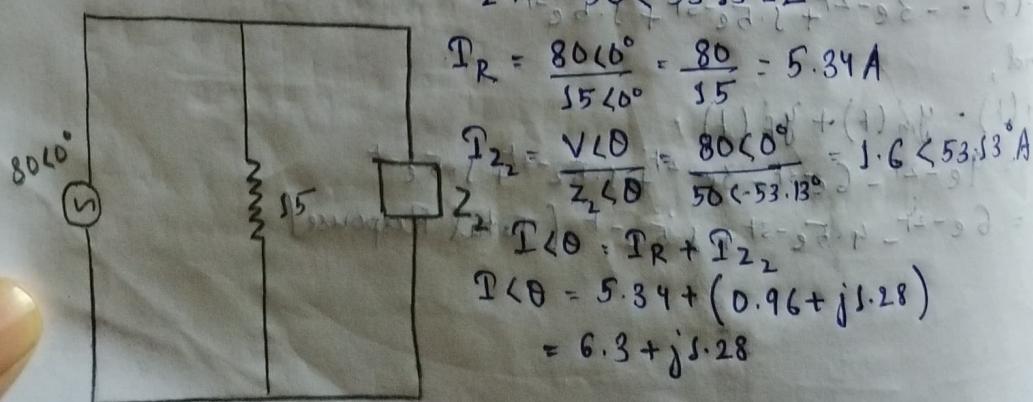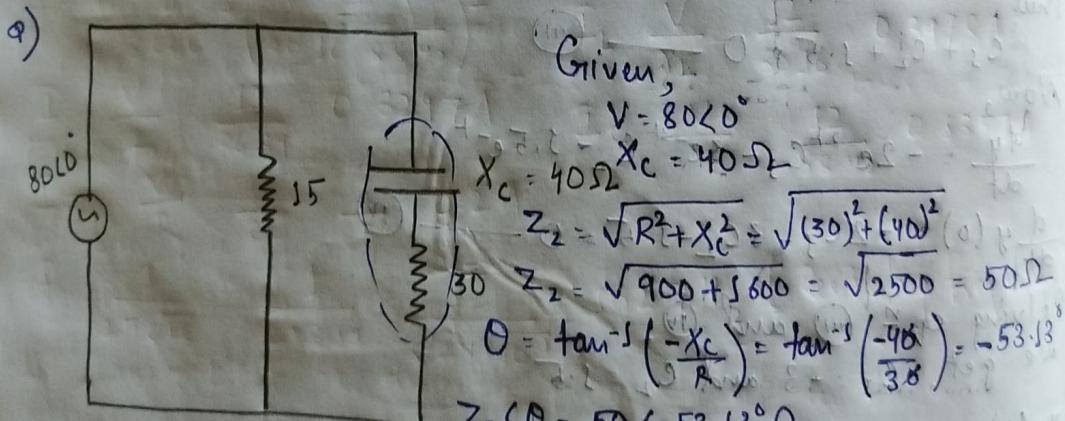$I = \sqrt{(5.369)^2 + (2.09)^2} = \sqrt{28.82 + 4.37} = \sqrt{33.2} = 5.762 \text{ A}$
 $\theta = \tan^{-1}\left(\frac{-2.09}{5.369}\right) = \tan^{-1}(0.39) = -23.3^\circ$
 $I \angle \theta = 5.762 \angle -23.3^\circ \text{ A}$
 $Z = \frac{V_{L0}}{I \angle \theta} = \frac{70\angle 0^\circ}{5.762 \angle -23.3^\circ} = 12.348 \angle +23.3^\circ \Omega$




$$I = \sqrt{(6.3)^2 + (1.28)^2} = \sqrt{89.69 + 1.64} = \sqrt{91.33} = 9.54 A$$

$$\theta = \tan^{-1}\left(\frac{1.28}{6.3}\right) = \tan^{-1}(0.203) = 11.475^\circ$$

$$I \angle \theta = 9.54 \angle 11.475^\circ A$$
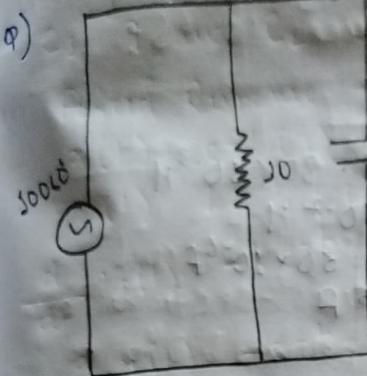
$$Z \angle \theta = \frac{V \angle \theta}{I \angle \theta} = \frac{80 \angle 0^\circ}{9.54 \angle 11.475^\circ} = 8.44 \angle -11.475^\circ \Omega$$



Given,

$$R = 10 \Omega$$

$$X_C = 20 \Omega \quad X_C = 20 \Omega$$

$$V = 100 \angle 0^\circ V$$

$$I_R = \frac{V \angle \theta}{R \angle \theta} = \frac{100 \angle 0^\circ}{10 \angle \theta} = 10 A$$

$$I_{XC} = \frac{V}{X_C} = \frac{100 \angle 0^\circ}{20 \angle -90^\circ} = 5 \angle 90^\circ A$$

$$I \angle \theta = I_R + j I_{XC}$$

$$= 10 + (0 + 5j) \quad [\text{Magnitude in case of RC-circuit}]$$


$$= 10 + 5j$$

$$I = \sqrt{(10)^2 + (5)^2} = \sqrt{100 + 25} = \sqrt{125} = 11.18 A$$

$$\theta = \tan^{-1}\left(\frac{5}{10}\right) = \tan^{-1}\left(\frac{1}{2}\right) = \tan^{-1}(0.5) = 26.56^\circ$$

$$\cos \theta = \cos(26.56^\circ) = 0.89 \quad [\text{power-factor}]$$
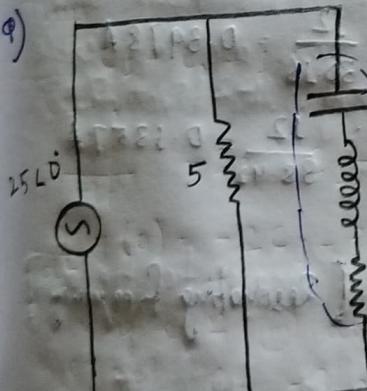
$$Z = \frac{V \angle \theta}{I \angle \theta} = \frac{100 \angle 0^\circ}{11.18 \angle 26.56^\circ} = 8.94 \angle -26.56^\circ \Omega$$



Given,

$$V = 25 \angle 0^\circ V$$

$$X_L = 50 \Omega \quad X_C = 20 \Omega$$


$$Z_2 = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(2)^2 + (50 - 20)^2}$$

$$Z_2 = \sqrt{4 + 900} = \sqrt{904} = 30.06 \Omega$$

$$\theta = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{50 - 20}{2}\right)$$

$$\theta = \tan^{-1}\left(\frac{30}{2}\right) = \tan^{-1}(15) = 86.59^\circ$$
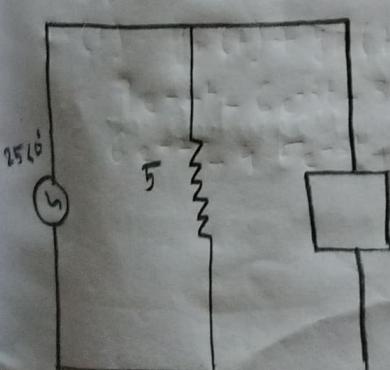
$$Z_2 \angle \theta = 30.06 \angle 86.59^\circ \Omega$$



$$I_R = \frac{25 \angle 0^\circ}{5 \angle 0^\circ} = \frac{25}{5} = 5 A$$

$$I_{Z_2} = \frac{V \angle \theta}{Z_2 \angle \theta} = \frac{25 \angle 0^\circ}{30.06 \angle 86.59^\circ} = 0.83 \angle -86.59^\circ A$$

$$Z_2 \quad I \angle \theta = I_R + j I_{Z_2}$$

$$I \angle \theta = 5 + (0.055 - 0.82j)$$

$$= 5.055 - j0.82$$


$$I = \sqrt{(5.055)^2 + (0.82)^2} = \sqrt{25.55 + 0.67} = \sqrt{26.22} = 5.12 A$$

$$\theta = \tan^{-1}\left(\frac{-0.82}{5.055}\right) = \tan^{-1}(0.362) = -9.2^\circ$$

$$I < 0 = 5.12 < -9.2^\circ A$$

$$Z < 0 = \frac{V < 0}{I < 0} = \frac{25 < 0^\circ}{5.12 < -9.2^\circ} = 4.88 < 9.2^\circ \Omega$$

Q)

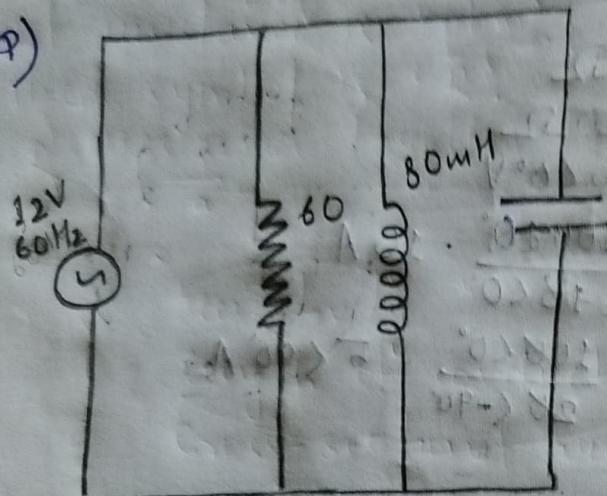

Given,

$$V = 32 V$$

$$f = 60 \text{ Hz}$$

$$30 \mu F \quad L = 80 \text{ mH} = 80 \times 10^{-3} \text{ H} \\ = 8 \times 10^{-2} \text{ H}$$

$$C = 30 \mu F = 30 \times 10^{-6} \text{ F} \\ = 3 \times 10^{-5} \text{ F}$$

$$R = 60 \Omega$$

$$X_L = 2\pi f L = 2 \times 3.14 \times 60 \times 8 \times 10^{-2} = 30.16 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 60 \times 3 \times 10^{-5}} = 88.42 \Omega$$

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{60}\right)^2 + \left(\frac{1}{30.16} - \frac{1}{88.42}\right)^2}}$$

$$= \frac{1}{36.39} = 36.39 \Omega$$

$$\frac{1}{\sqrt{\frac{1}{3600} + \left(\frac{1}{30.16} - \frac{1}{88.42}\right)^2}} \quad I_L = \frac{V}{X_L} = \frac{32}{30.16} = 0.3978 A$$

$$I = \frac{V}{Z} = \frac{32}{36.39} = 0.8297 A \quad I_C = \frac{V}{X_C} = \frac{32}{88.42} = 0.357 A$$

$$I_R = \frac{V}{R} = \frac{32}{60} = \frac{1}{5} = 0.2 A$$

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times 3.14 \times \sqrt{24 \times 10^{-5}}} = 502.7 \text{ Hz} \quad [\text{Resonating Frequency}]$$