


Module - 3 : DC Circuit Analysis

Ohm's Law :-

Current is directly proportional to voltage (in a DC circuit).

Mathematically,
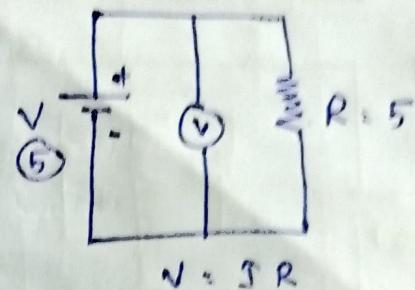
$$\left. \begin{array}{l} V = IR \\ \Rightarrow I = \frac{V}{R} \\ \Rightarrow R = \frac{V}{I} \end{array} \right\} \text{Depending upon the question}$$




As we increase the voltage, the current increases and vice-versa.

NOTE :-

AC Representation :

Reason: Dimming of light isn't observed

because of such a small time interval.

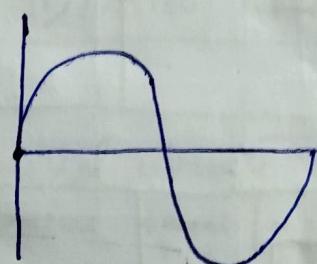

$$f = 50 \text{ Hz}$$

$$T = \frac{s}{f} = \frac{s}{50}$$

$$T = 0.02 \text{ s}$$

Series and Parallel Circuits :-


Series : $R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$ (n no. of resistors)







Parallel : $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$ (n no. of resistors)


* For 2 resistors in parallel :- [Reciprocal of result]

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad [R_{eq} : \text{Equivalent Resistance}]$$


a)

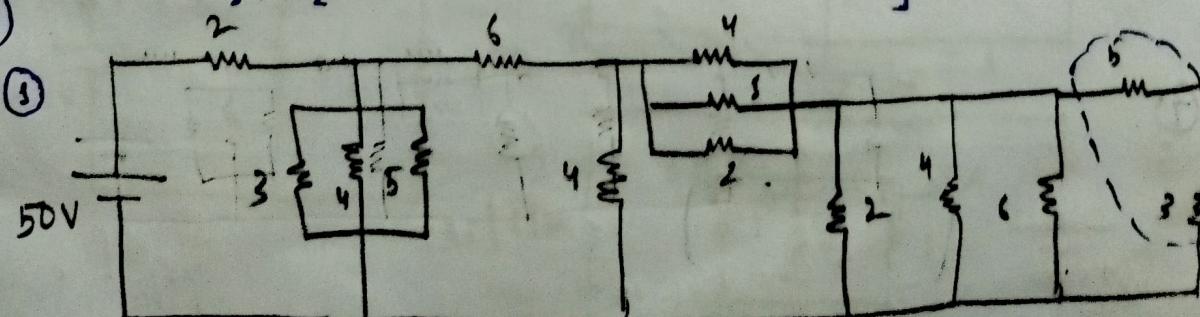

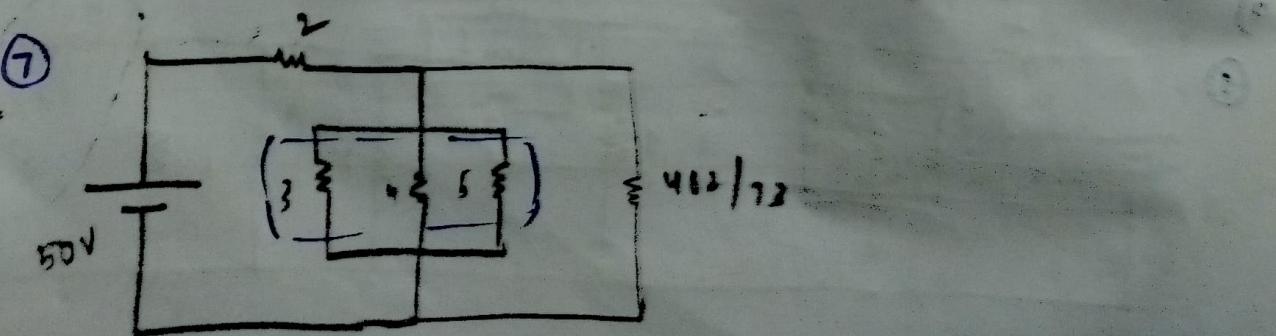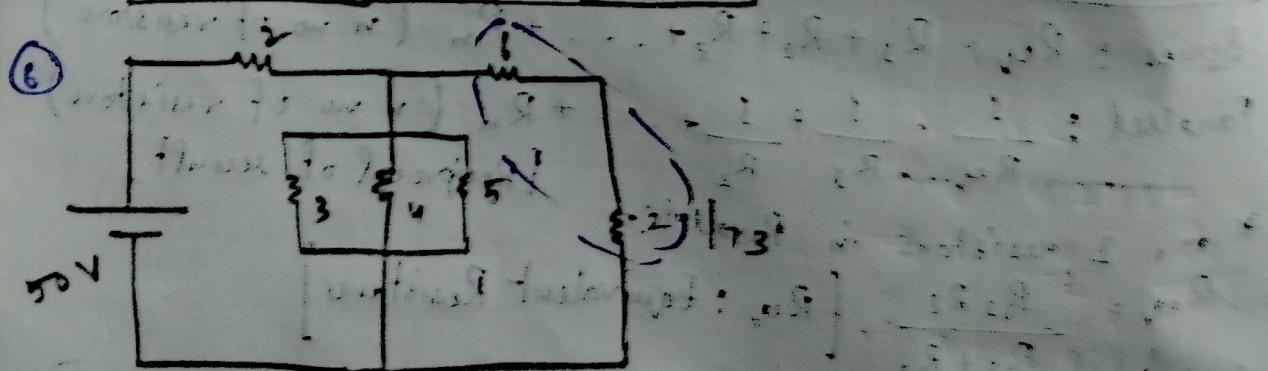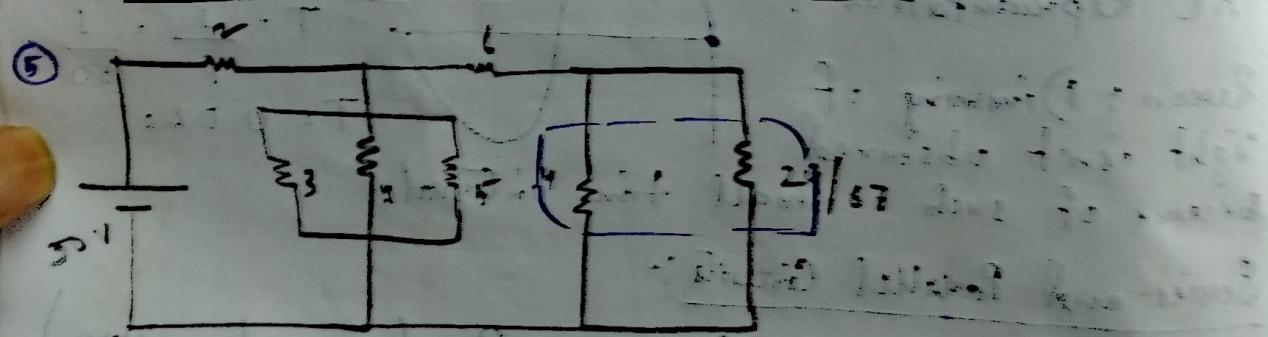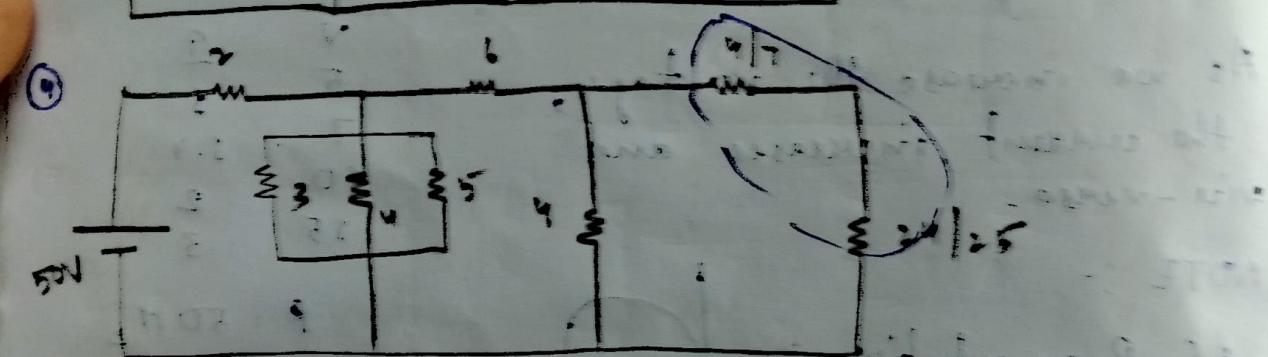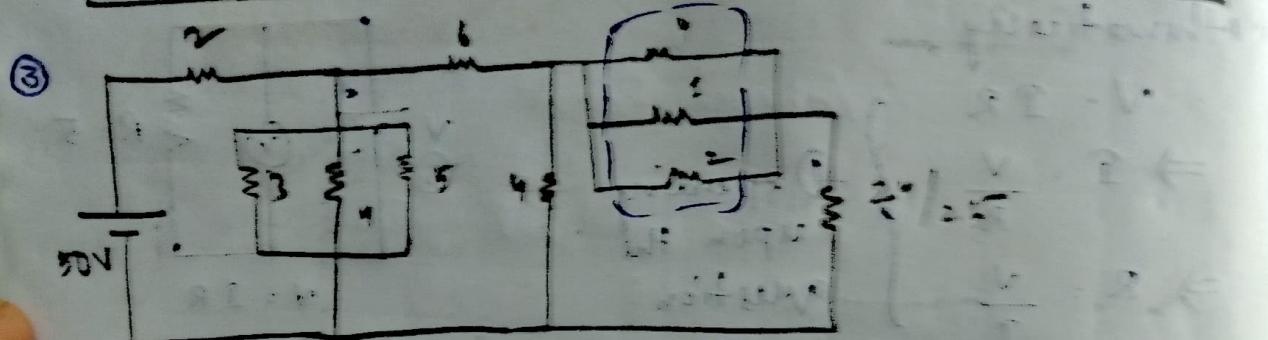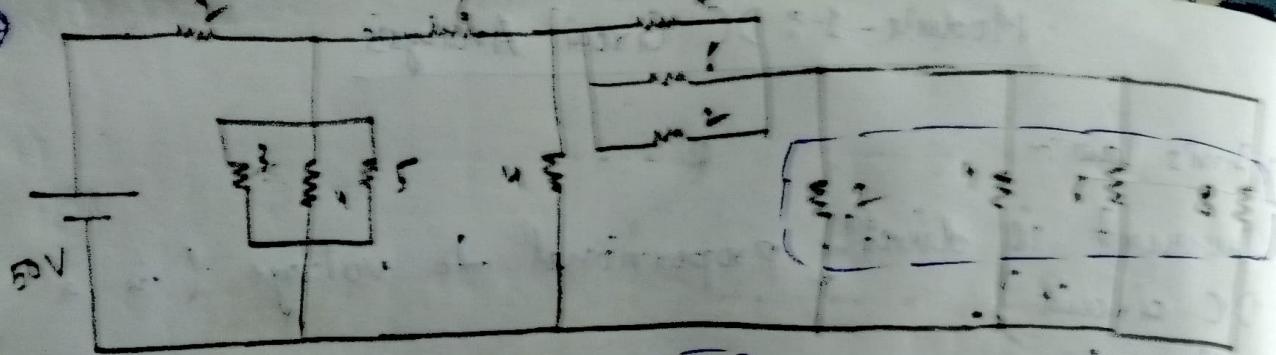


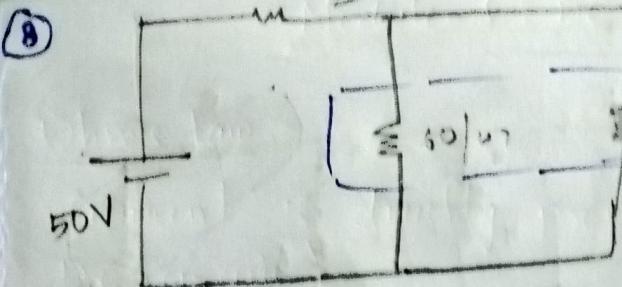

$$6.2 / 7.2$$

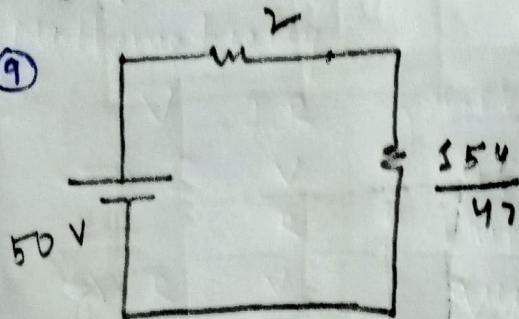

$$\frac{554}{47}$$

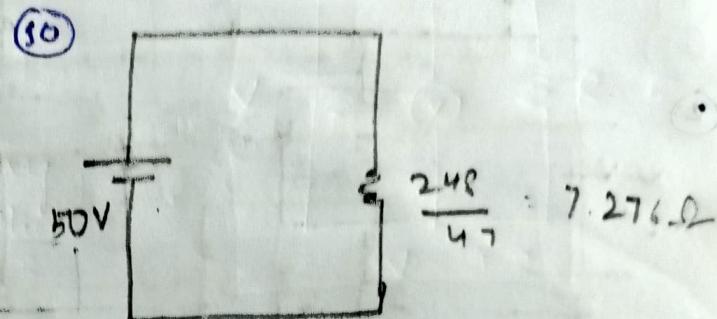

$$\frac{248}{47}$$

$$: 7.276.2$$

$$V = 50V ; I = ? \quad V = IR$$


$$R_{eq} = 7.276 \Omega \quad I = \frac{V}{R} = \frac{50}{7.276} = 6.87 A$$

Current And Voltage Division Rule :-

Current Division Rule :-

Applicable for only parallel circuits as current at every point / branch remains same / constant in case of series.


Maximum no. of resistors required = 2

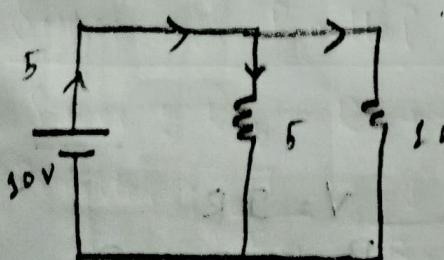

$$I_R = I_T \times \frac{\text{Opp. resistance}}{\text{Total resistance}}$$

$$I_{10} = 5 \times \frac{10}{15} = \frac{5}{3} \approx 1.67 A$$
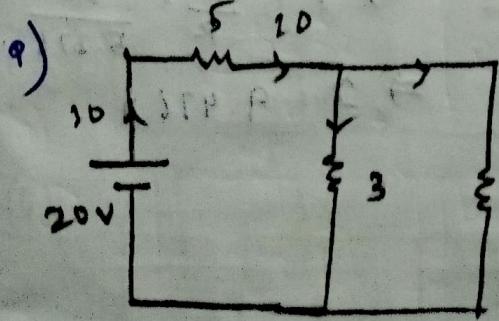
$$I_5 = 5 \times \frac{5}{15} = \frac{5}{3} \approx 1.67 A$$








$$I_5 = 5 A \text{ (no branch)}$$


$$I_3 = 5 \times \frac{7}{13} = 7 A$$

$$I_7 = 5 \times \frac{3}{13} = 3 A$$







H.W. ①

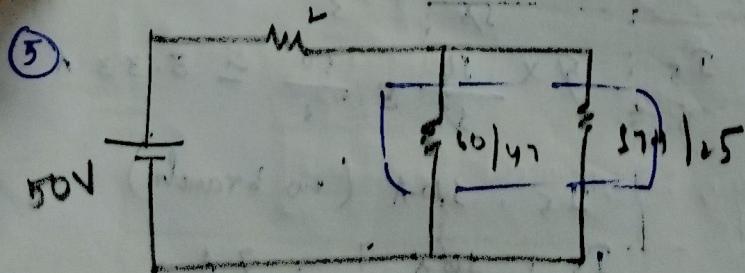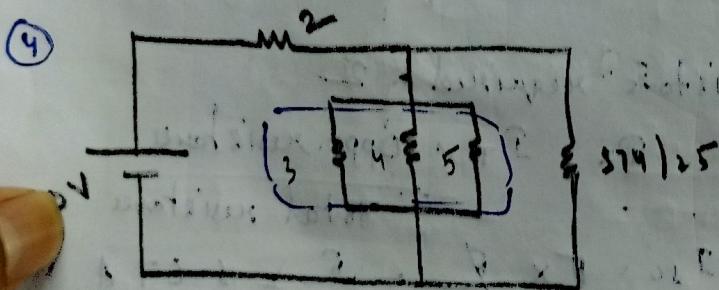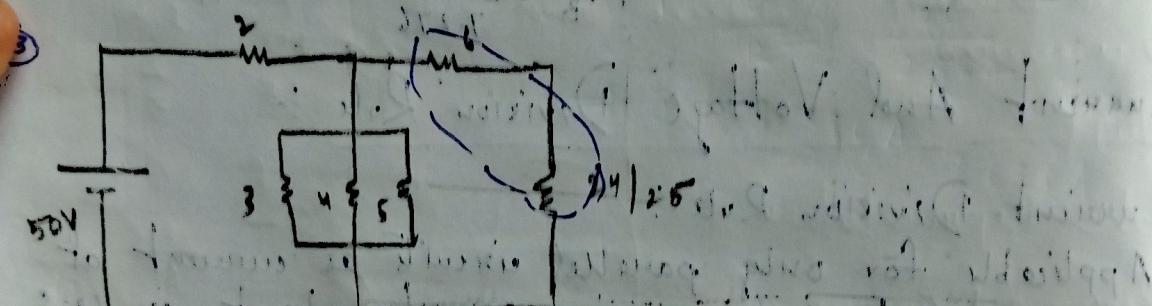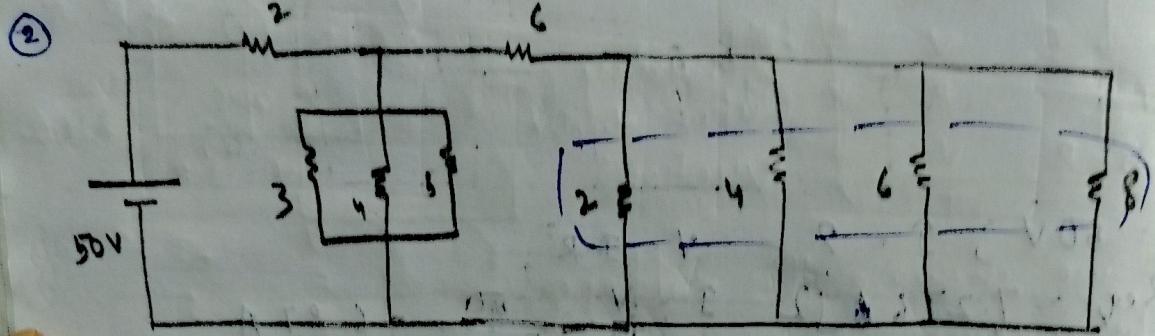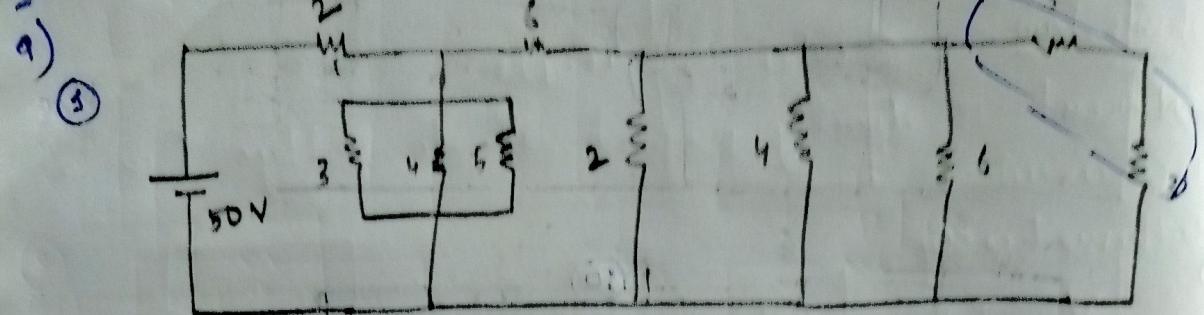

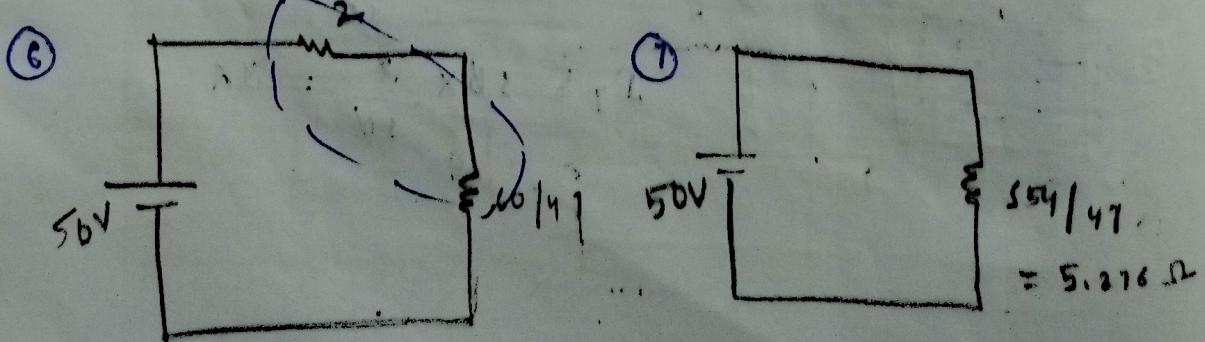
$$V = IR$$
$$R_{eq} = 5.276 \Omega$$
$$\Rightarrow I = \frac{V}{R} = \frac{50}{5.276}$$
$$\Rightarrow I = 9.476 A$$




$$554/47 = 5.276 \Omega$$

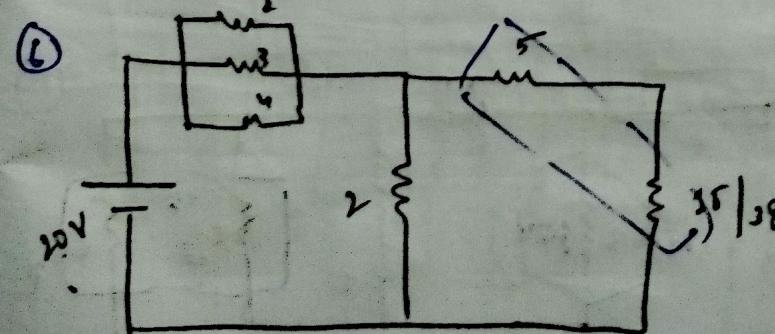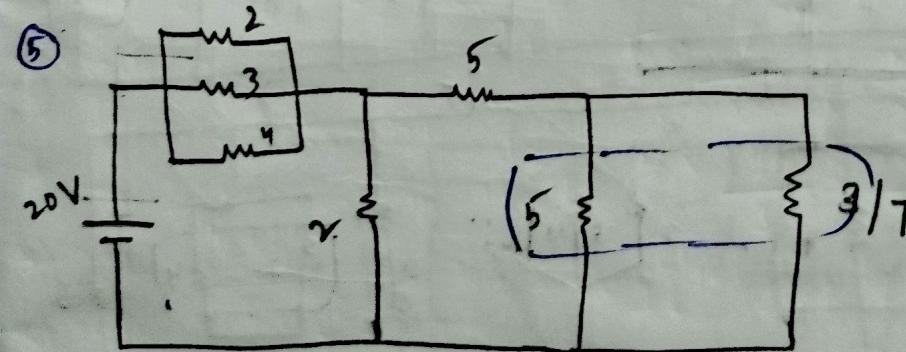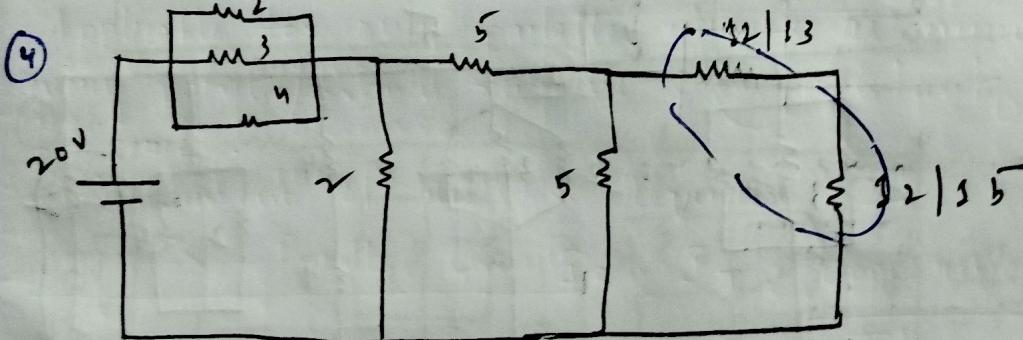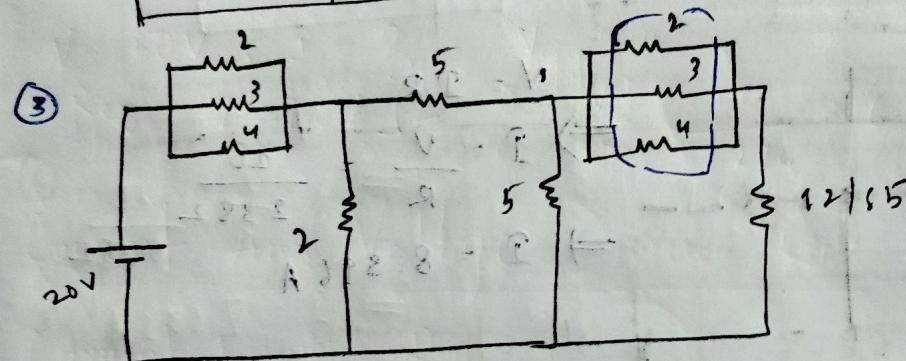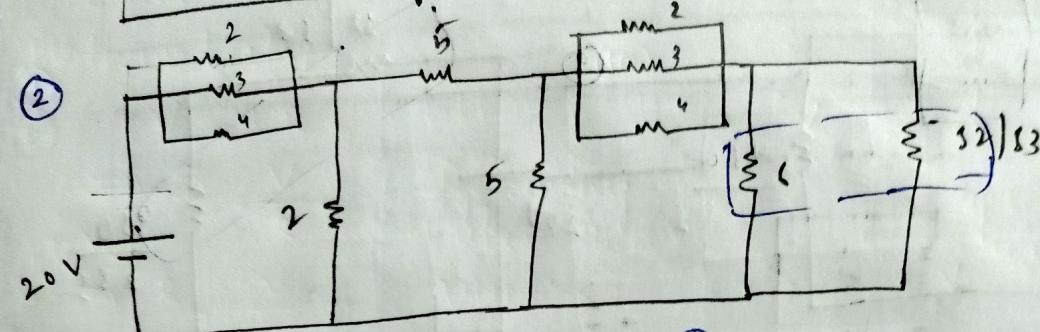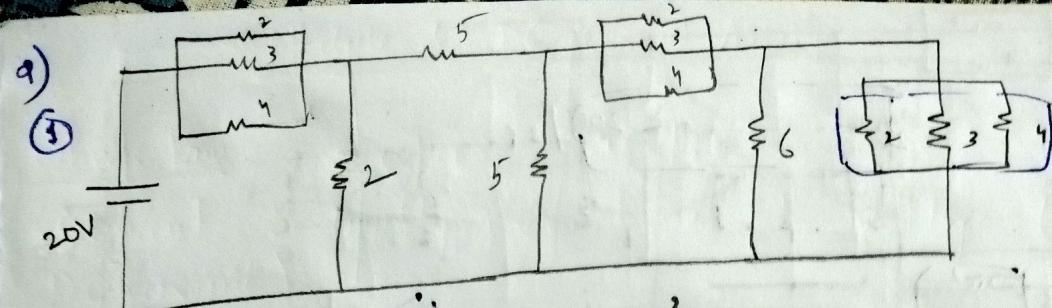


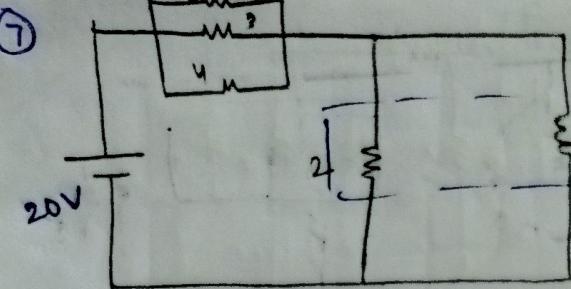


$$20V / 3\Omega$$

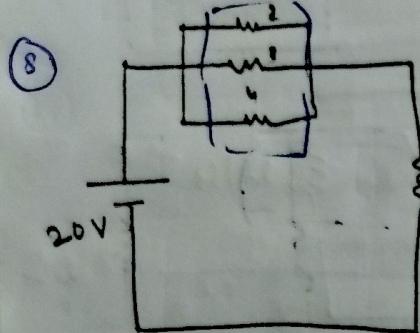




$$450 / 285$$






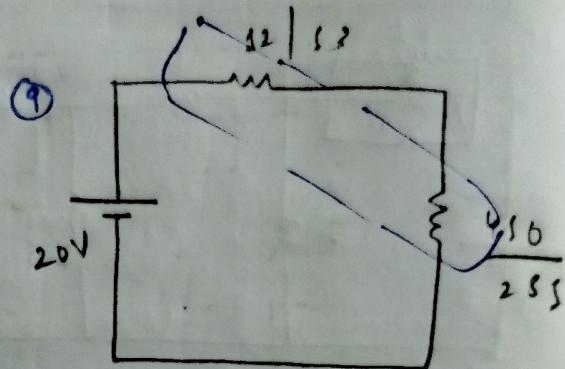


$$450 / 285$$

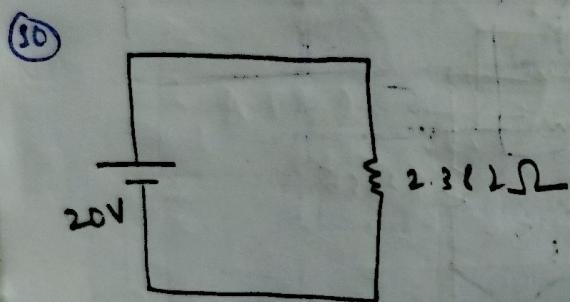

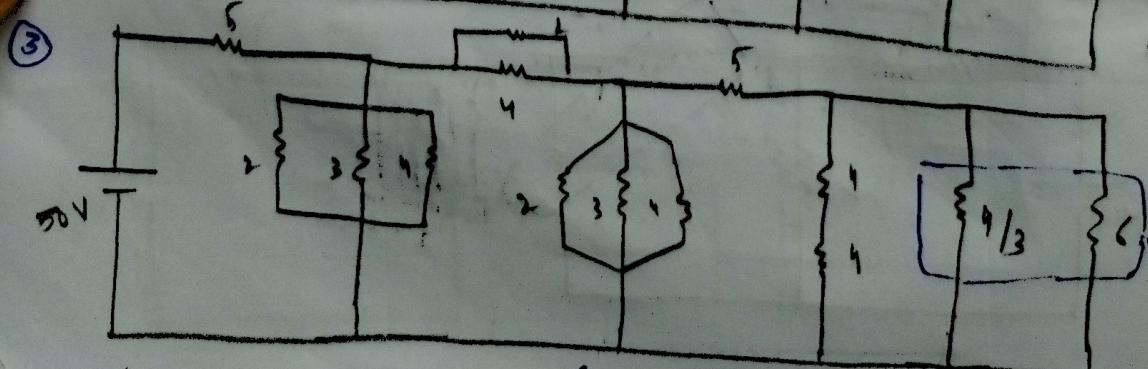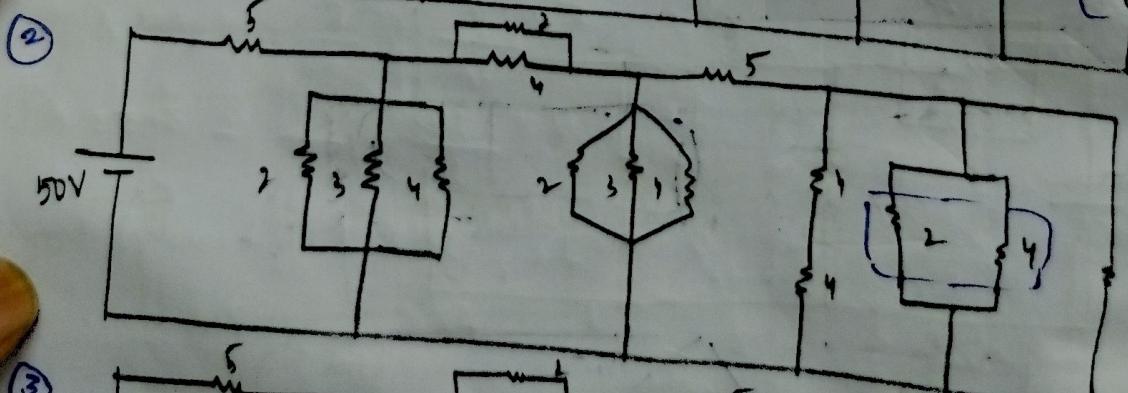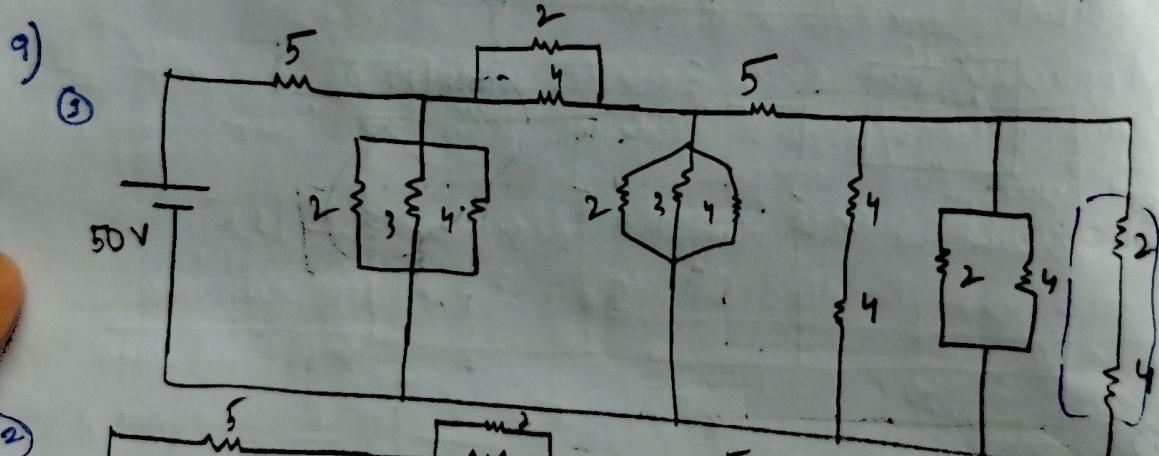
$$\begin{aligned} V &= IR \\ \Rightarrow I &= \frac{V}{R} = \frac{20}{2.382} \\ \Rightarrow I &= 8.396 A \end{aligned}$$




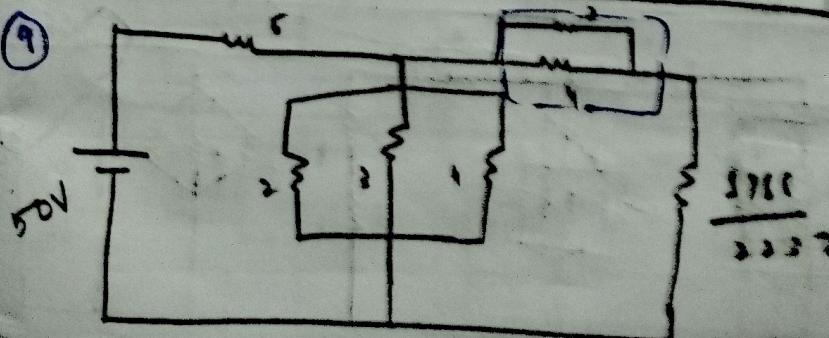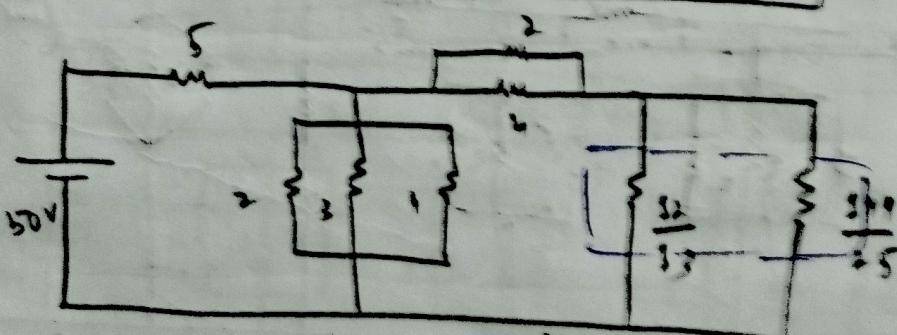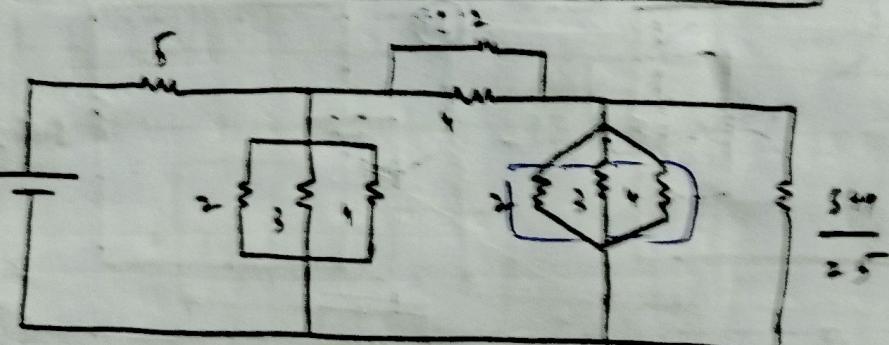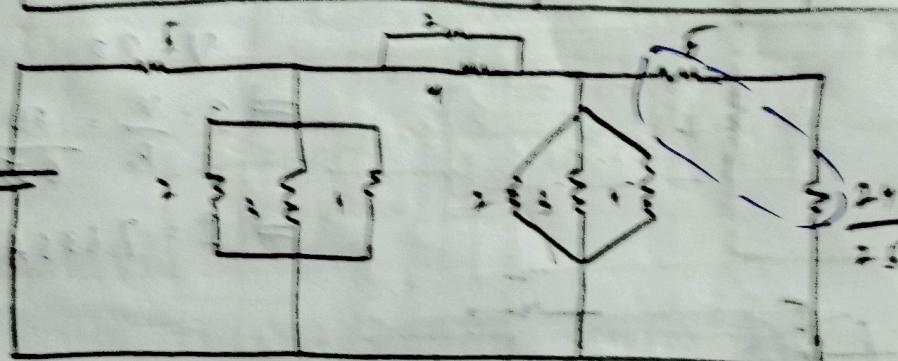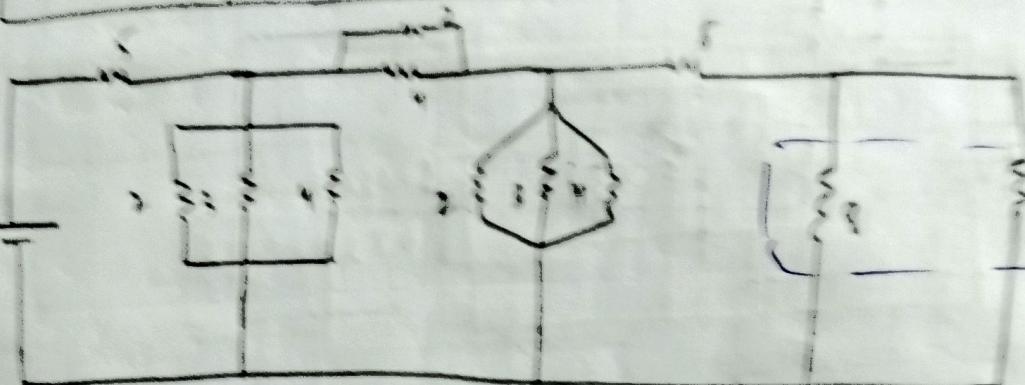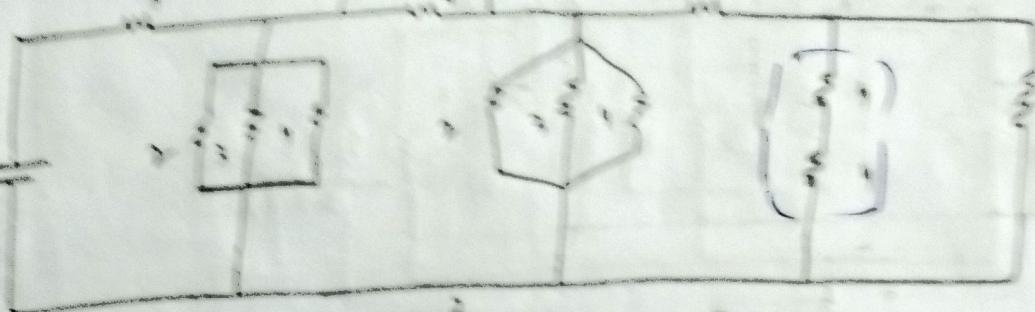


(30)

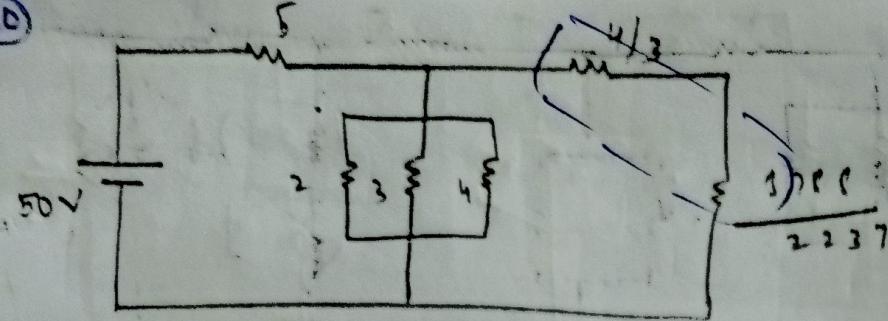


(31)

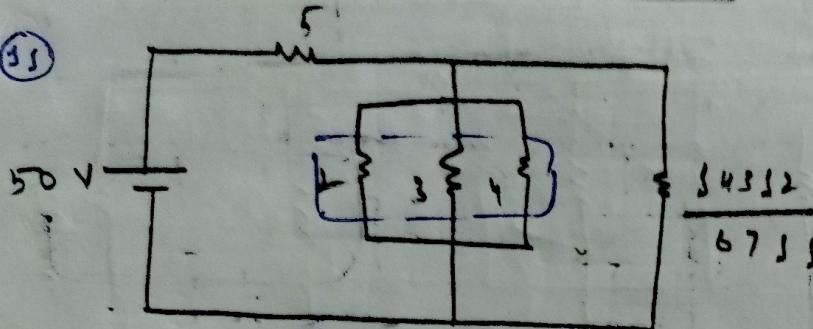


(32)

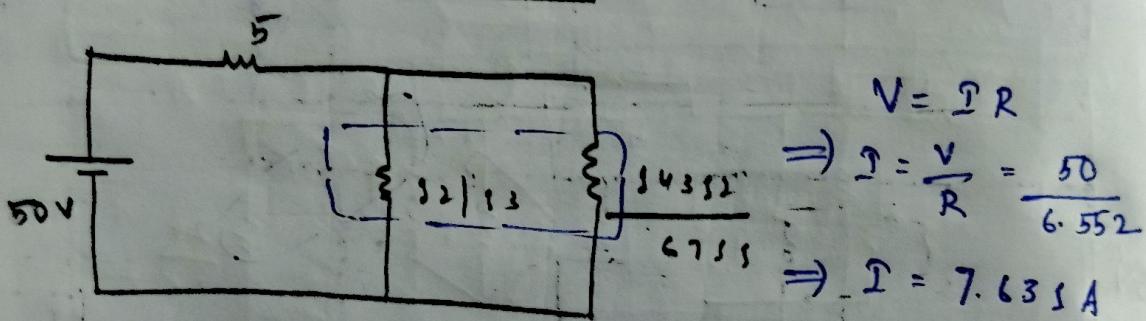


(33)

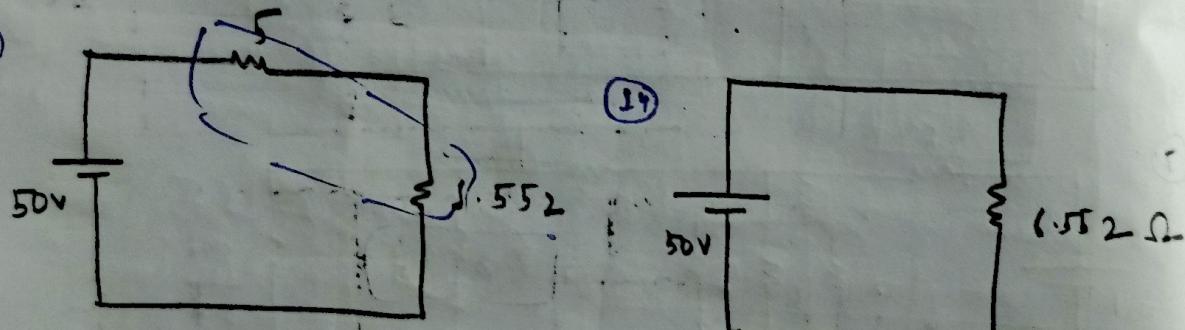


(34)






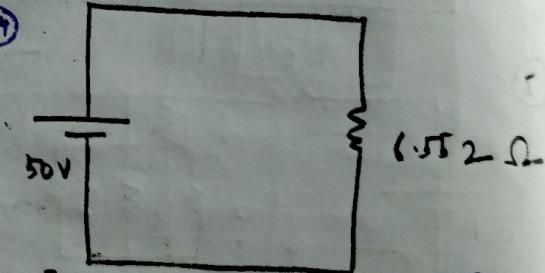








(35)

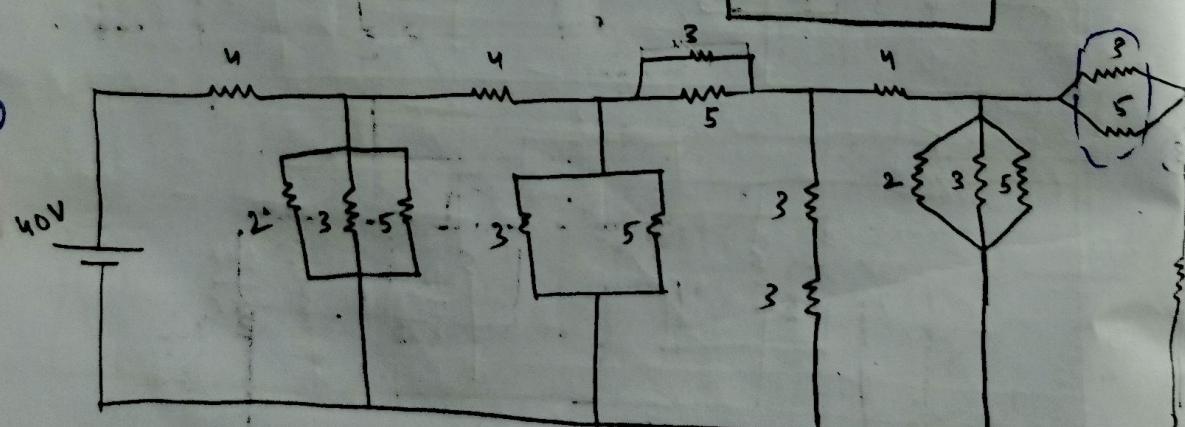


(2)

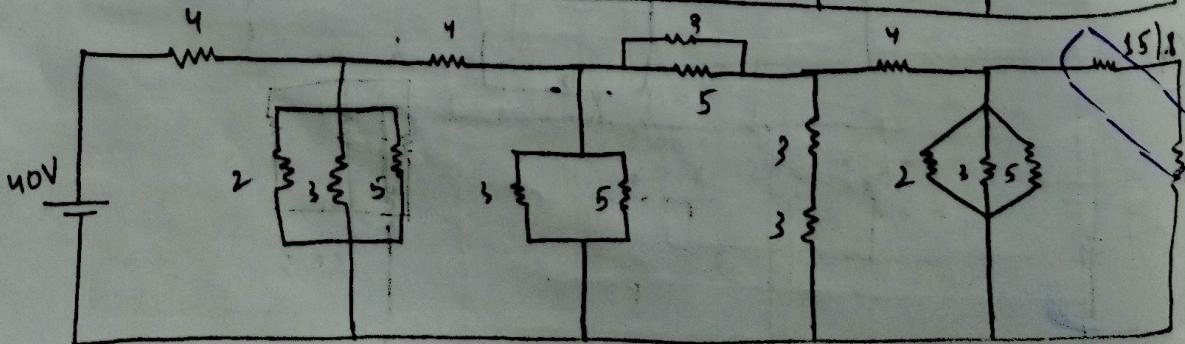

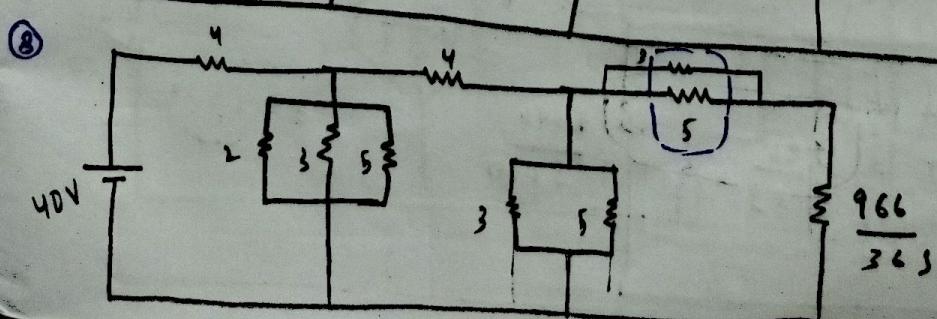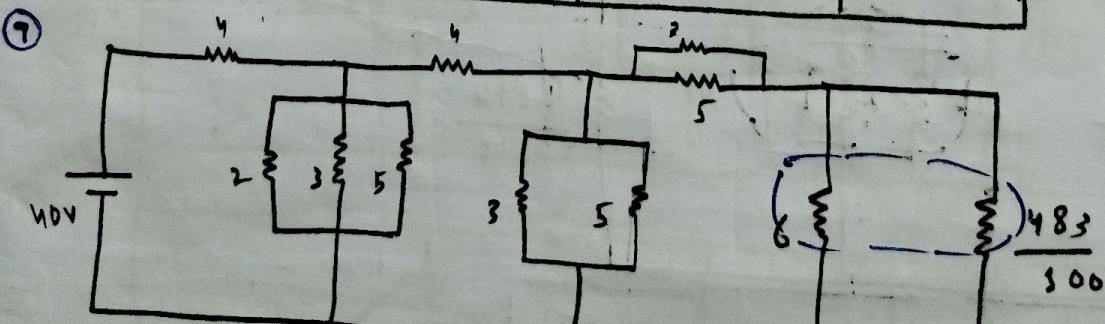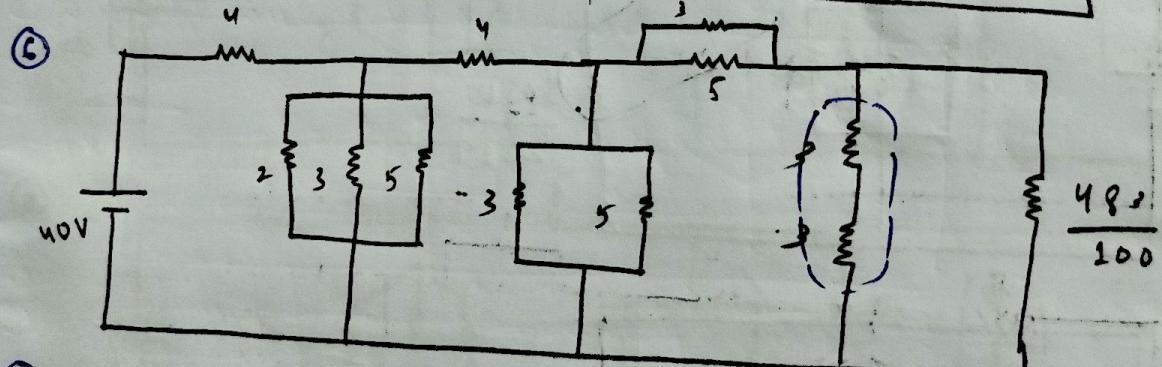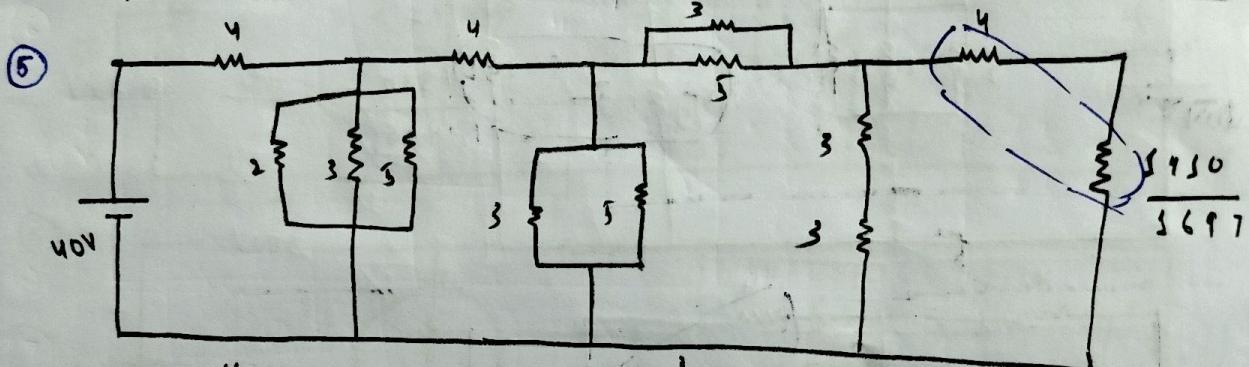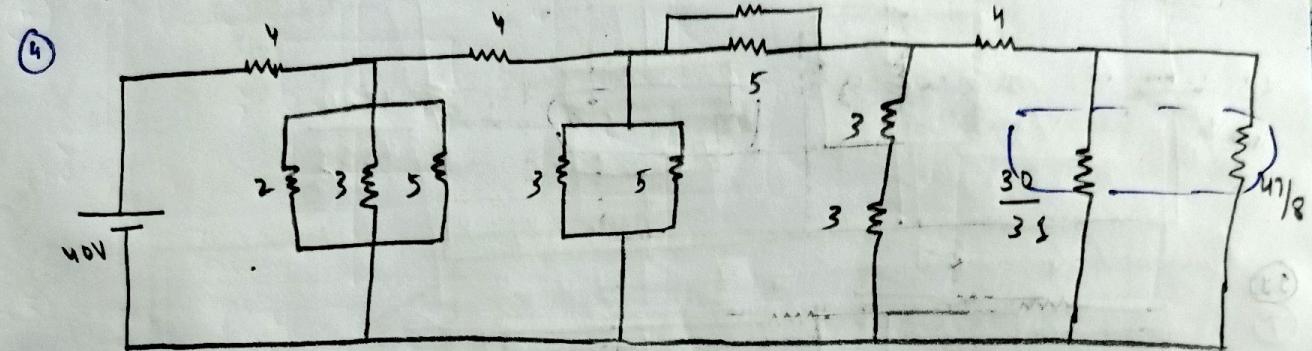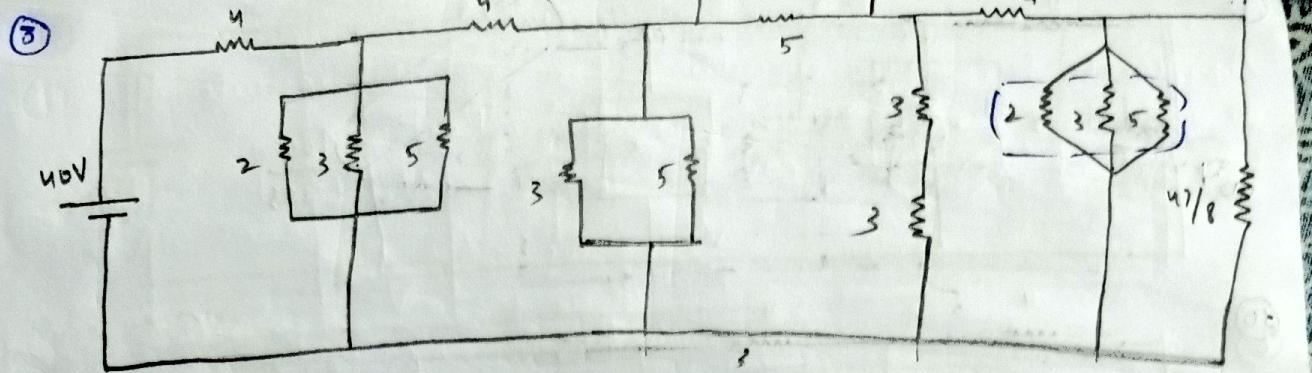


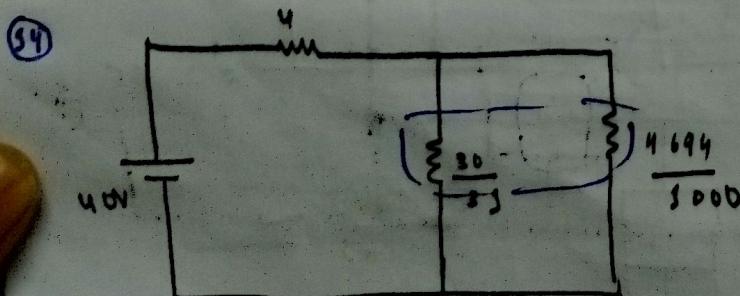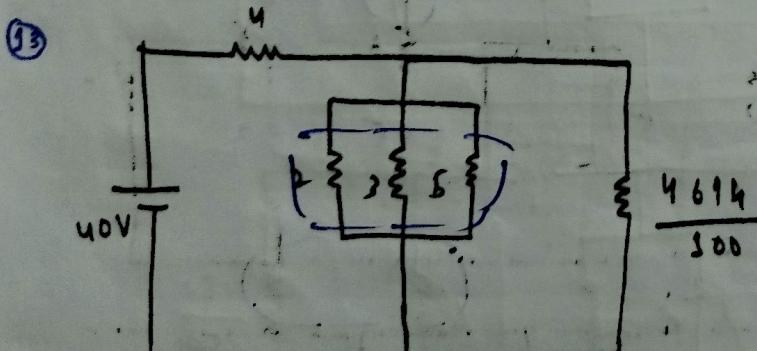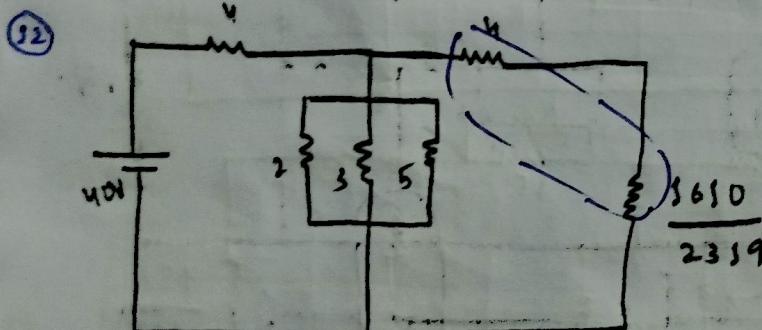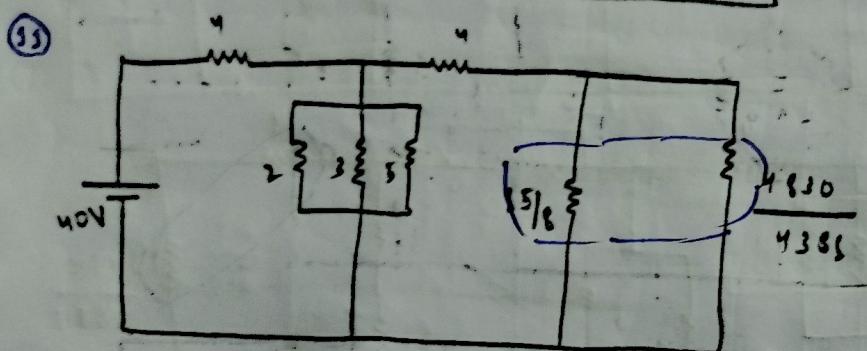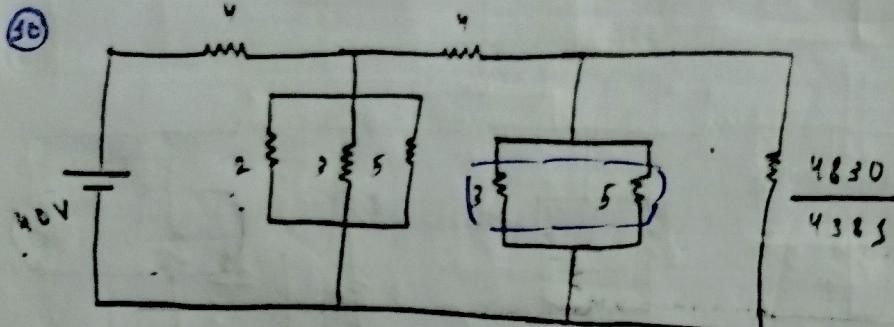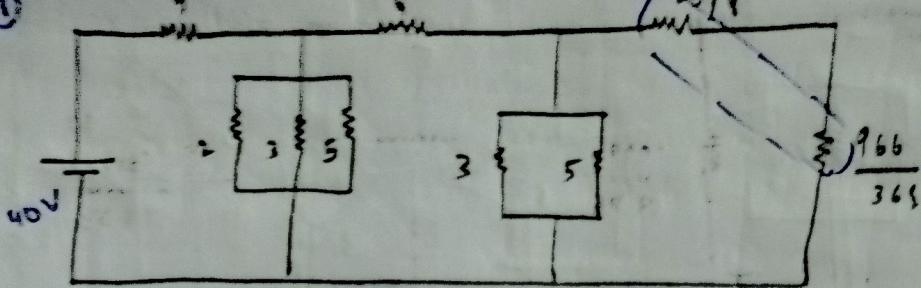

(35)

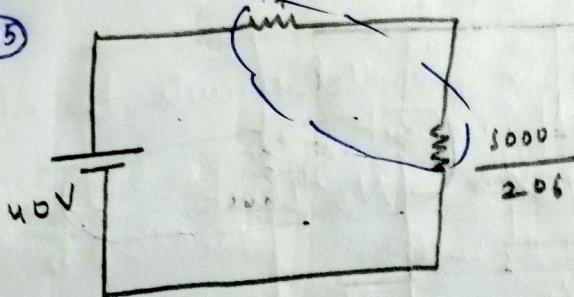

(36)

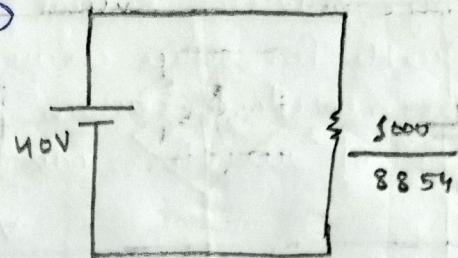

$$V = 40V$$


$$R_{eq} = \frac{5000}{8854} \Omega$$

$$V = IR \Rightarrow I = \frac{V}{R} = \frac{40}{\frac{5000}{25}} = 354.36A$$


(mathematically incorrect)

4)


(3)

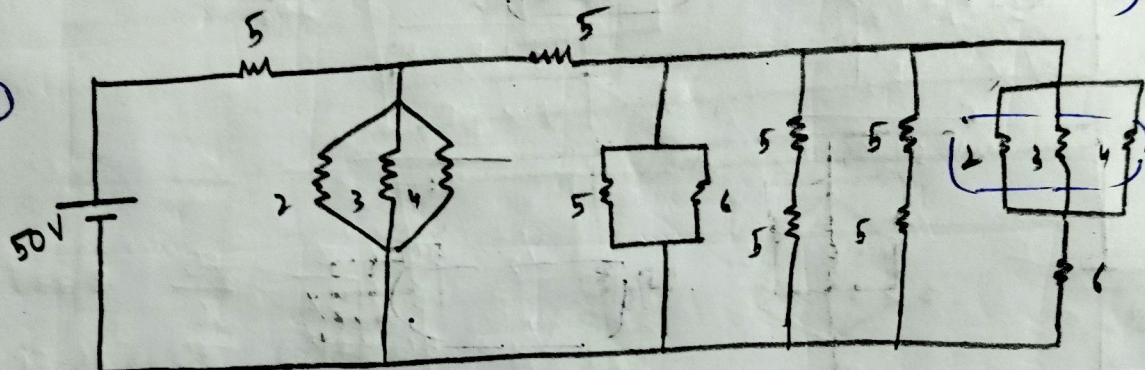


(2)






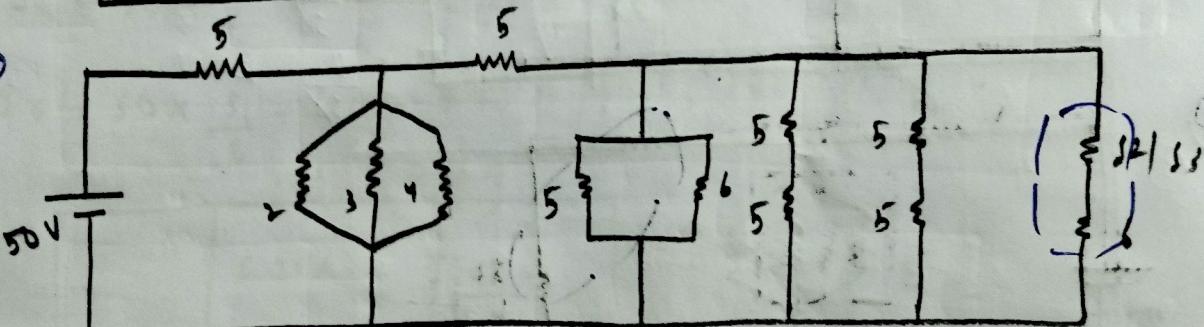


(3)

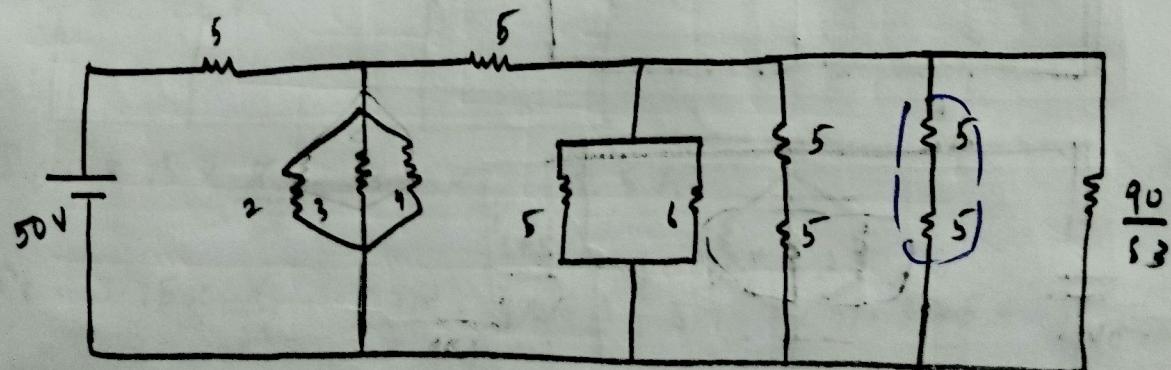


(4)

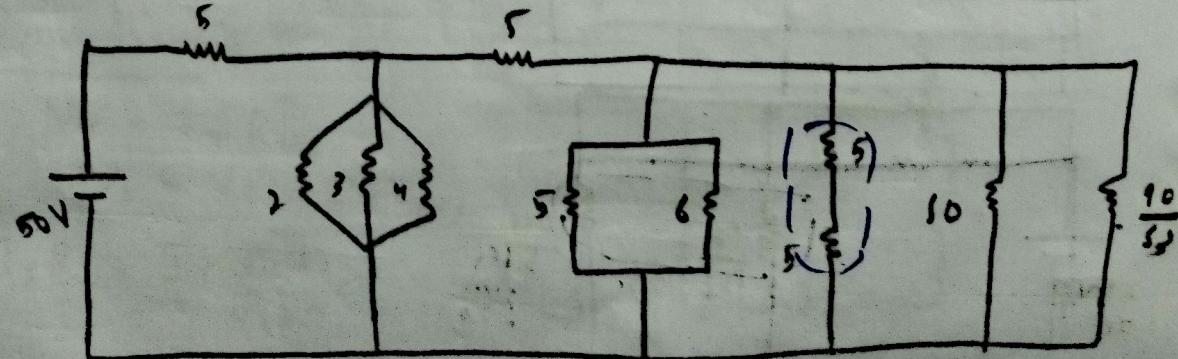


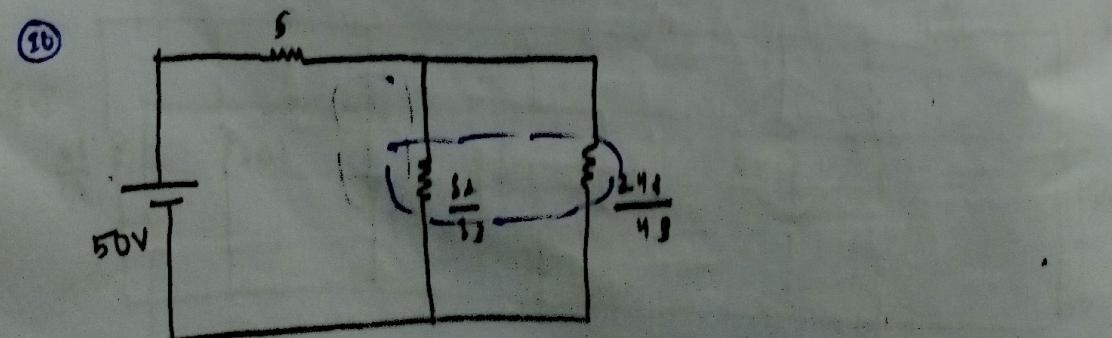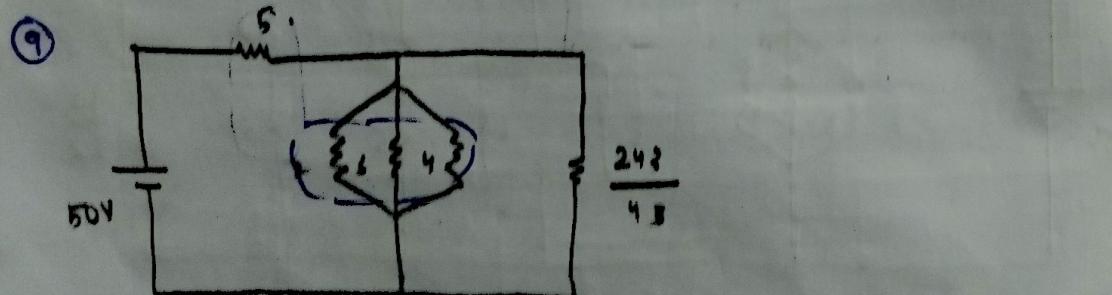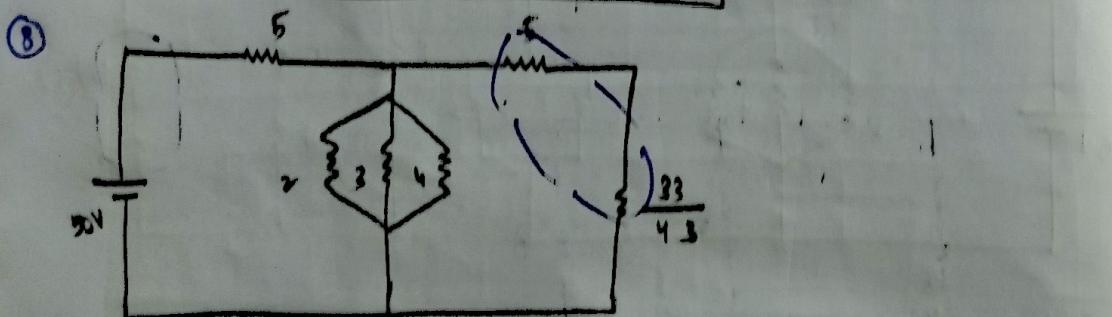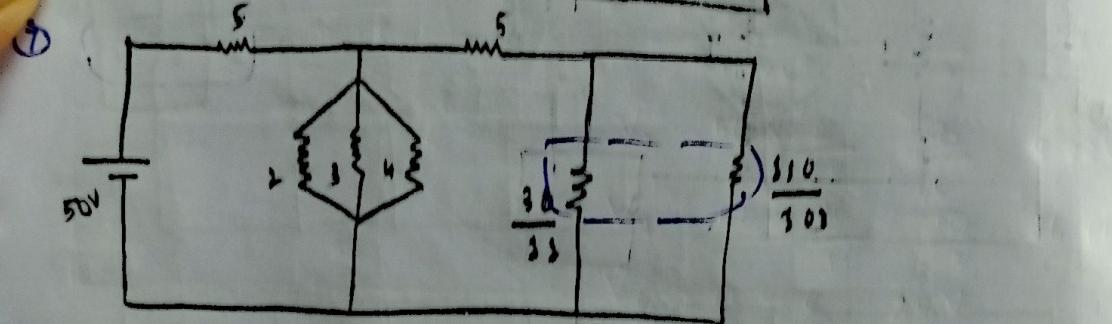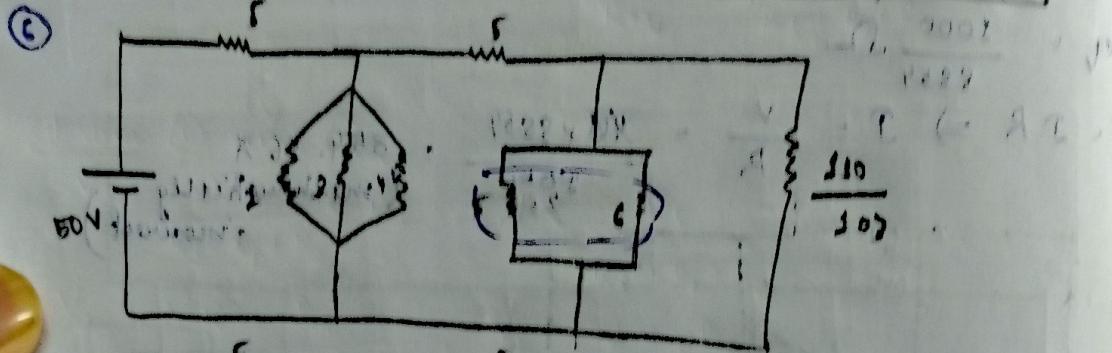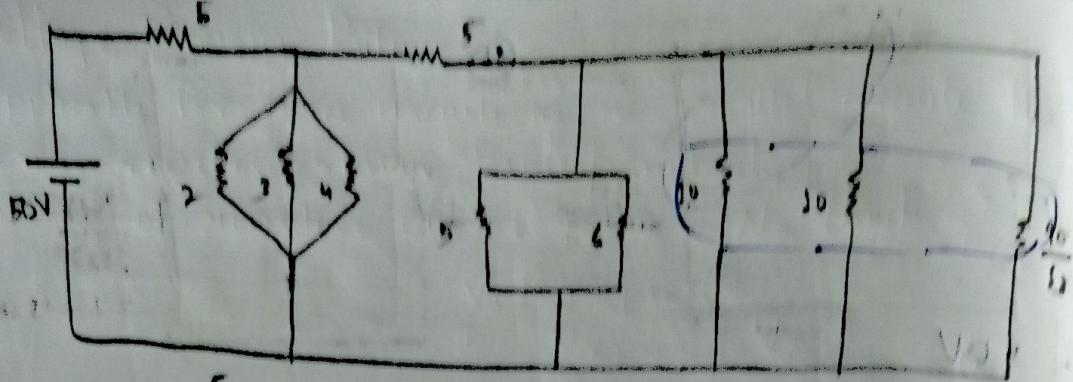

(11)

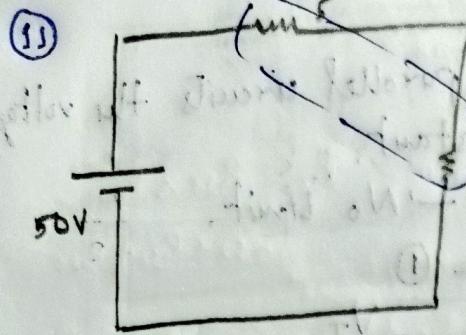

(12)

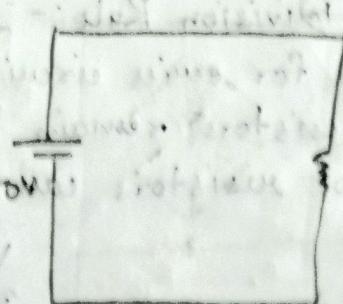


$$V = 50V$$

$$R_{eq} = 5.793 \Omega$$


$$V = IR \Rightarrow I = \frac{V}{R} = \frac{50}{5.793} = 8.683 A$$

a)

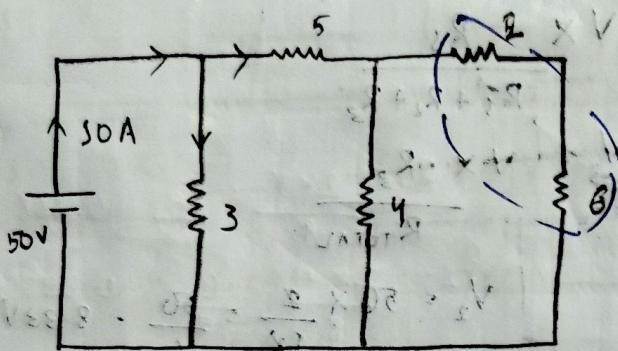

$$I_3 = 50 \times \frac{5}{8} = \frac{50}{8} = 6.25 A$$

$$I_4 = 50 \times \frac{3}{8} = \frac{50}{8} = 3.75 A \quad | \quad 50 - 6.25 = 3.75 A$$

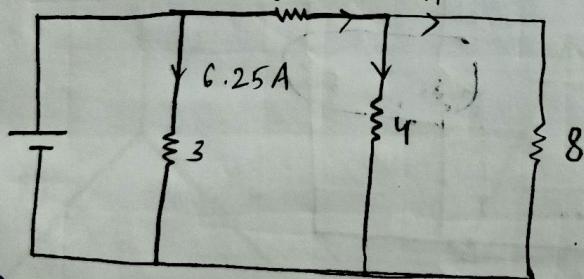

$$I_8 = 3.75 \times \frac{8}{3} = 3.75 \times \frac{2}{3} = 2.5 A$$

$$I_8 = 3.75 \times \frac{8}{3} = \frac{3.75}{3} = 1.25 A \quad | \quad 3.75 - 2.5 = 1.25 A$$


Derivation :-

$$V_T = I_T R_{eq}$$

$$V_S = V_T = I_T R_{eq}$$

$$I_S R_S = I_T \frac{R_S R_L}{R_S + R_L}$$


$$I_S = I_T \frac{R_2}{R_S + R_2}$$

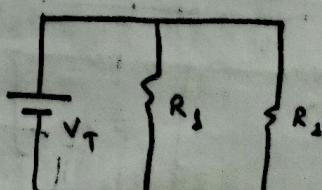

$$I_0 = I_T \times \frac{\text{Oppo. Resistance}}{\text{Total Resistance}}$$

Voltage Division Rule :-

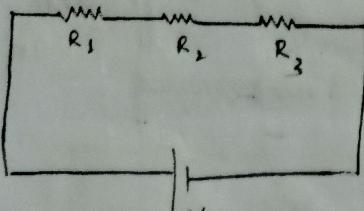Applicable for series circuits as in parallel circuits the voltage across resistors remain same / constant.
'n' no. of resistors can be taken - No limit.




$$V_s = I R_1 \quad \text{--- (1)}$$

$$I = \frac{V_t}{R_{\text{TOTAL}}} = \frac{V_t}{R_1 + R_2 + R_3} \quad \text{--- (2)}$$

From (1) and (2),

$$V_s = \frac{V_t}{R_1 + R_2 + R_3} \times R_1 = V \times \frac{R_1}{R_1 + R_2 + R_3}$$



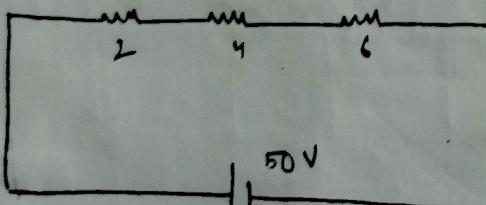
$$V_2 = V \times \frac{R_2}{R_1 + R_2 + R_3}; \quad V_3 = V \times \frac{R_3}{R_{\text{TOTAL}}}$$






$$V_2 = 50 \times \frac{2}{5} = \frac{50}{5} = 8.33V$$

$$V_6 = 50 \times \frac{3}{5} = \frac{50}{5} = 16.66V$$

$$V_6 = 50 \times \frac{3}{5} = 25V$$

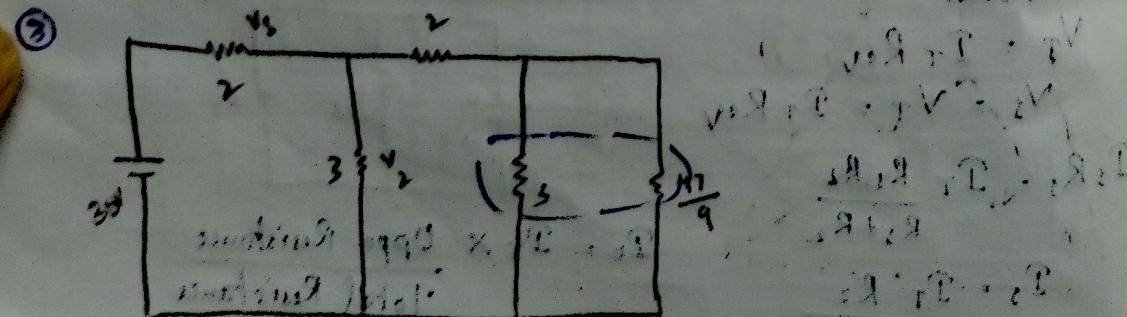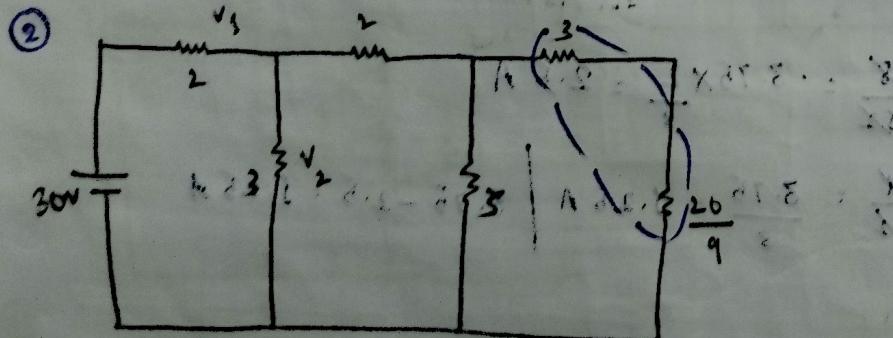
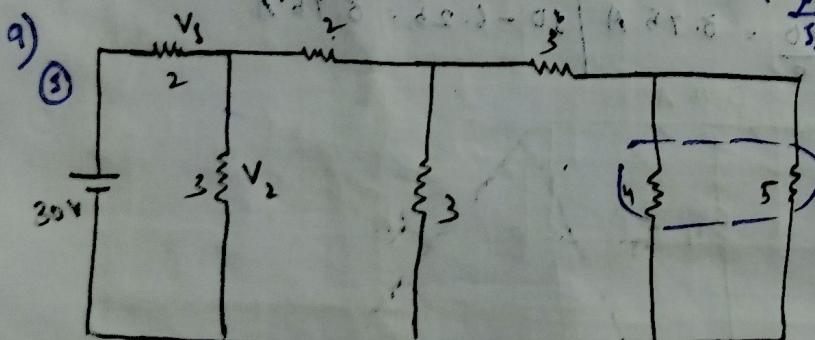


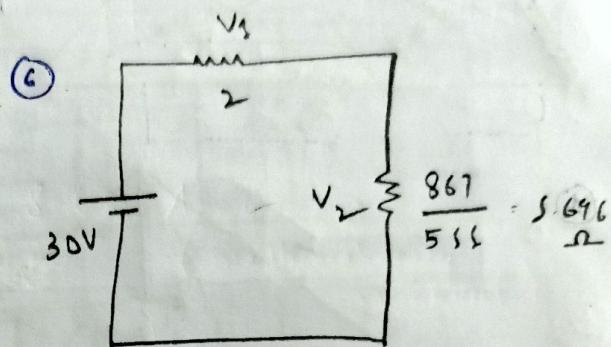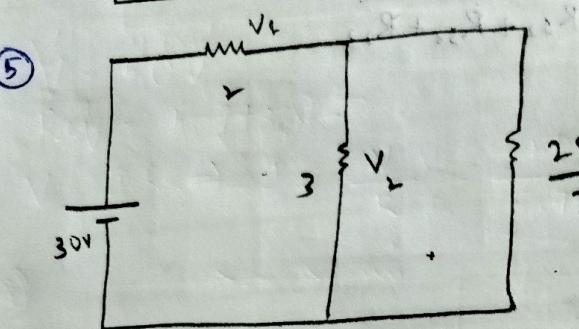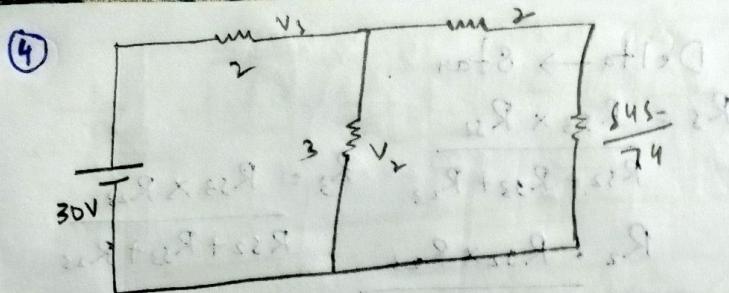

$$V_1 = 30 \times \frac{2}{3.696} = 16.233 \text{ V}$$


$$V_2 = 30 \times \frac{1.5696}{3.696} = 13.766 \text{ V}$$

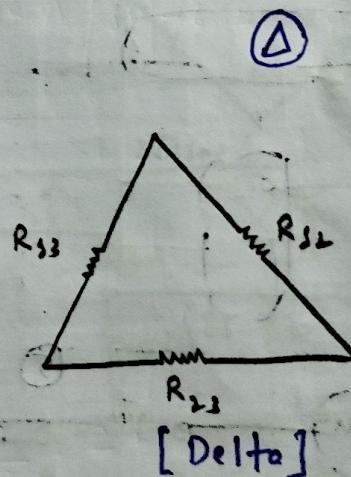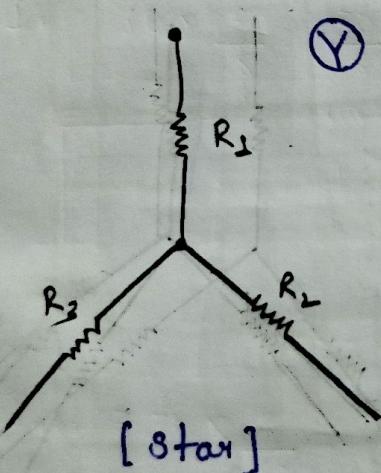Star-Delta and Delta to Star Transformation :-




Star \rightarrow Delta
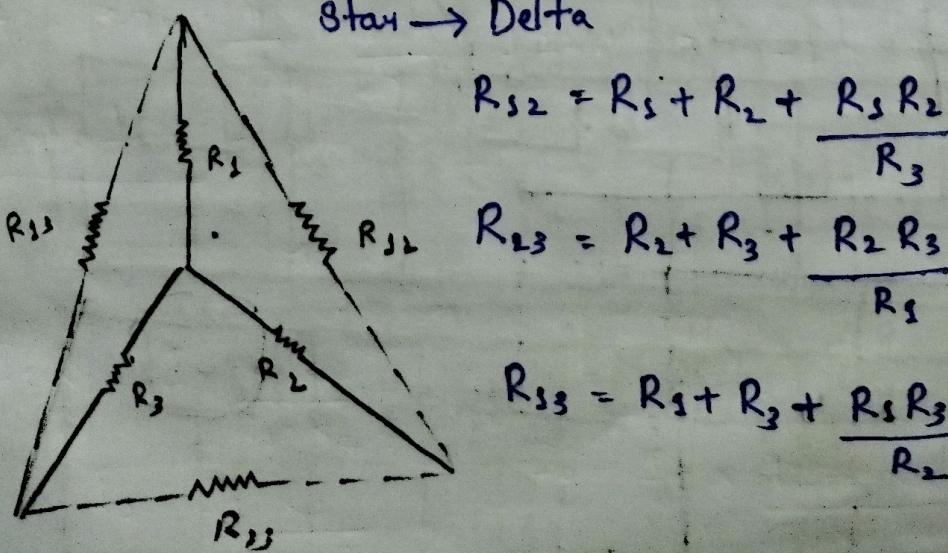
$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$


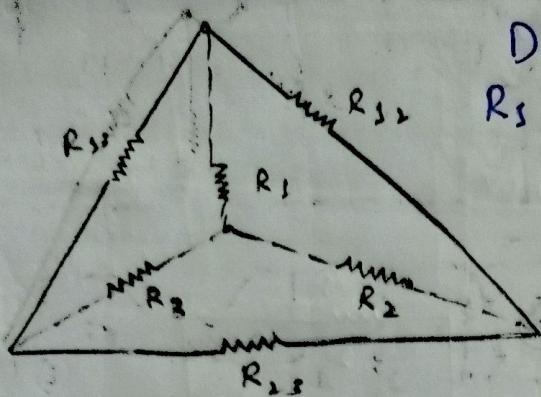
$$R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$




Delta \rightarrow Star

$$R_s = \frac{R_{s3} \times R_{s2}}{R_{s2} + R_{s3} + R_{23}}$$

$$R_3 = \frac{R_{s3} \times R_{23}}{R_{s2} + R_{s3} + R_{23}}$$

$$R_2 = \frac{R_{s2} \times R_{23}}{R_{s2} + R_{s3} + R_{23}}$$


①

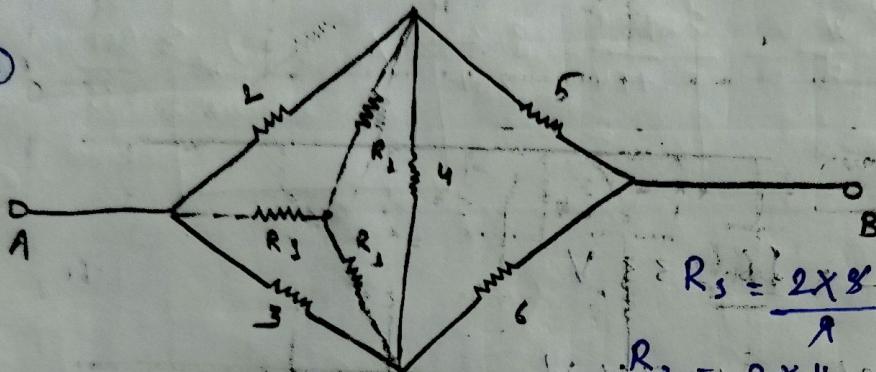

$$R_s = \frac{2 \times 8}{9} = \frac{2}{\frac{9}{3}} = 0.666$$


$$R_2 = \frac{2 \times 4}{9} = \frac{8}{9} \approx 0.888$$

②

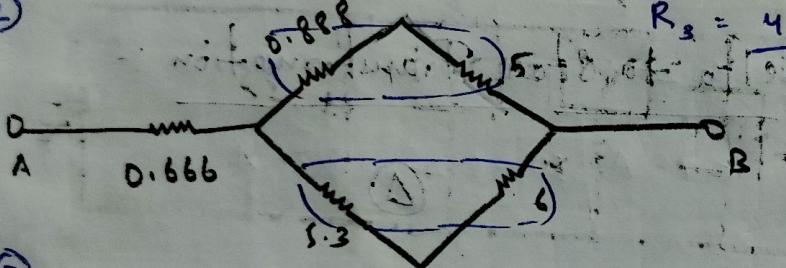


$$R_s = \frac{4 \times 8}{9} = \frac{4}{\frac{9}{3}} = 3.3$$


③

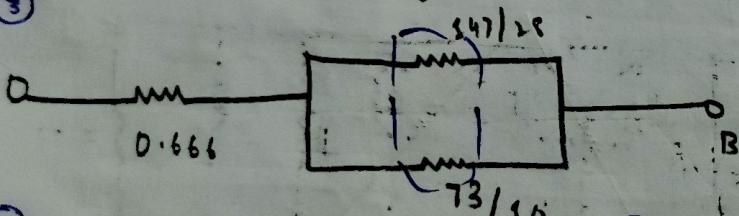


④

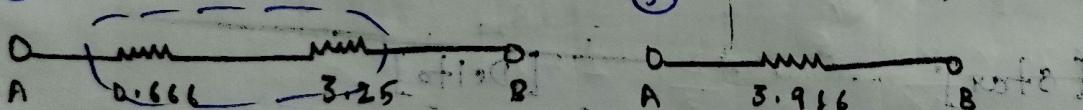


⑤







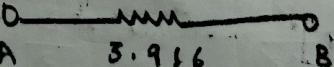









⑥







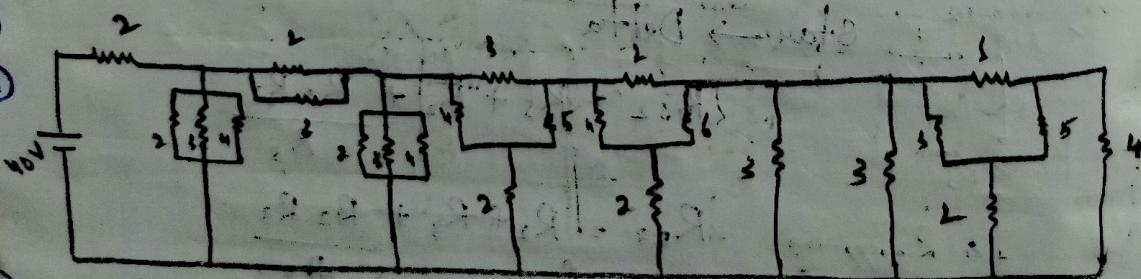


⑦

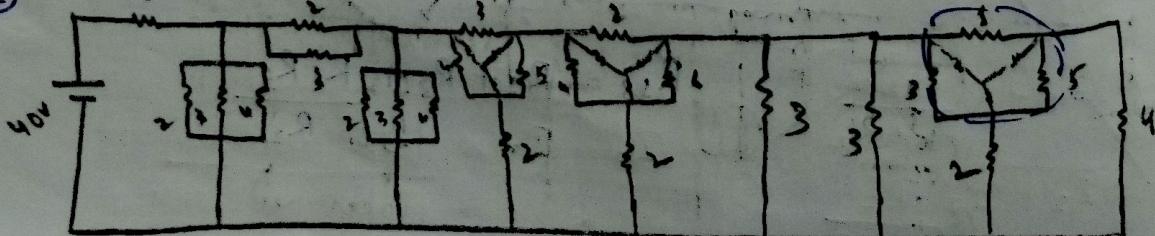


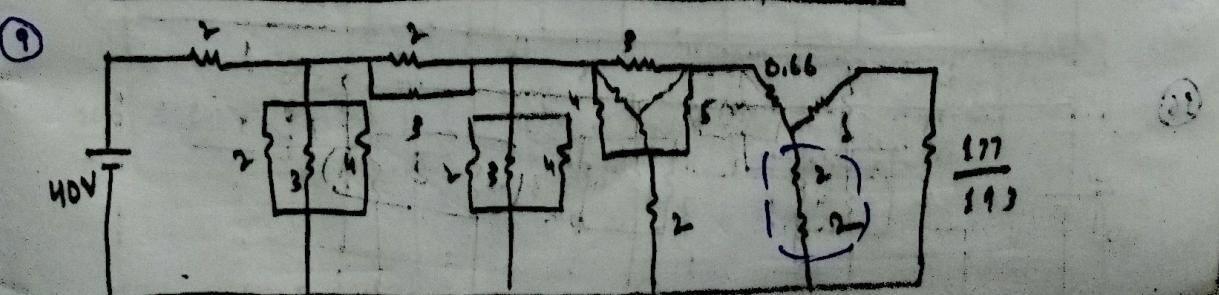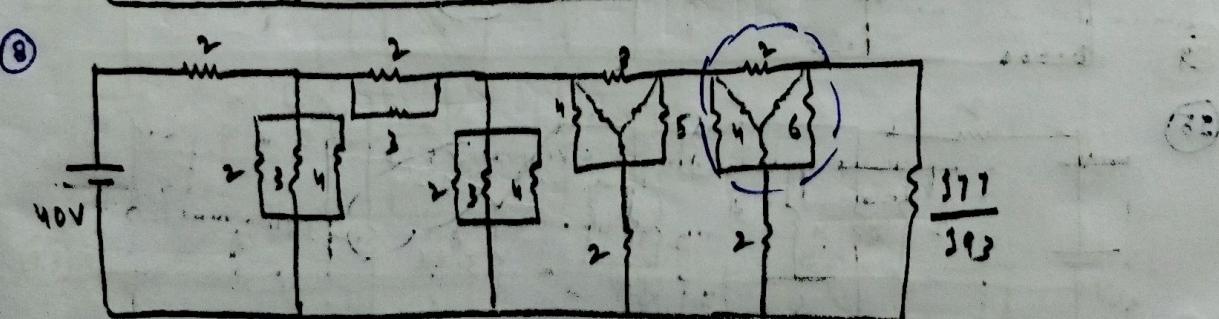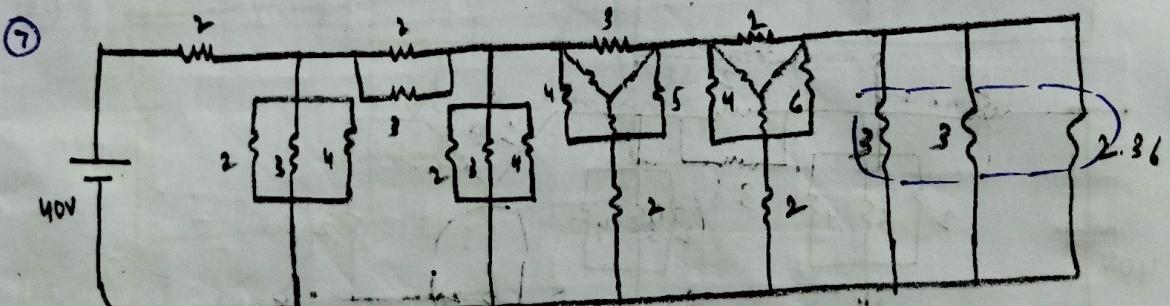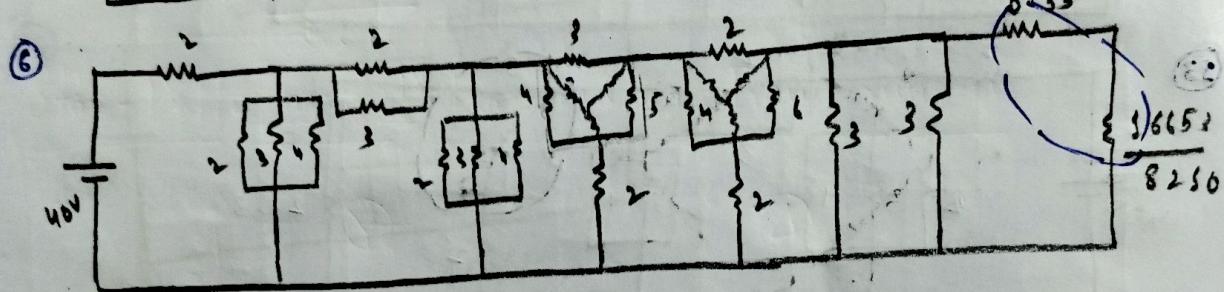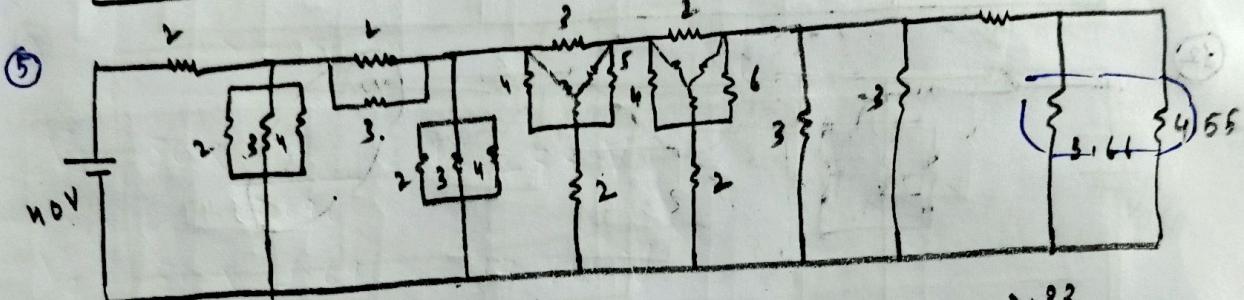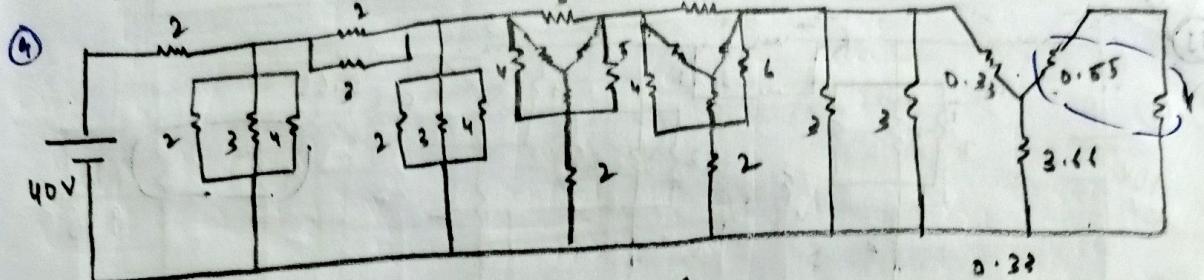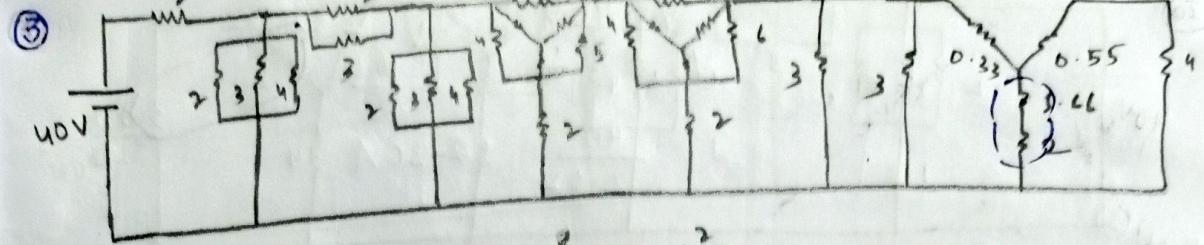

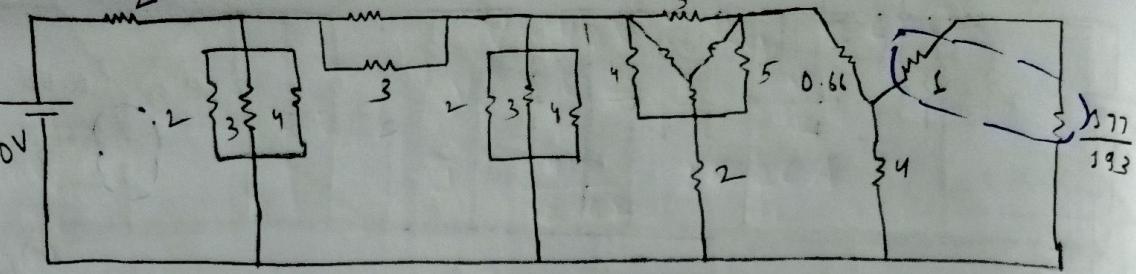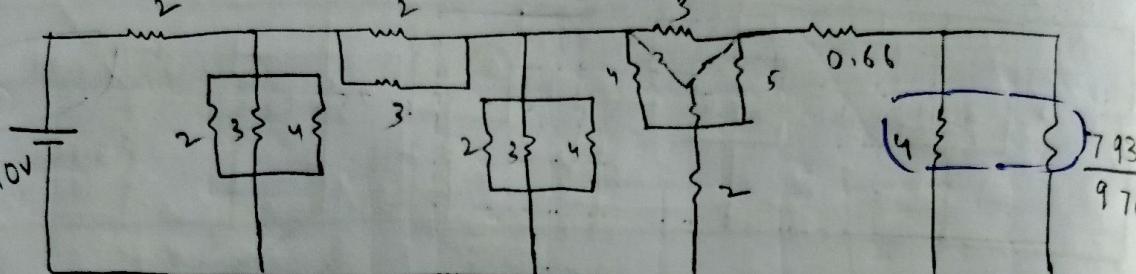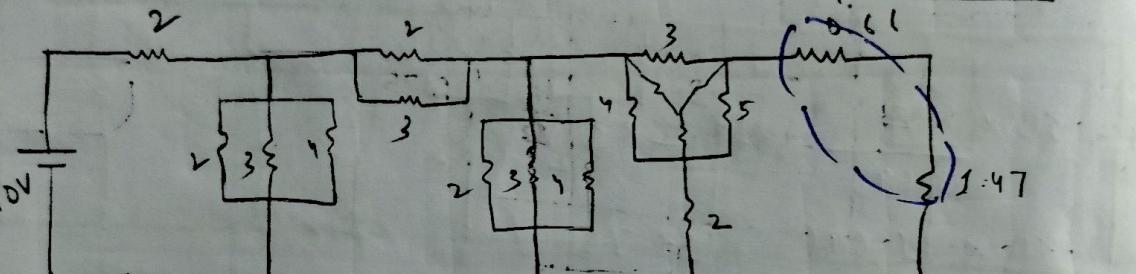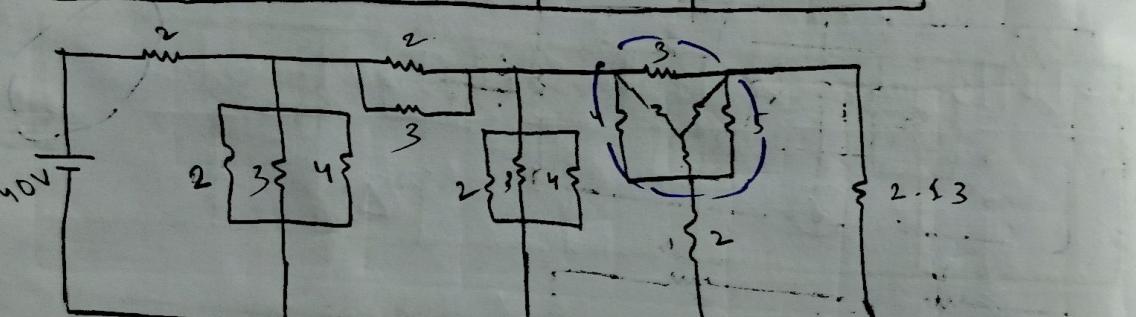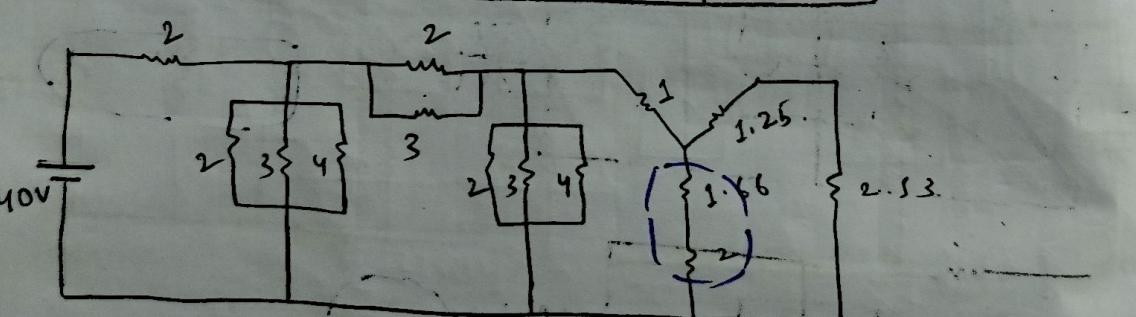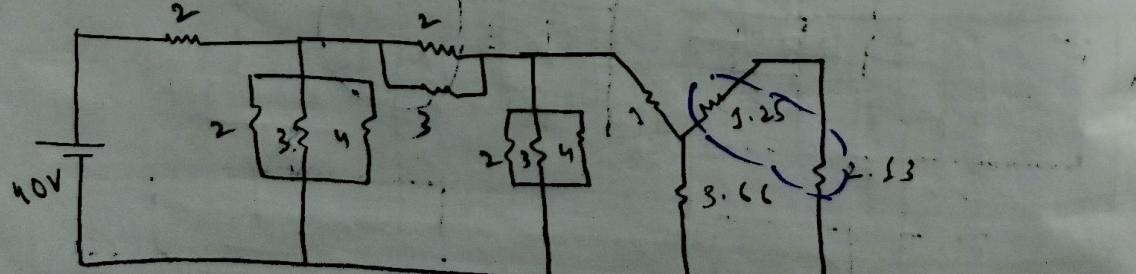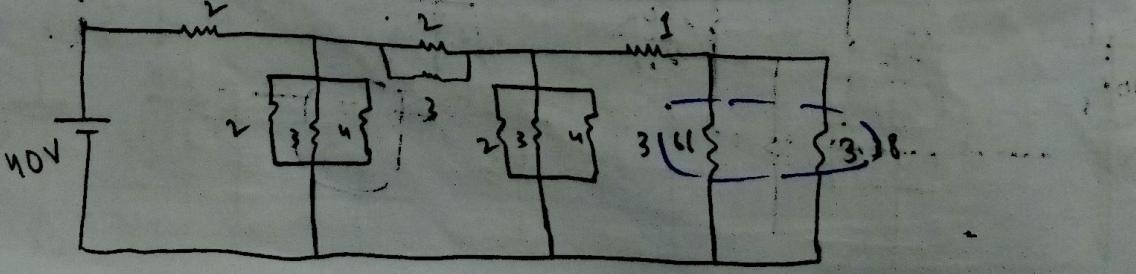- (10) 
- (11) 
- (12) 
- (13) 
- (14) 
- (15) 
- (16) 

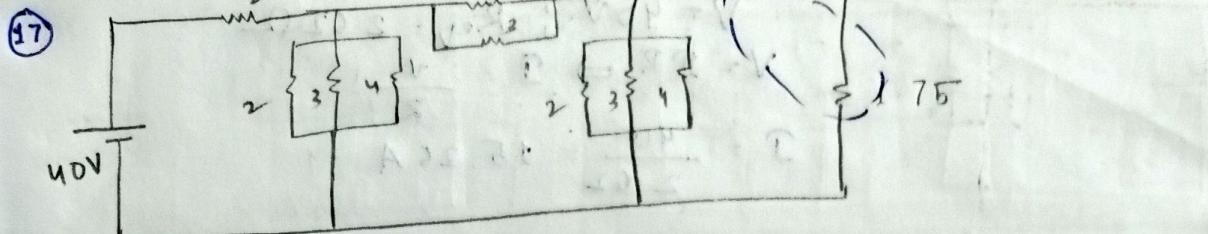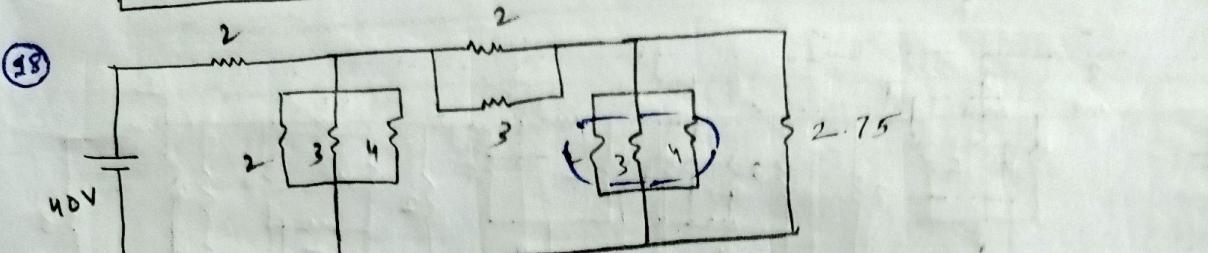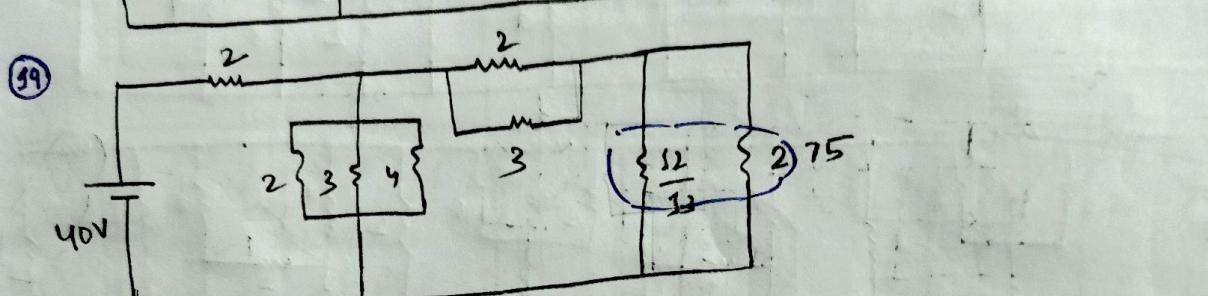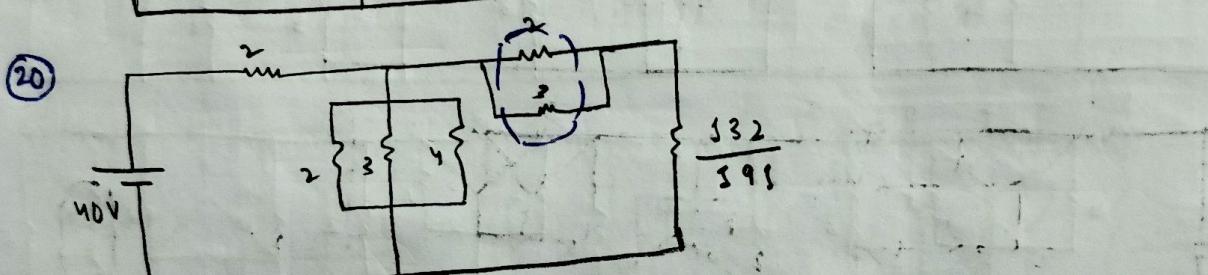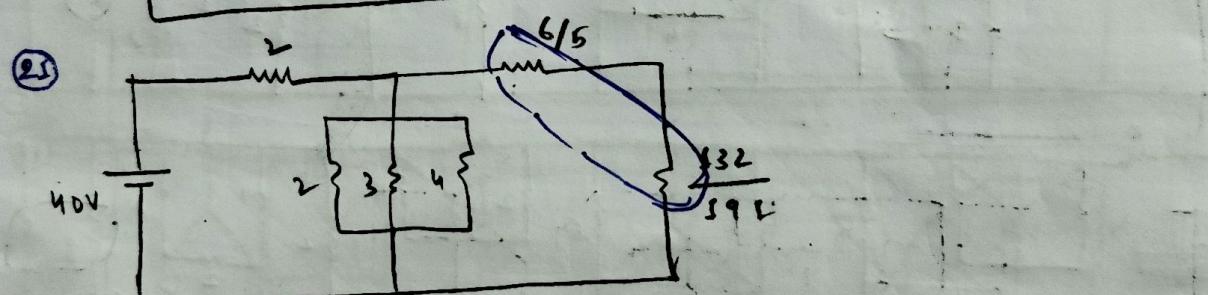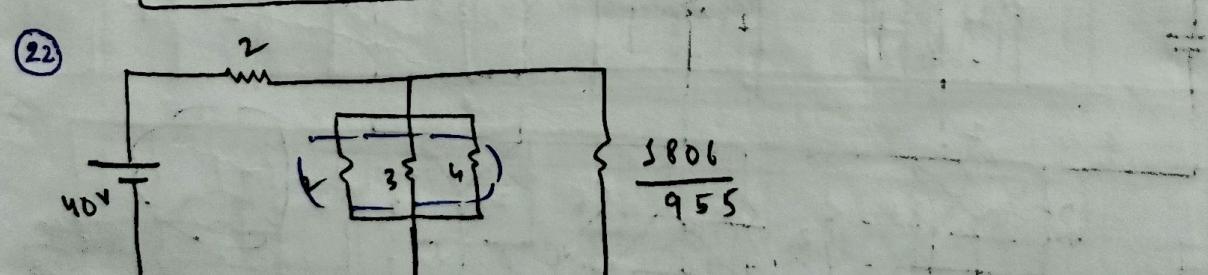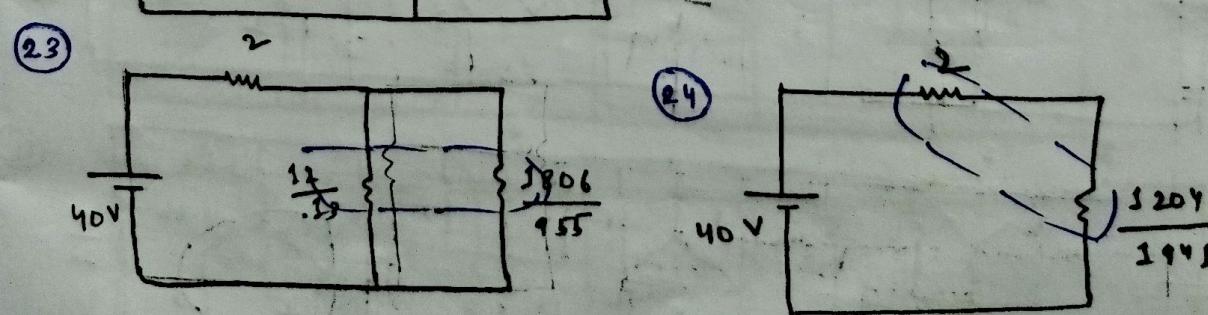- (17) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A 75 ohm load is connected across the rightmost resistor of the right branch and the common return path.
- (18) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A 2.75 ohm load is connected across the rightmost resistor of the right branch and the common return path.
- (19) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A 75 ohm load is connected across the rightmost resistor of the right branch and the common return path. The rightmost resistor of the right branch is circled in blue.
- (20) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A load of $\frac{532}{595}$ ohms is connected across the rightmost resistor of the right branch and the common return path. The rightmost resistor of the right branch is circled in blue.
- (21) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A load of $\frac{6}{5}$ ohms is connected across the rightmost resistor of the right branch and the common return path. The rightmost resistor of the right branch is circled in blue.
- (22) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A load of $\frac{5806}{955}$ ohms is connected across the rightmost resistor of the right branch and the common return path. The rightmost resistor of the right branch is circled in blue.
- (23) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A load of $\frac{5806}{955}$ ohms is connected across the rightmost resistor of the right branch and the common return path. The rightmost resistor of the right branch is circled in blue.
- (24) 
 A circuit diagram with a 40V DC voltage source at the bottom left. Two parallel branches are connected to the top wire. The left branch contains two resistors in series, labeled 2 and 3, with a total value of 4 ohms. The right branch contains two resistors in series, labeled 2 and 3, with a total value of 1 ohm. A load of $\frac{5204}{1941}$ ohms is connected across the rightmost resistor of the right branch and the common return path. The rightmost resistor of the right branch is circled in blue.

(2)

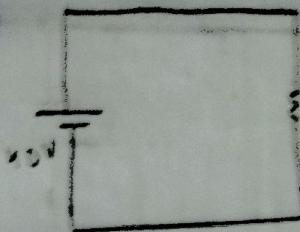


$$V = 40 \text{ V} ; R_{\text{eq}} = 2.62 \Omega$$

$$V = 22 \Rightarrow I = \frac{V}{R}$$


$$I = \frac{40}{2.62} = 15.26 \text{ A}$$

K.W.


(3)

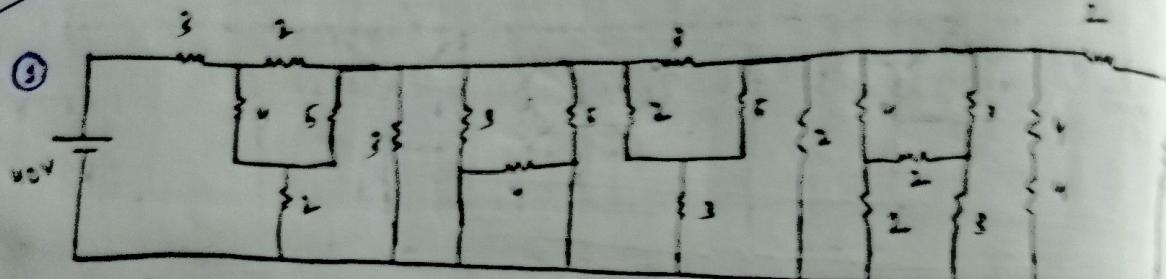


(2)

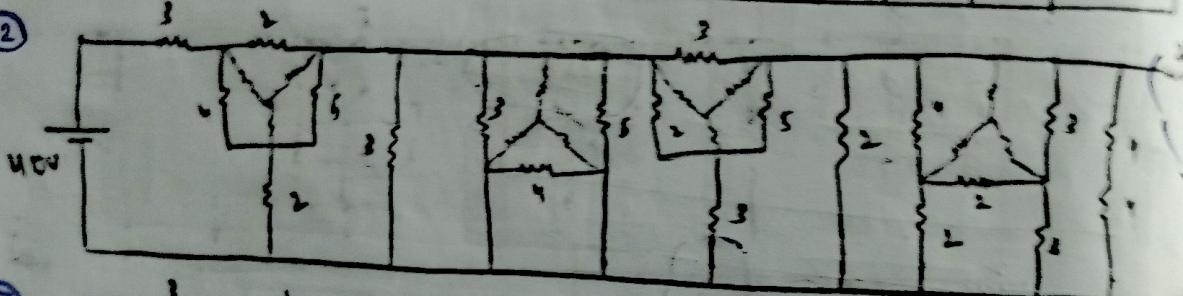



(3)







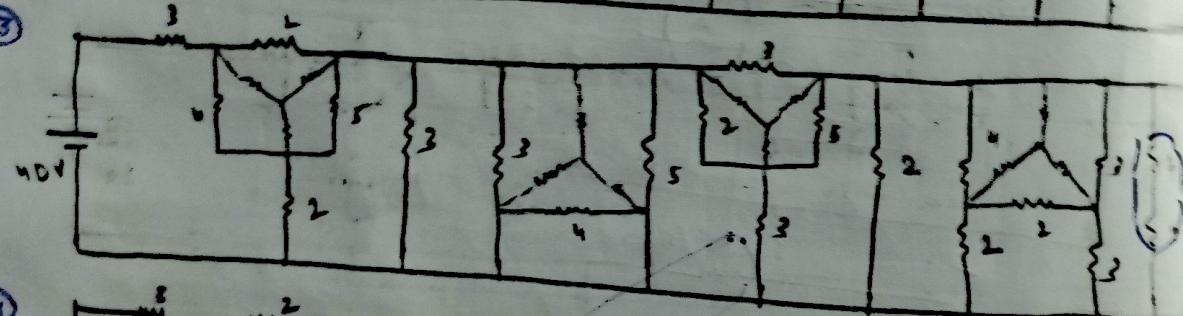


(4)

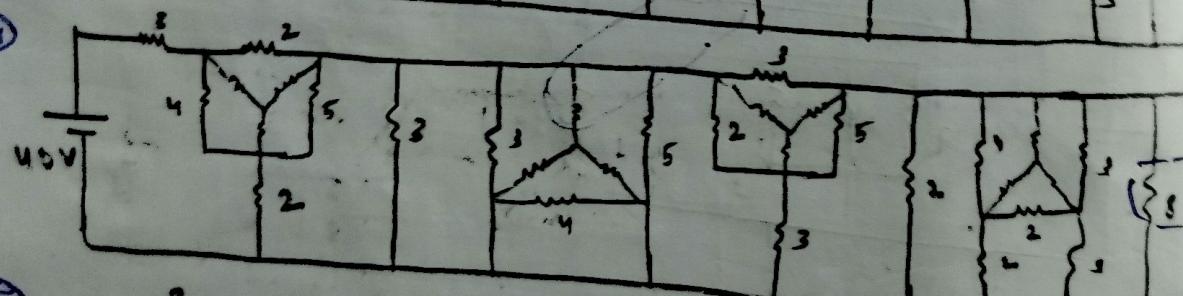


(5)

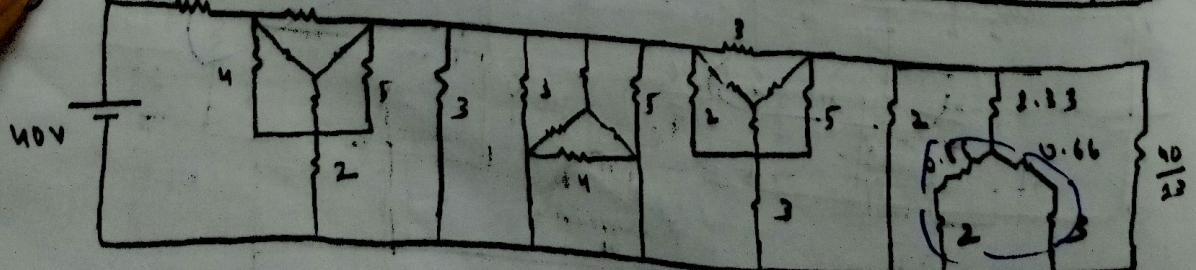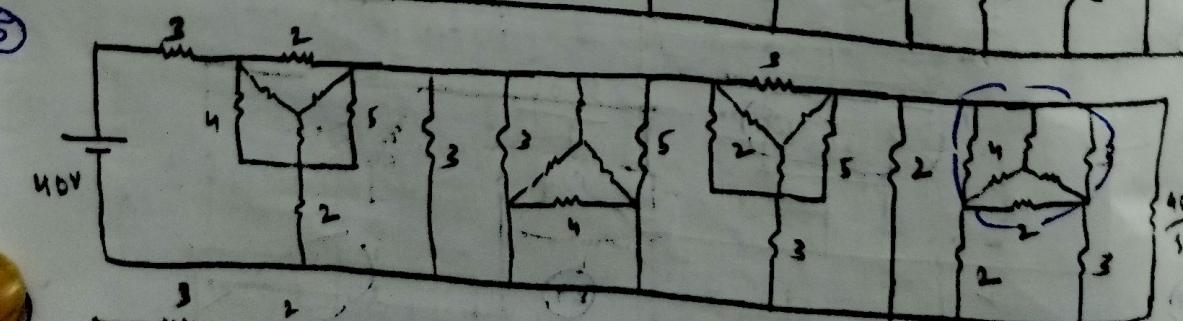


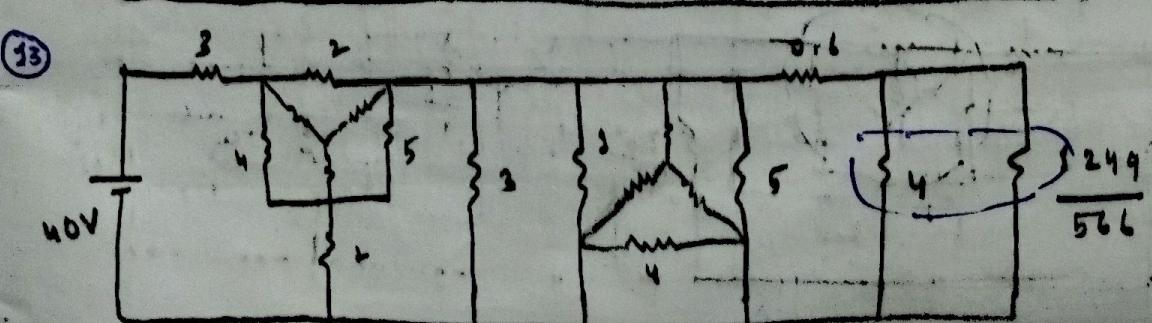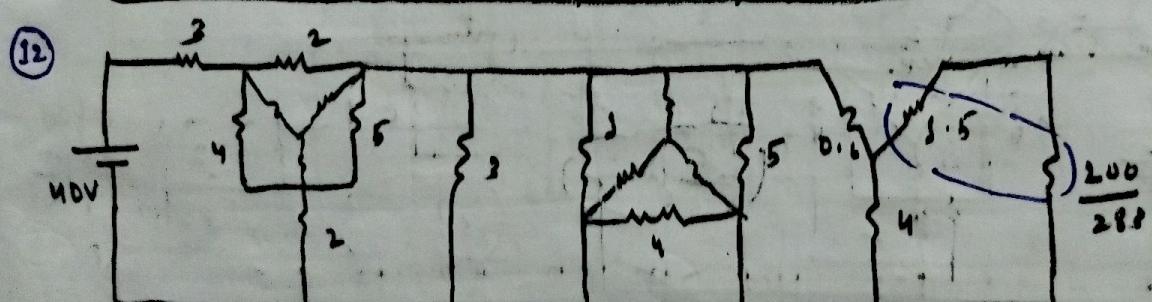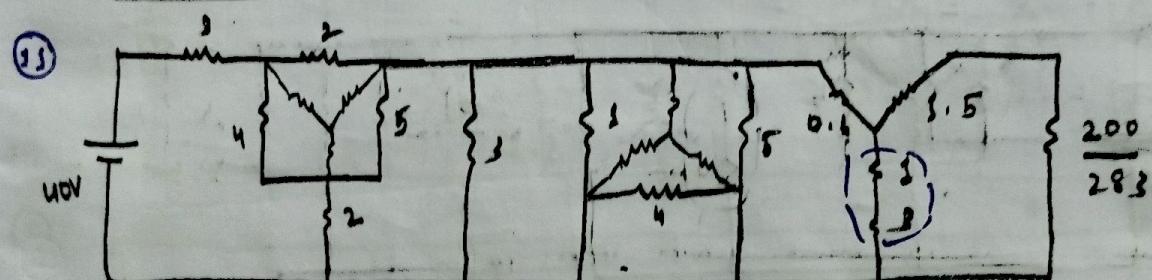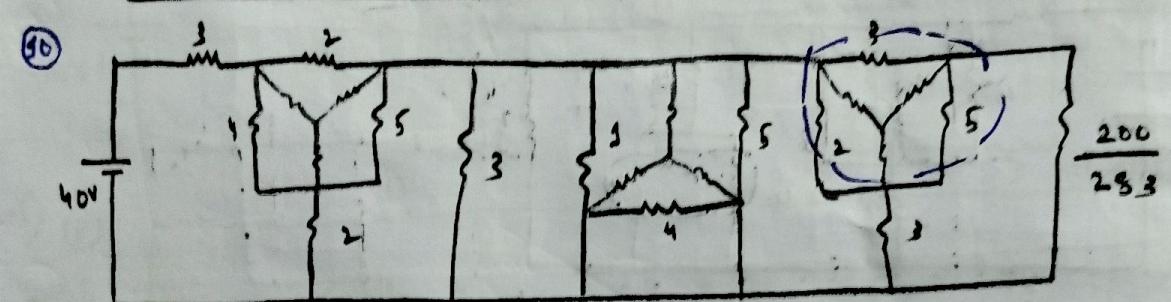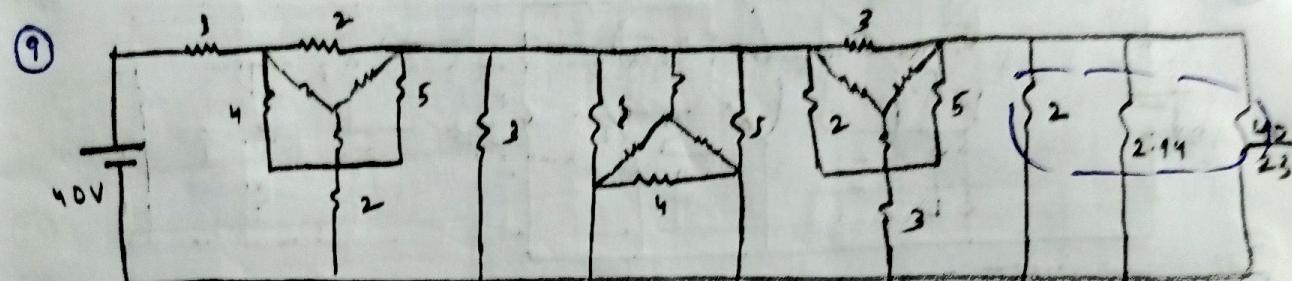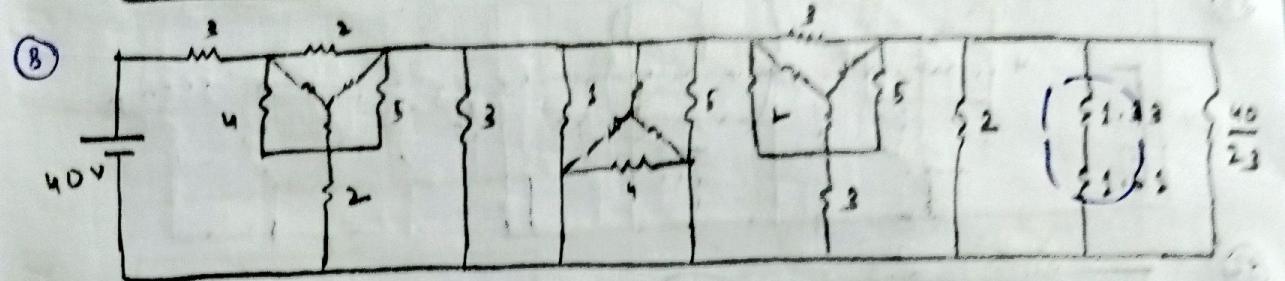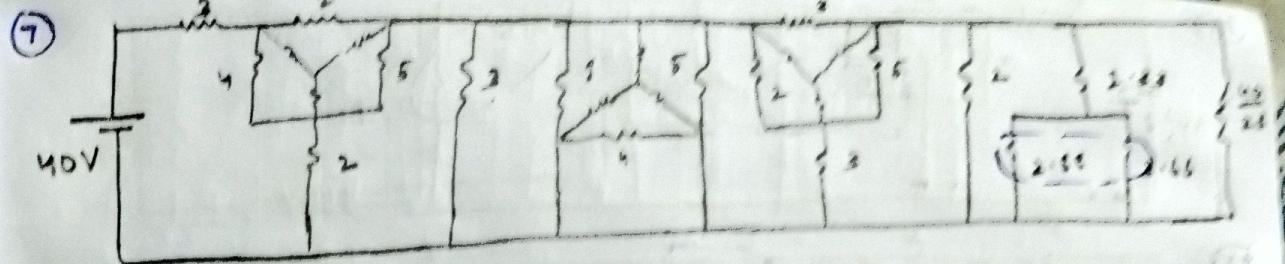


(34)

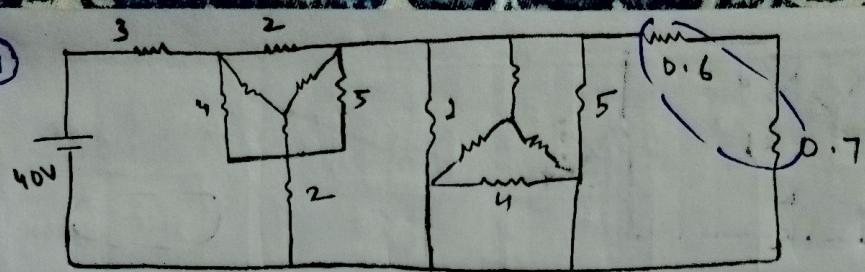


(35)

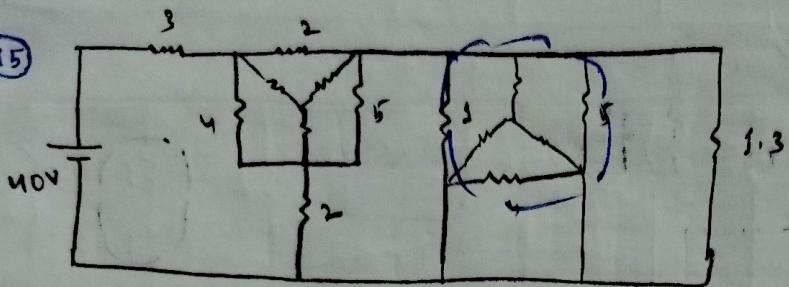


(36)

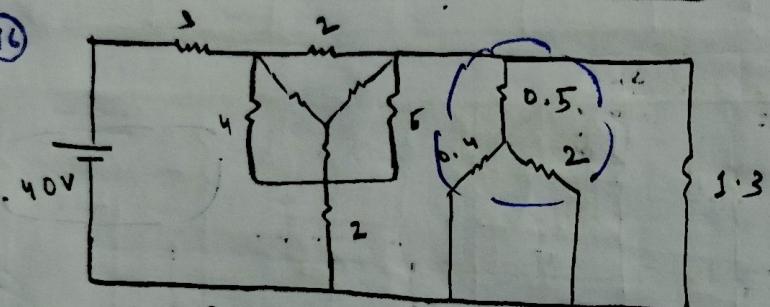



(37)



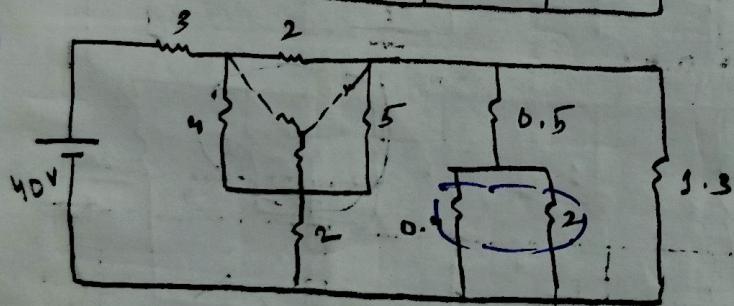


(38)

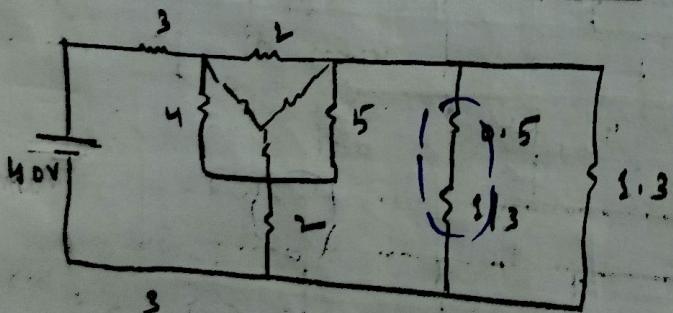

(39)




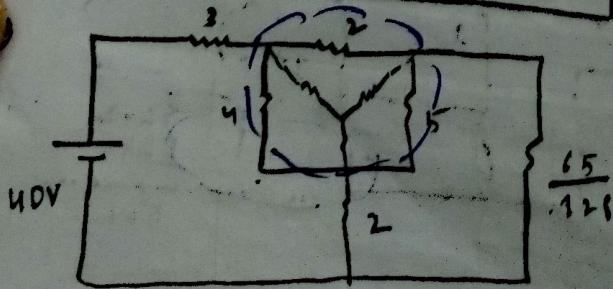
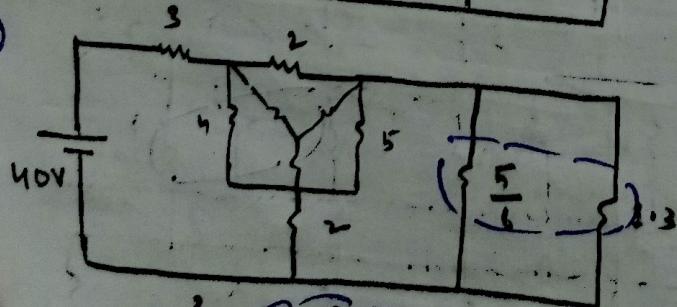






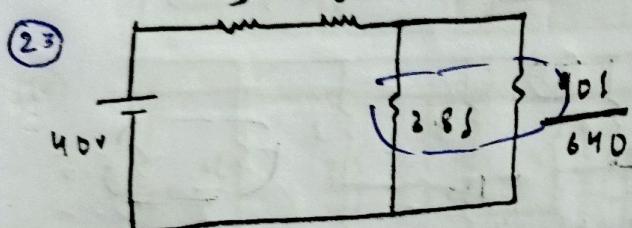
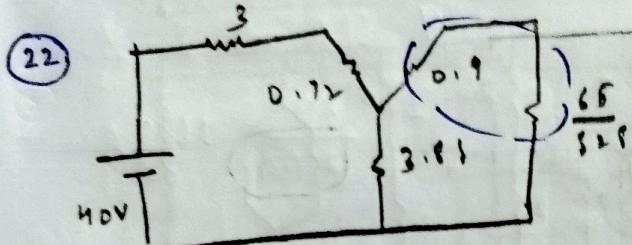
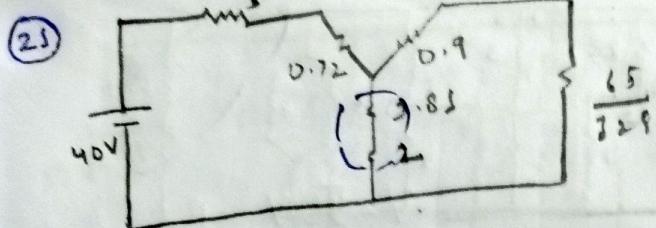









$$V = 40V ; R_{eq} = 4.69 \Omega$$

$$V = IR \Rightarrow I = \frac{V}{R}$$


$$I = \frac{40}{4.69} = 8.521$$

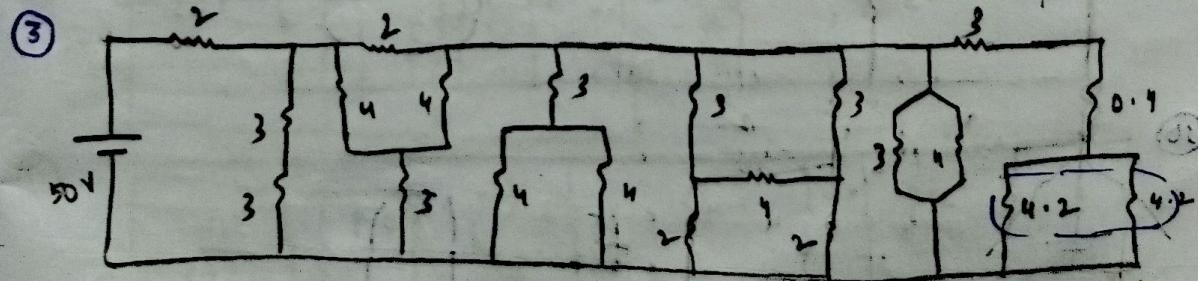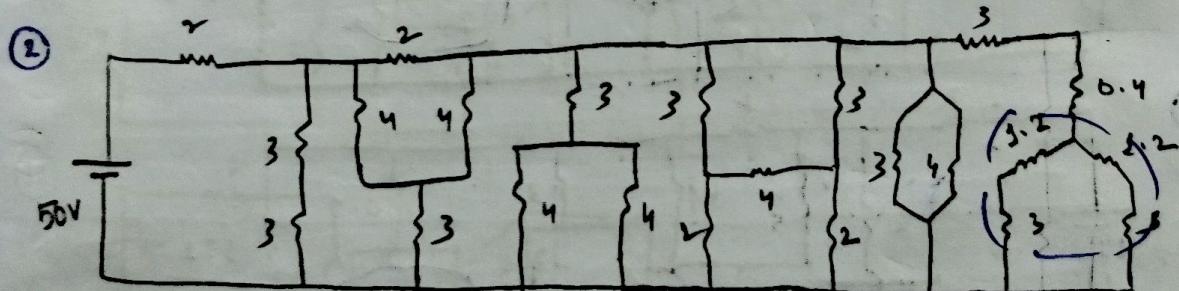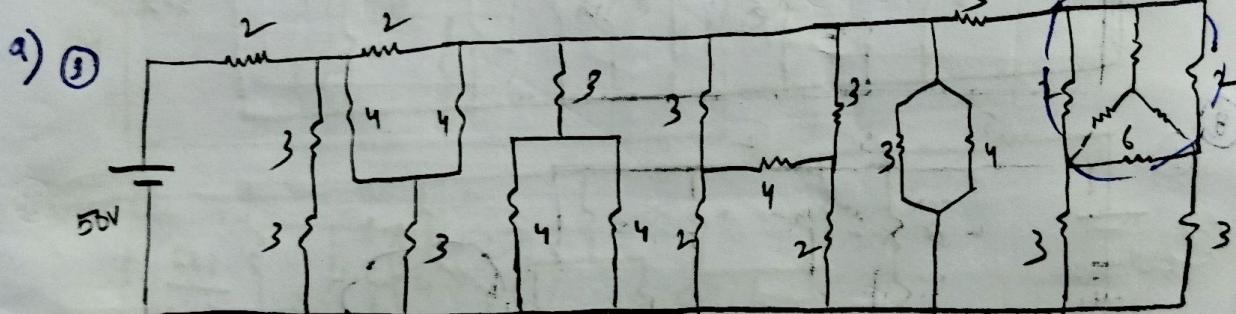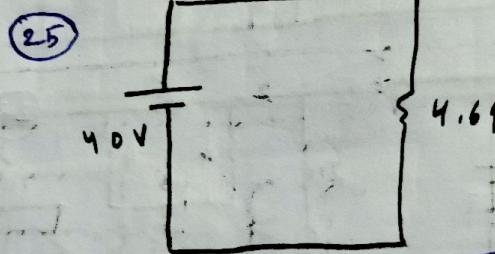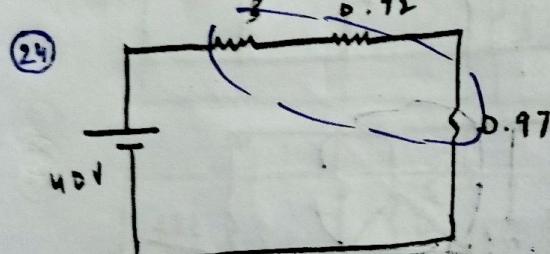

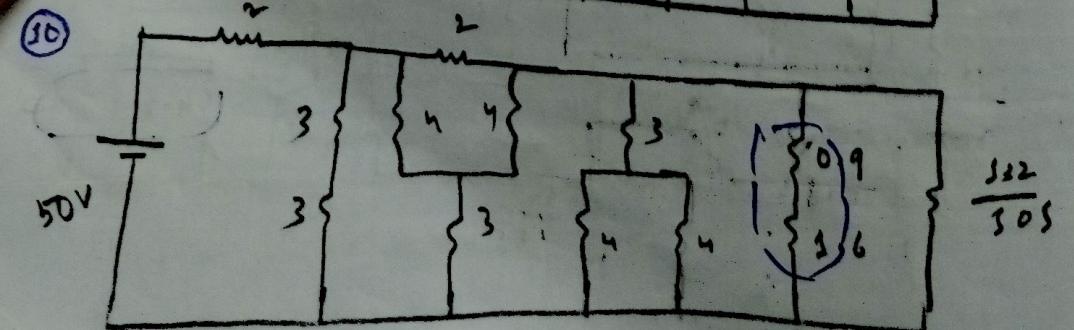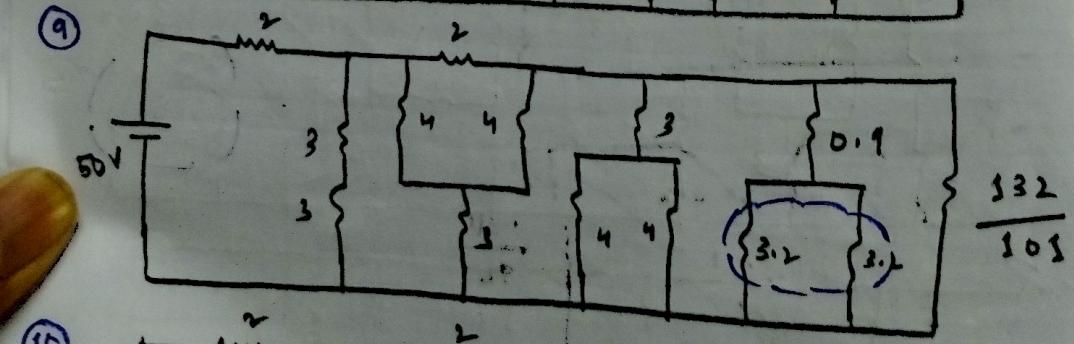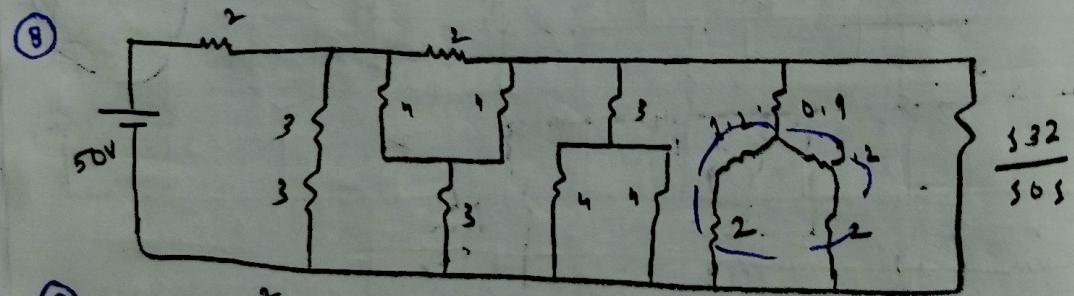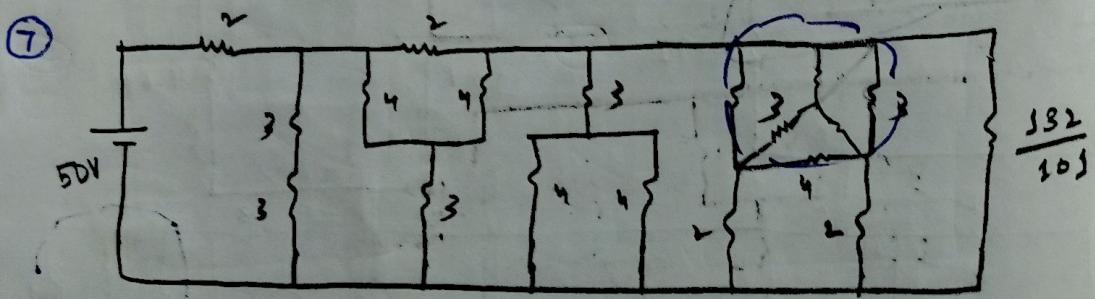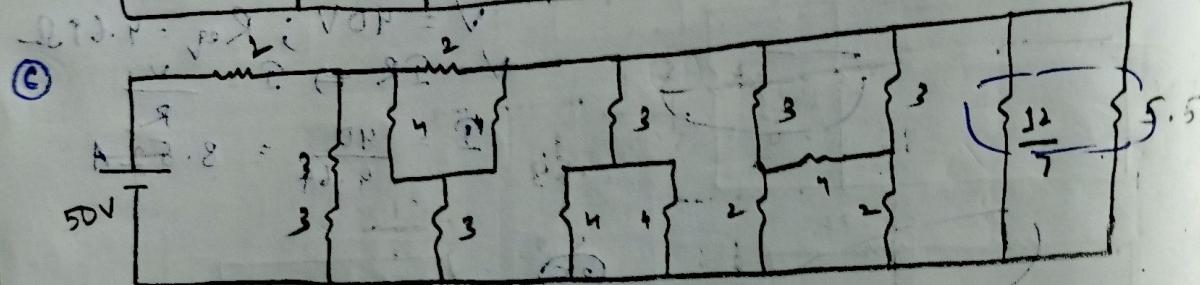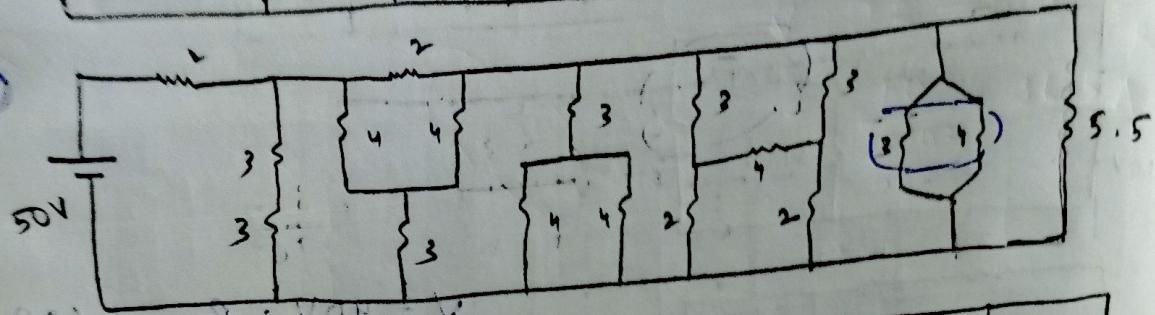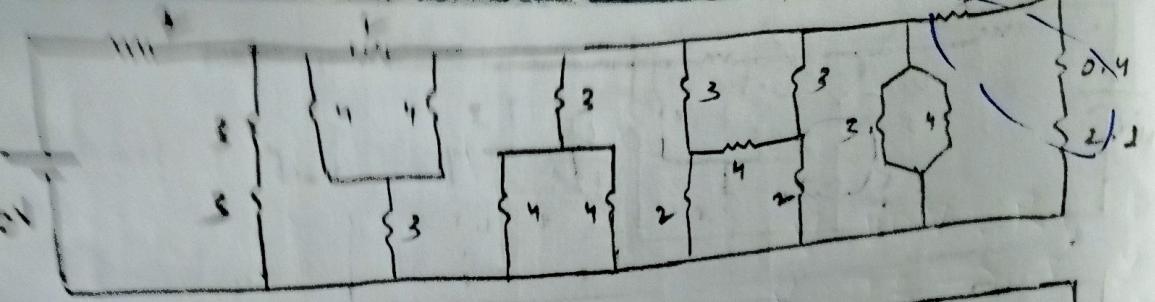

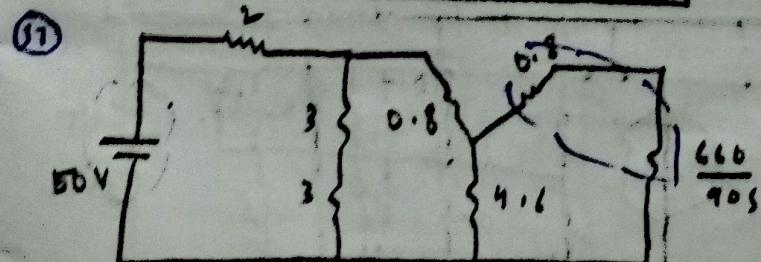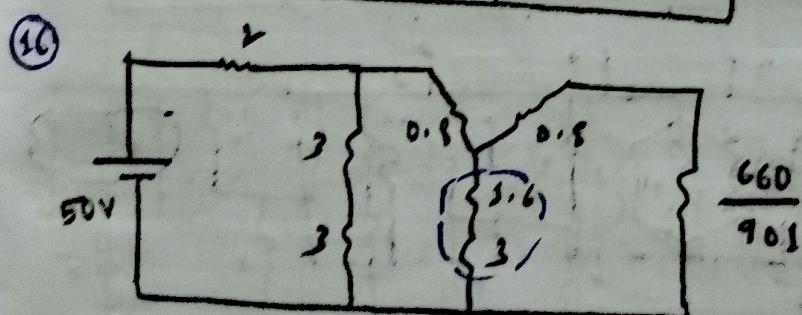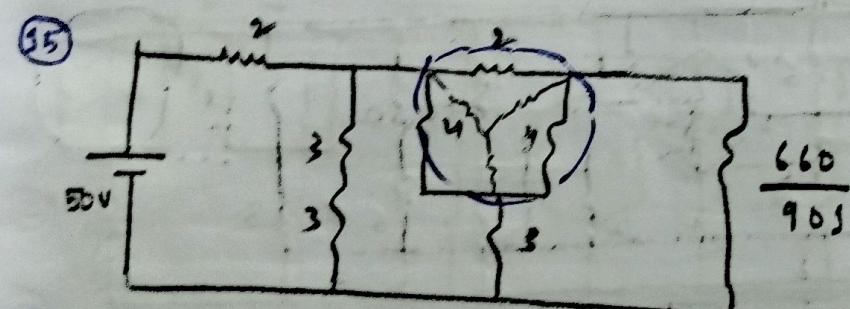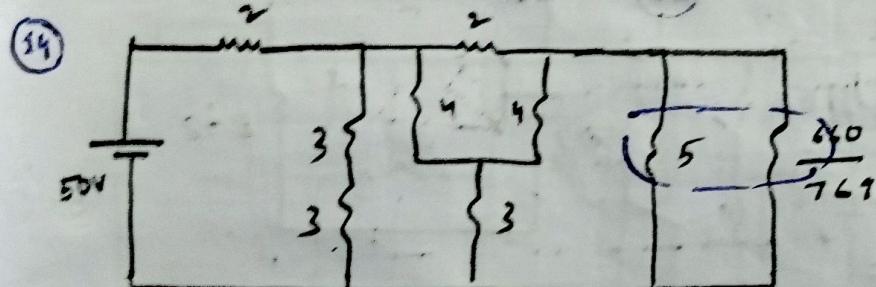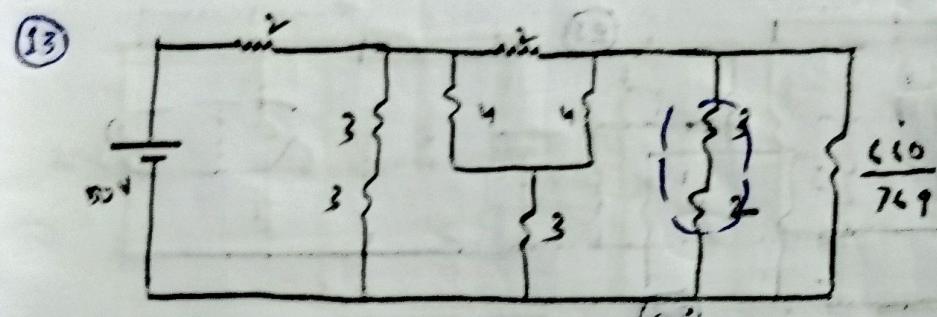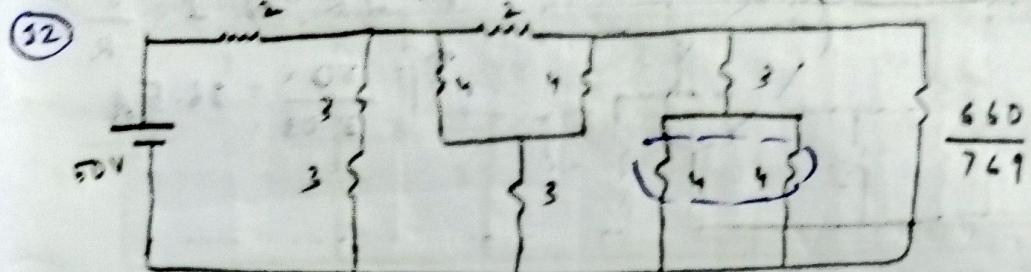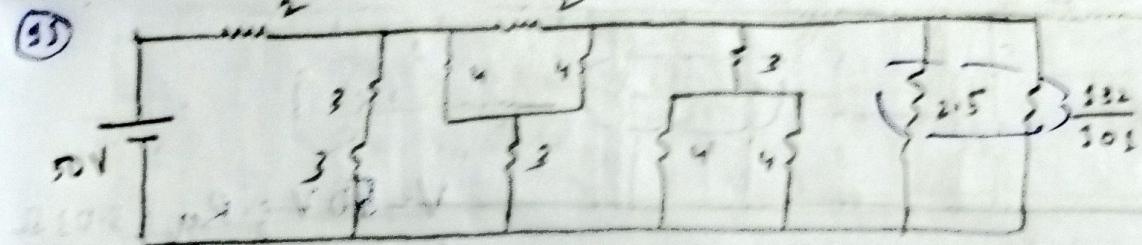

98

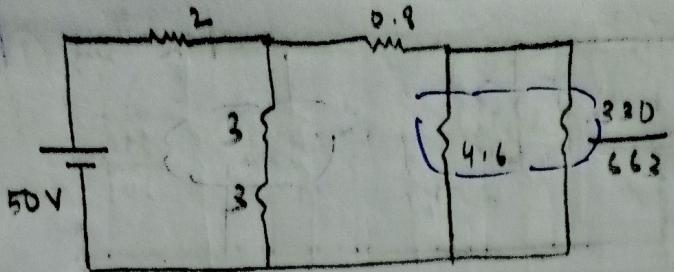


$$V = 50V; R_g = 3.03\Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{50}{3.03} = 16.5A$$


99

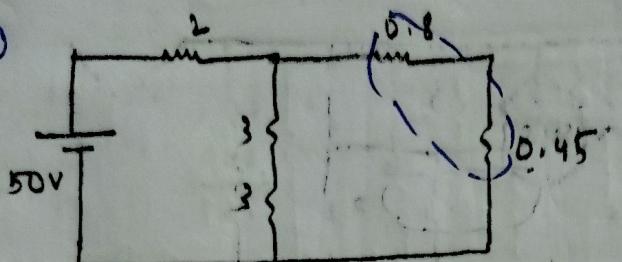


100

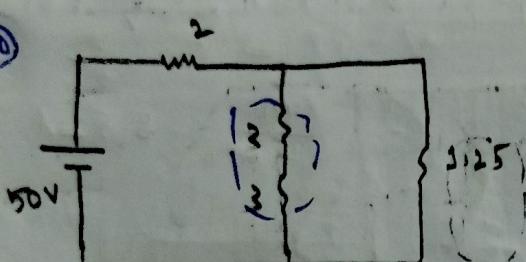


101

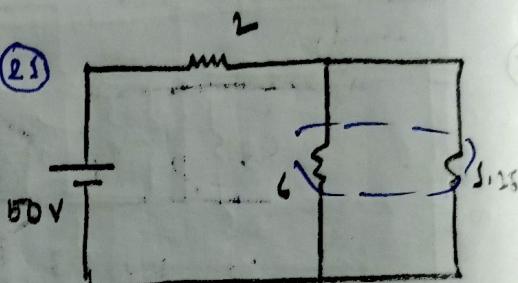


102

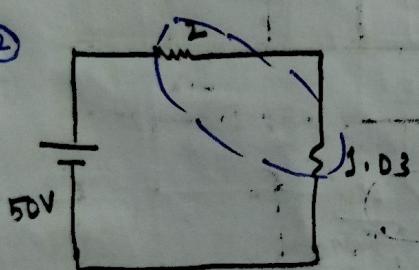


103

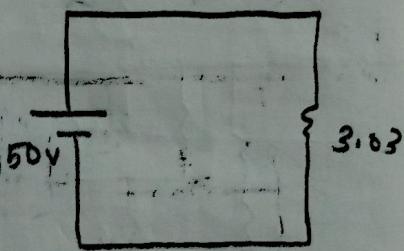


104







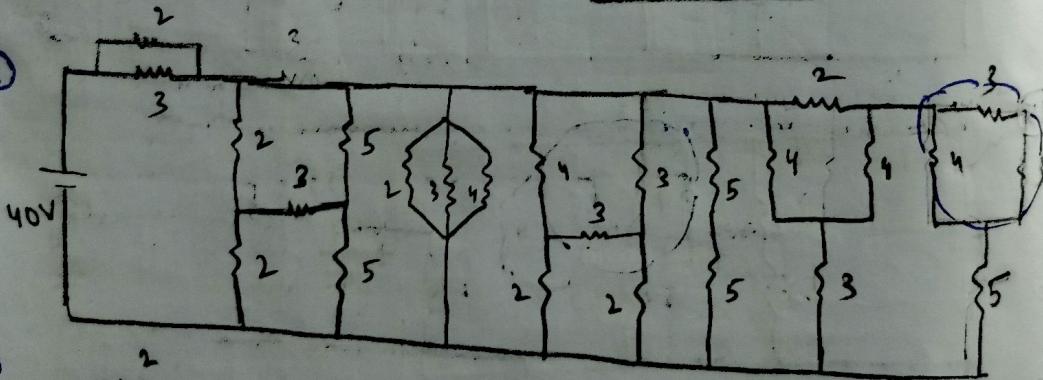








105

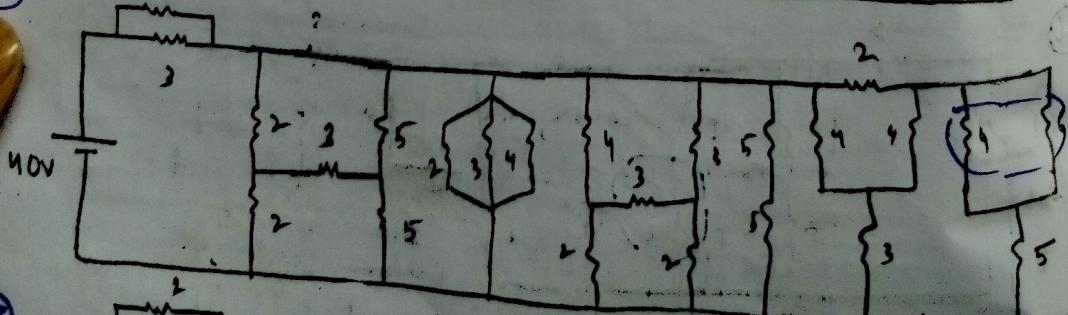


106

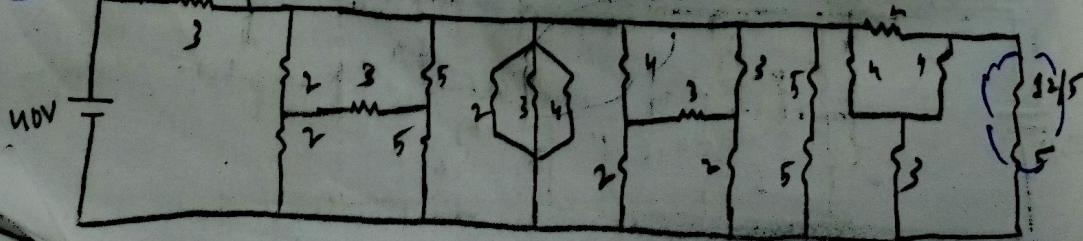

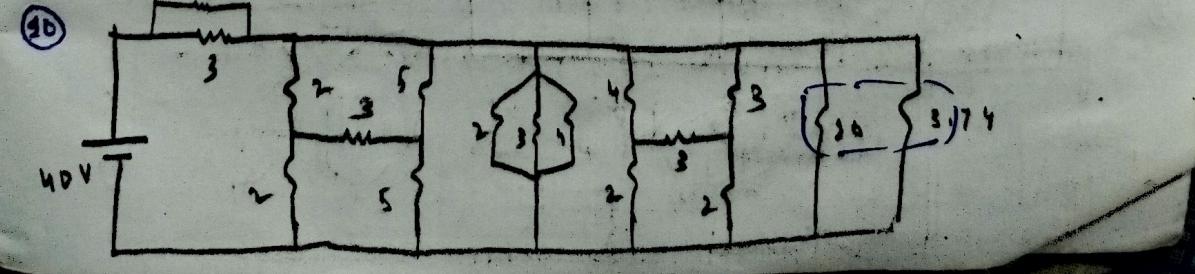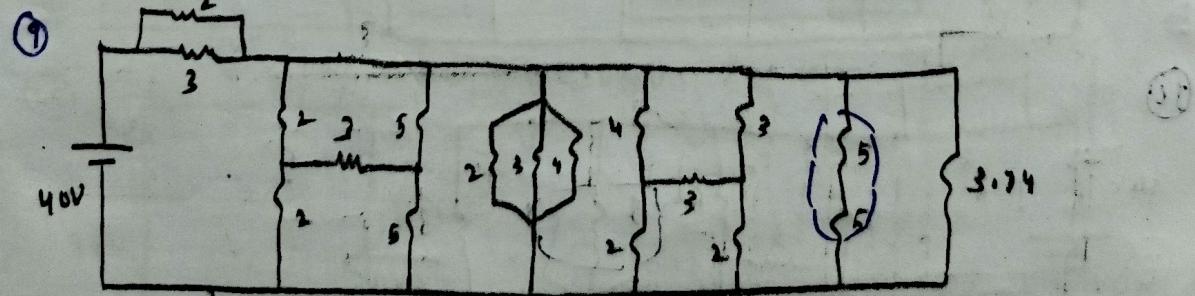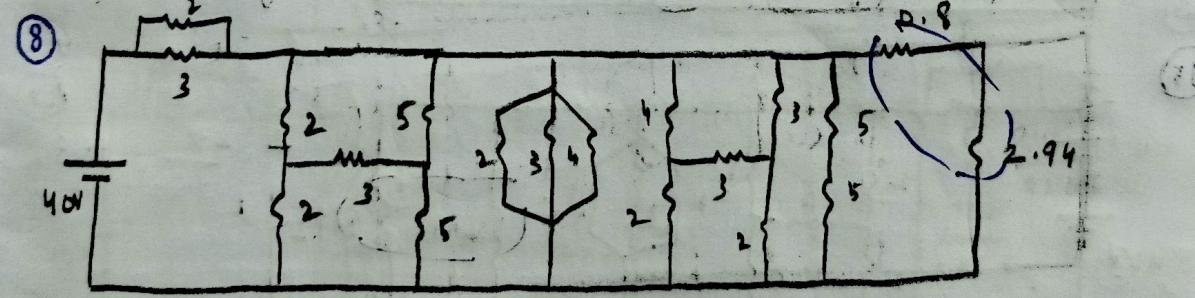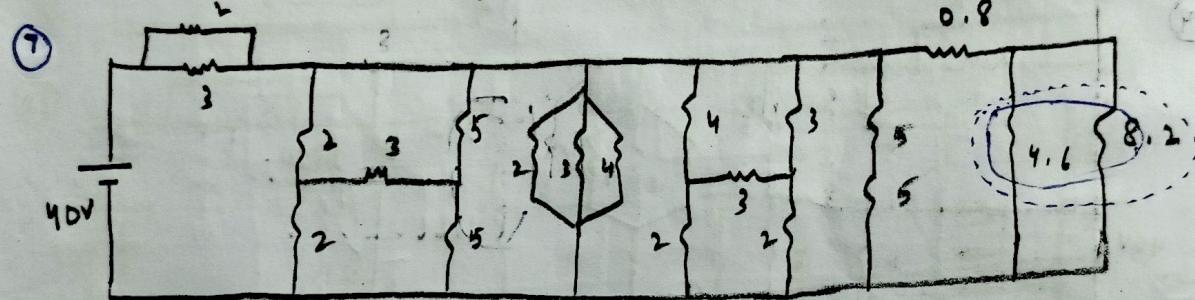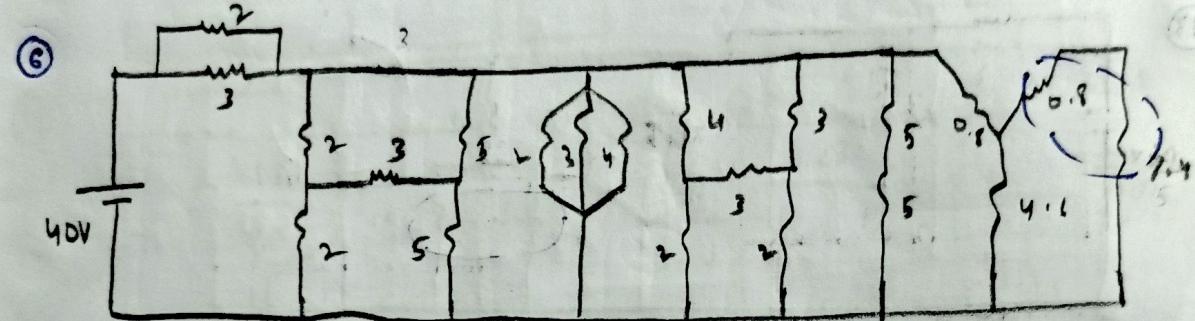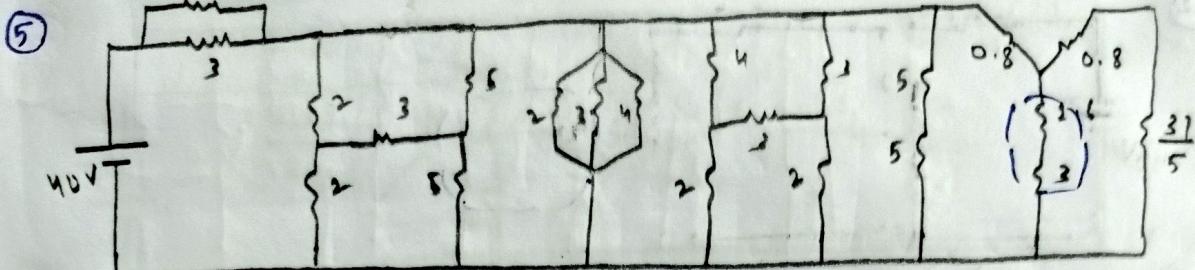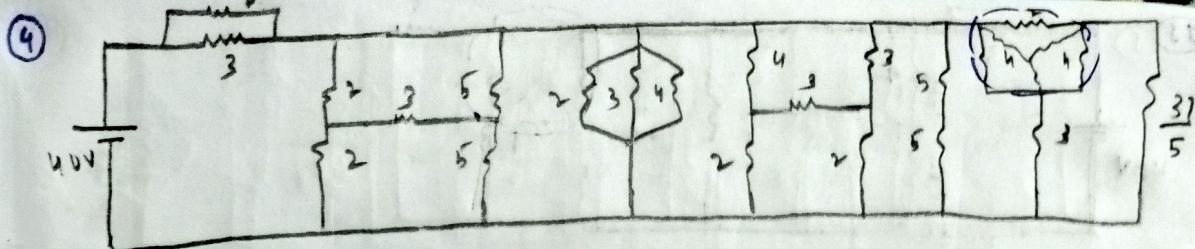


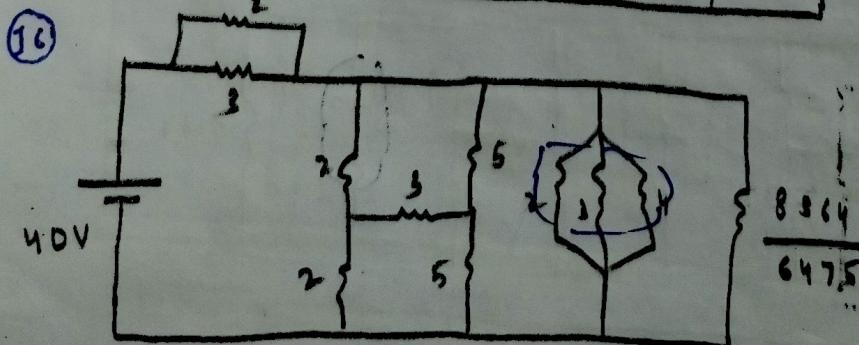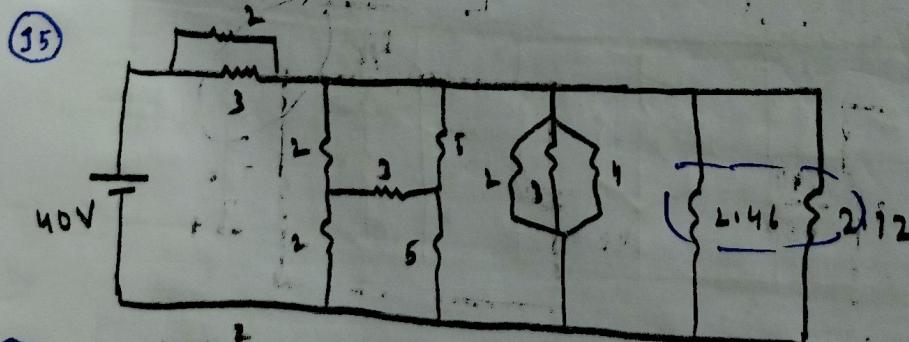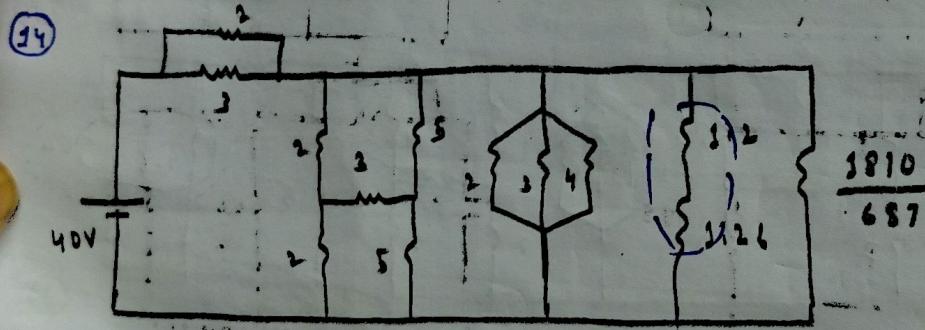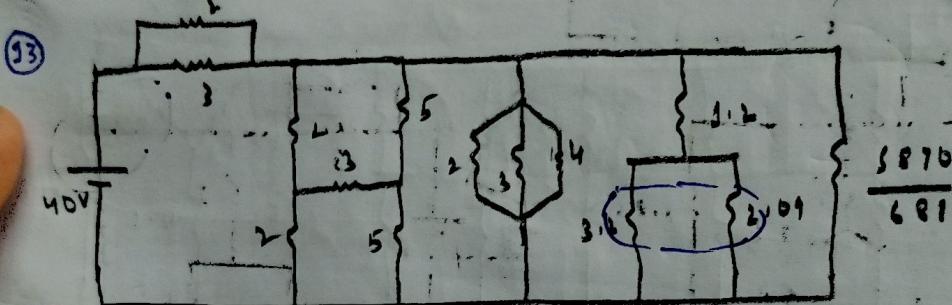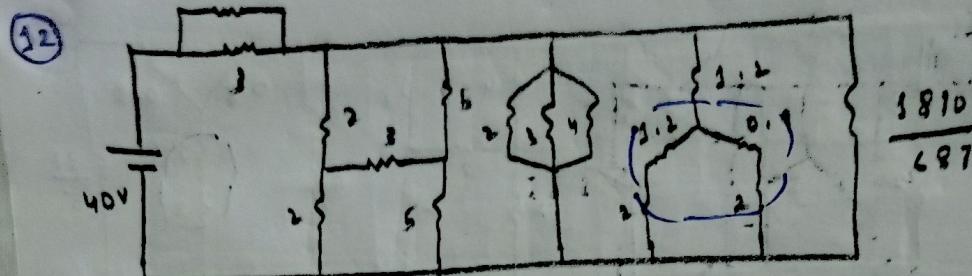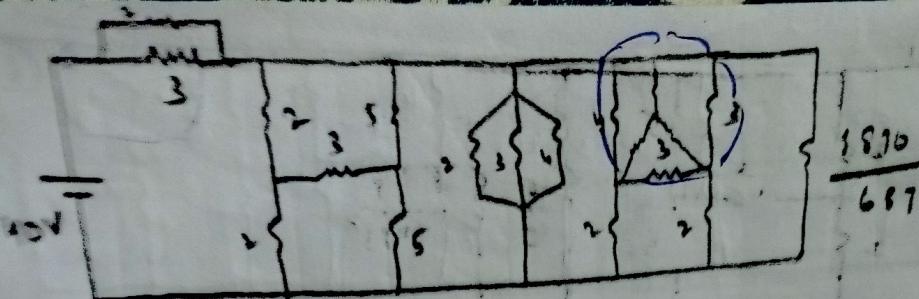


(17)

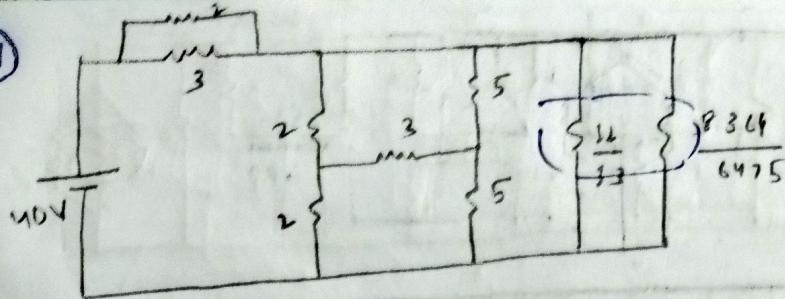


(18)

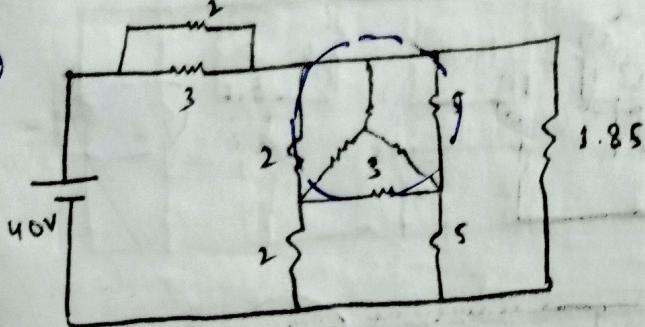


(19)

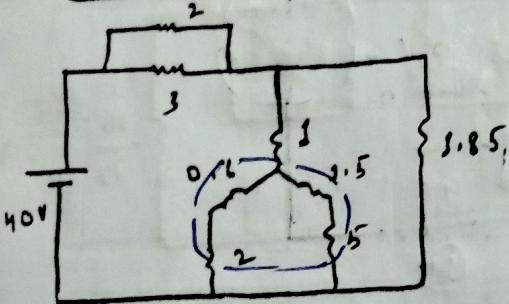


(20)

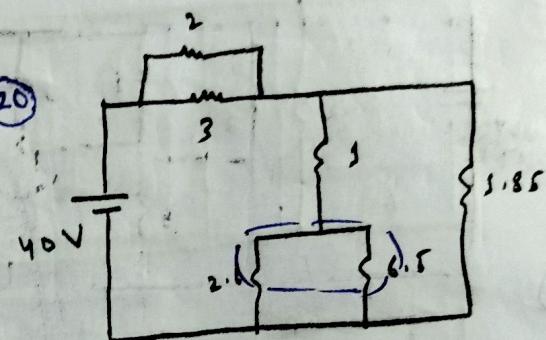


(21)

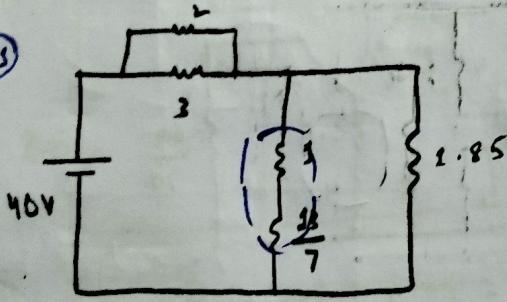


(22)

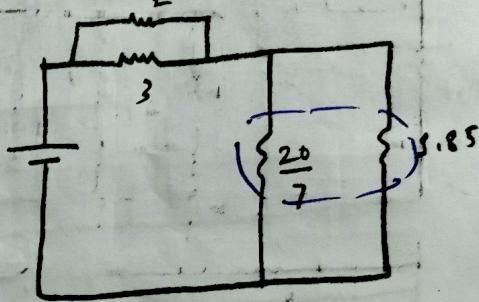


(23)

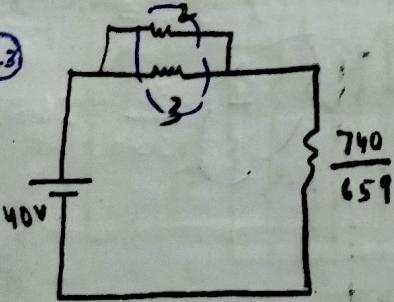

(24)

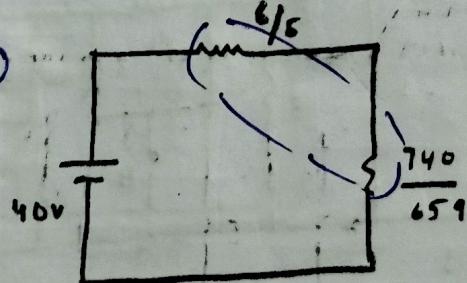








(25)







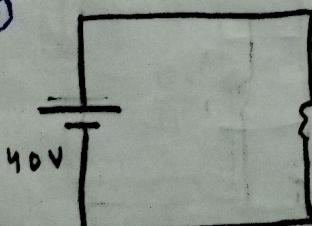


$$V = 40V ; R_{eq} = 2.32 \Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{40}{2.32} = 17.24 A$$

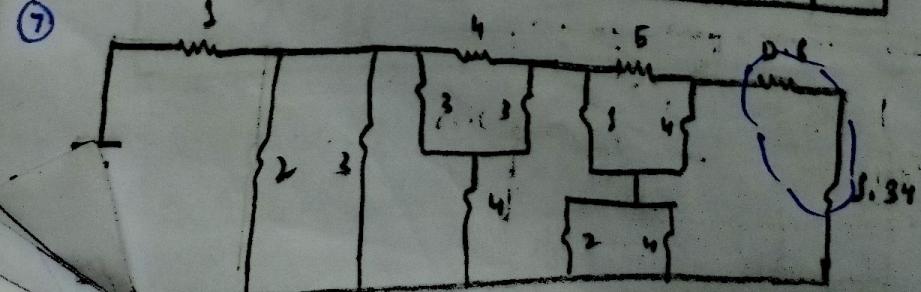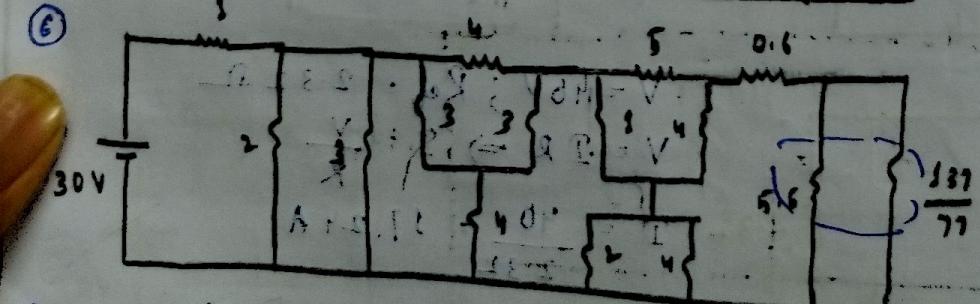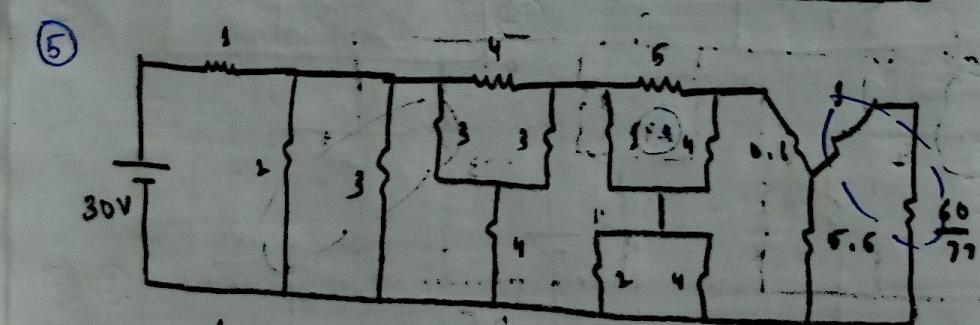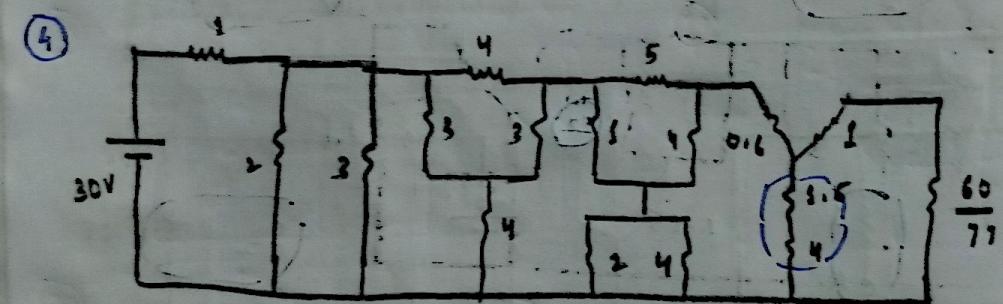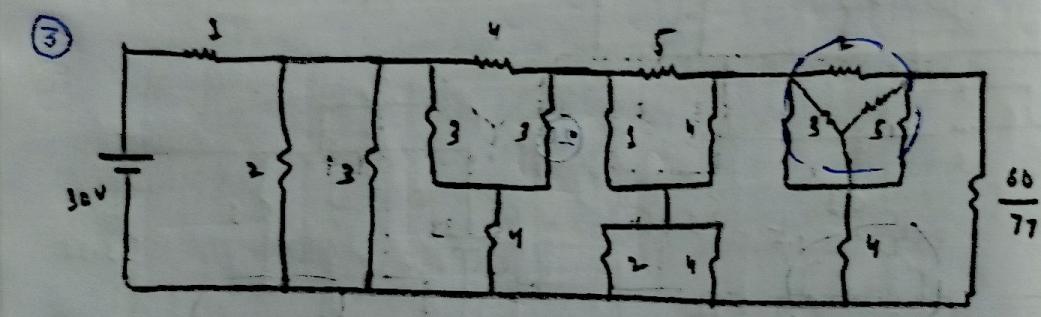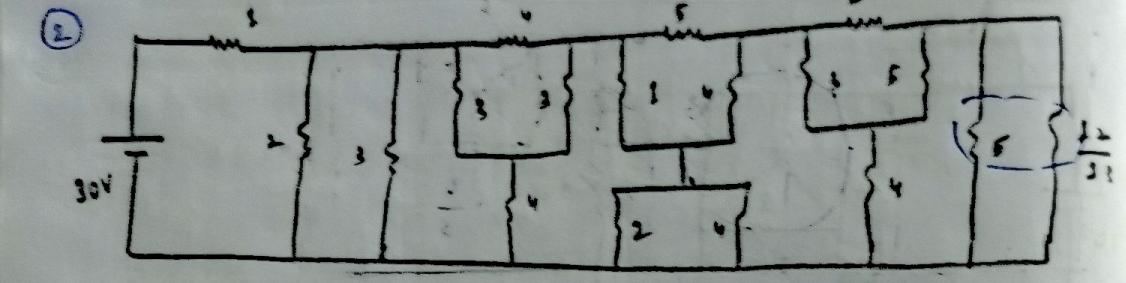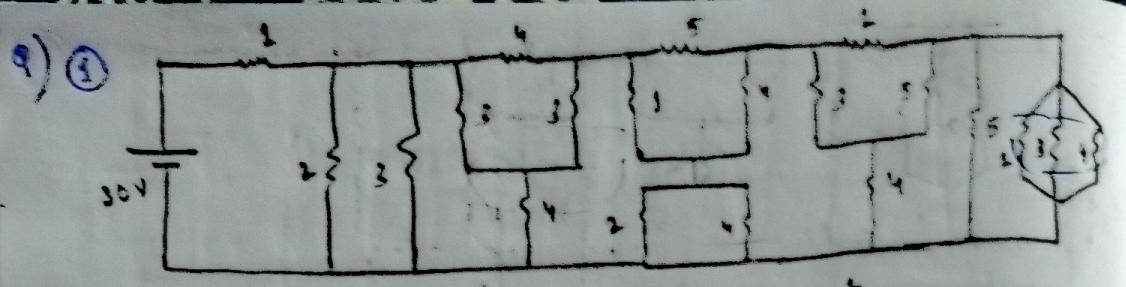


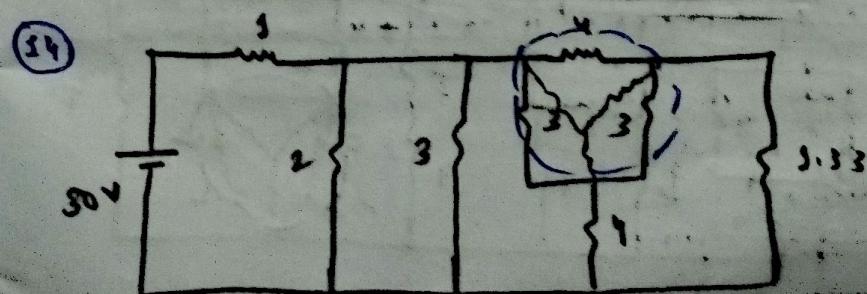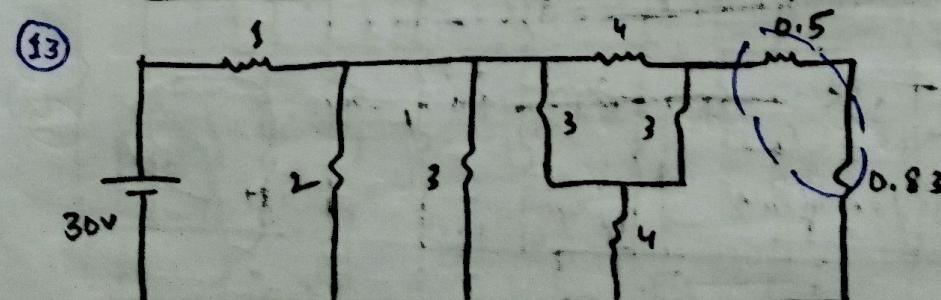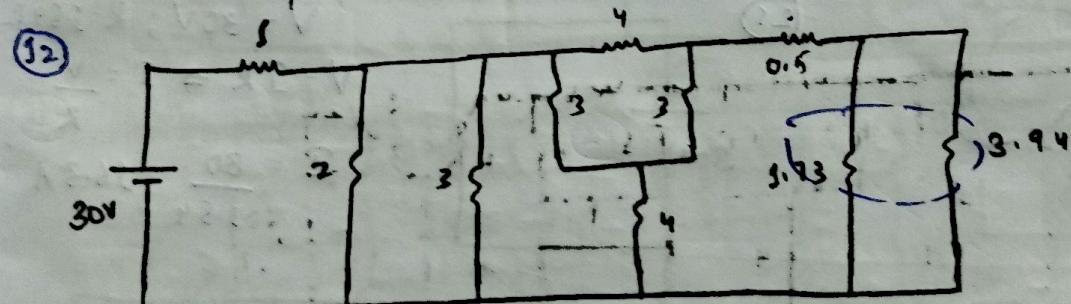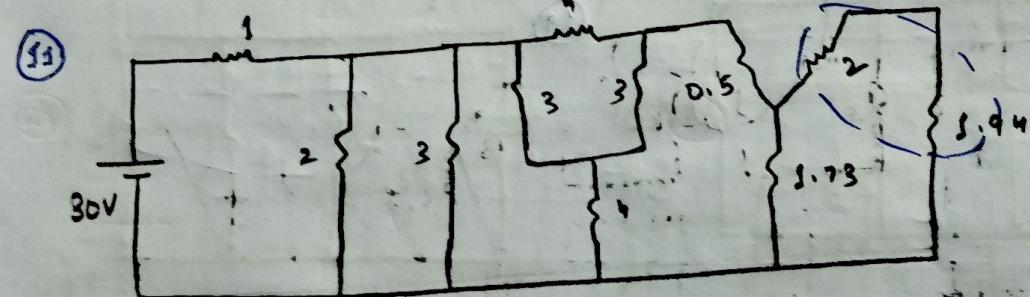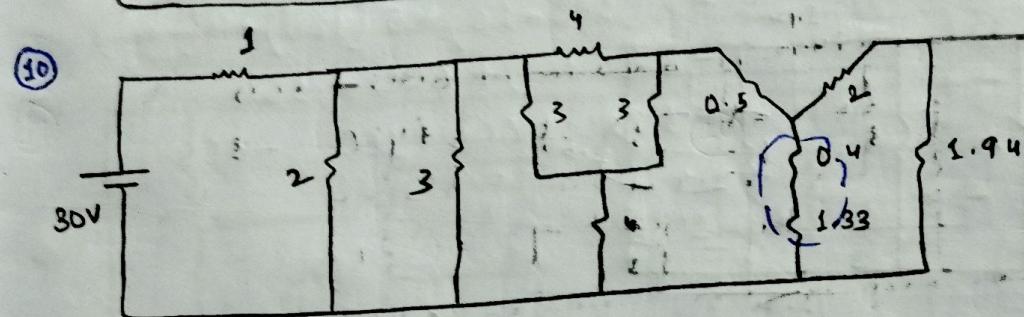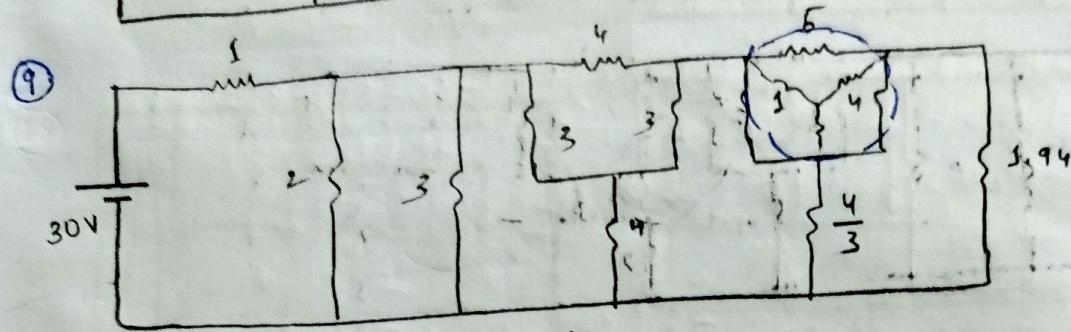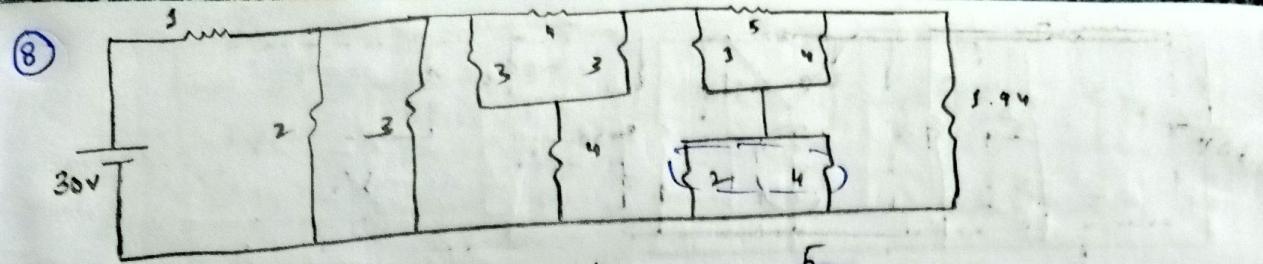


15

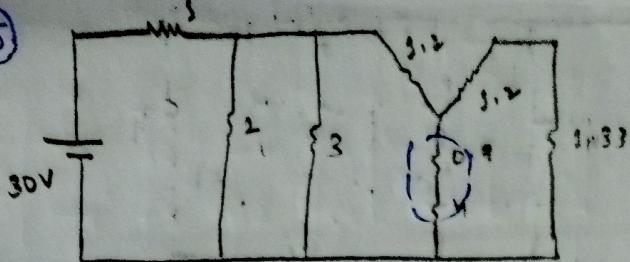


16

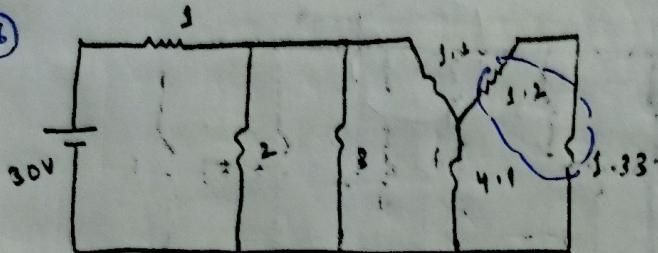


17

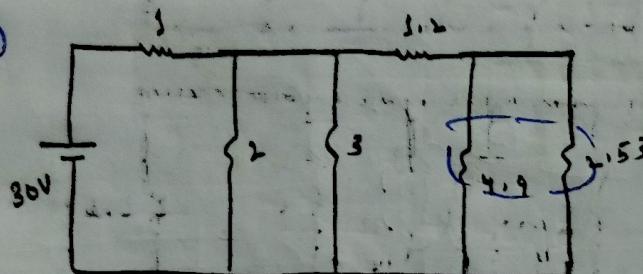


18

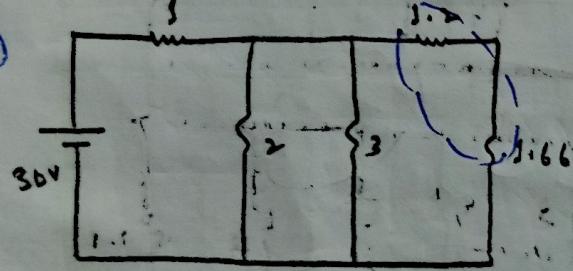


19

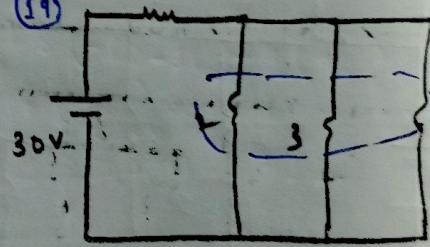

20

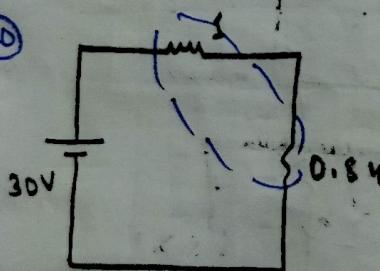

21

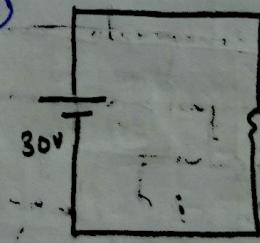


$$V = 30V; R = 3.84 \Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{30}{3.84} = 7.84 A$$

Q) ①

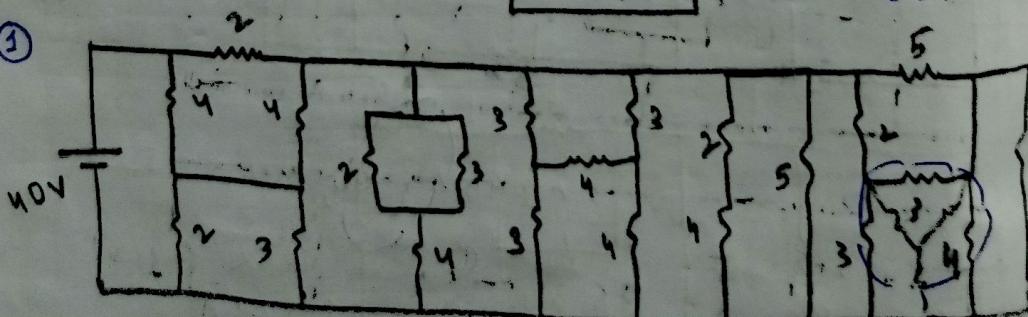


②

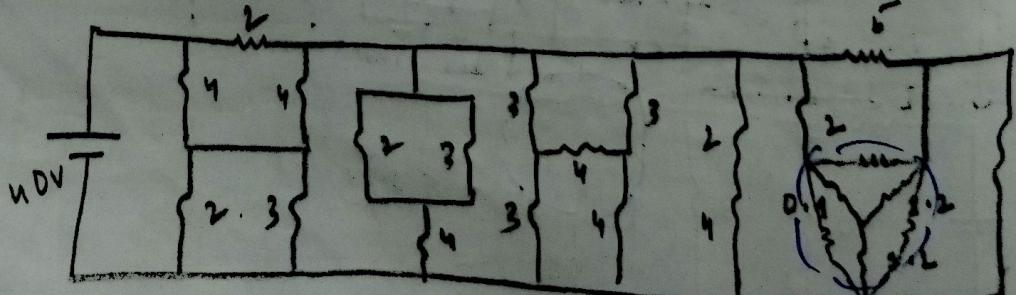


- (3)
40V
- (4)
40V 0.54
- (5)
40V 0.53
- (6)
40V 0.51
- (7)
40V 0.29
- (8)
40V 0.29


⑨

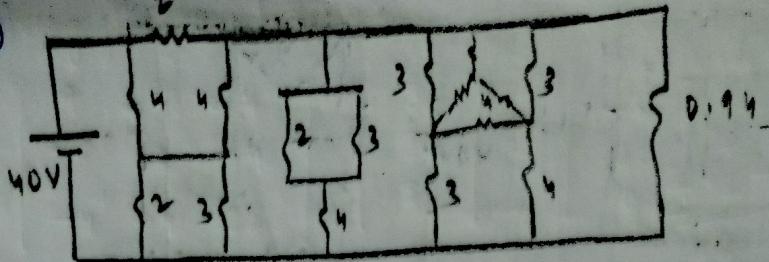


⑩

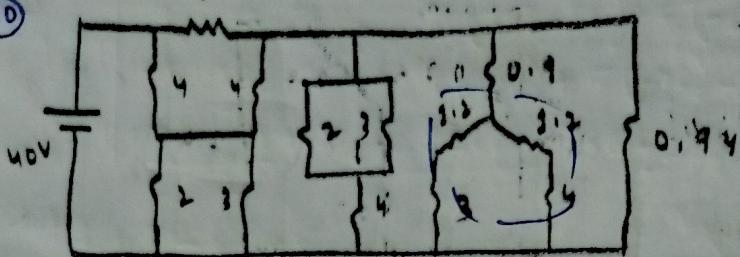


⑪

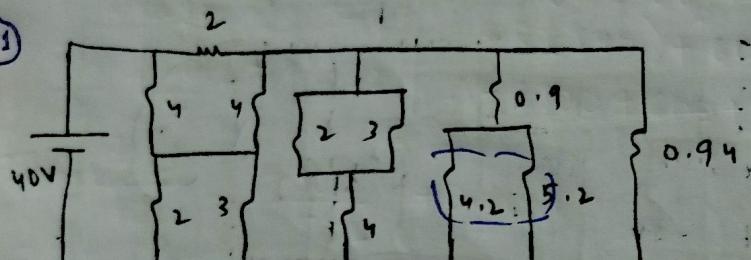


⑫

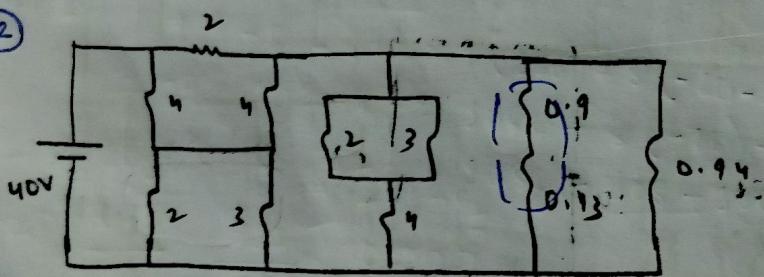


⑬

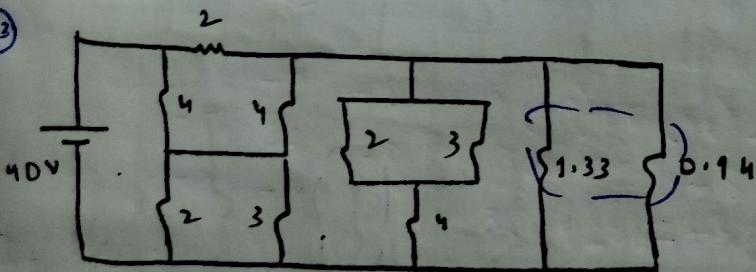



⑭

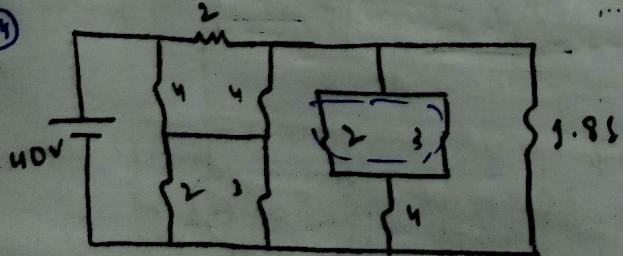

⑮

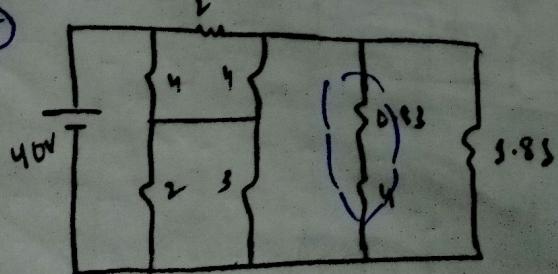


(16)

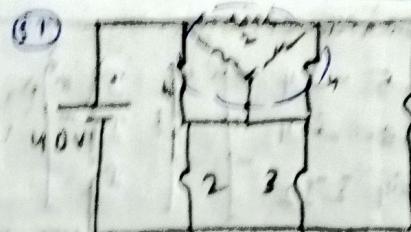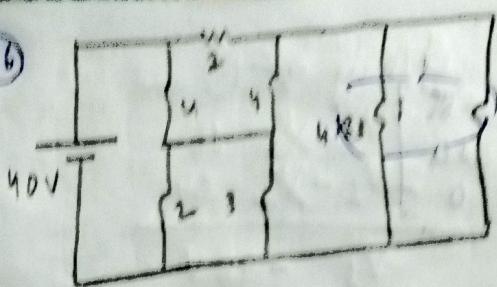


2.01

(18)

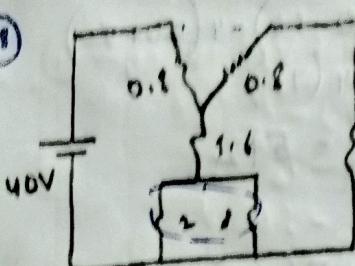


2.03

(19)

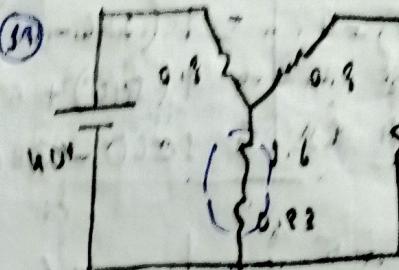


2.03

(20)

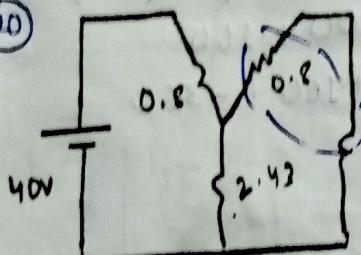


2.03

(21)

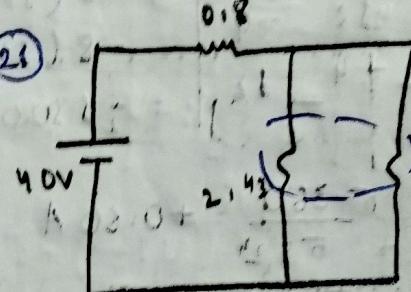


2.03

(22)

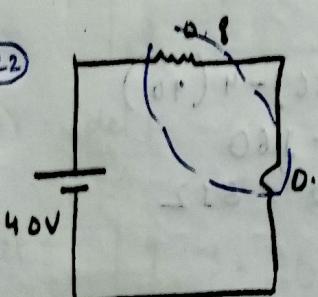

2.03

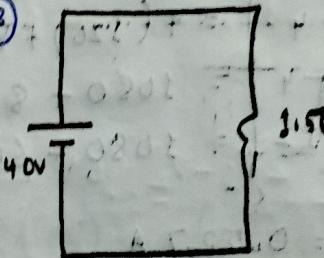

2.03

$$V = 40V; R = 5.56\Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{40}{5.56} = 25.64A$$

KVL and KCL

KVL :-

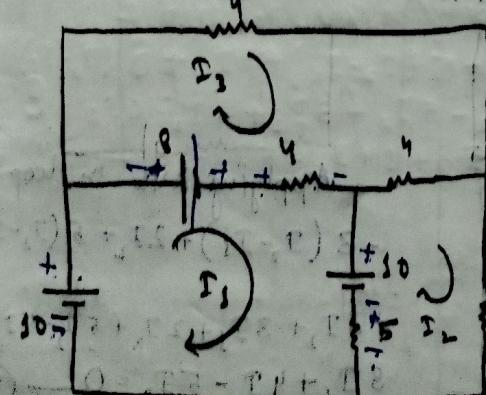Voltage drop in a closed loop is always zero.



Applying KVL in loop 1

$$-50 + 8 + 4(I_1 - I_2) + 5(I_2 - I_3) = 0$$

$$-50 + 8 + 4I_1 - 4I_2 + 5I_2 - 5I_3 = 0$$

$$9I_1 - 5I_2 - 4I_3 = -8 \quad (1)$$

Applying KVL in loop 2,

$$-50 + 4(I_2 - I_3) + 4I_2 + 5(I_2 - I_1) = 0$$

$$-50 + 4I_2 - 4I_3 + 4I_2 + 5I_2 - 5I_1 = 0$$

$$-5I_1 + 8I_2 + 4I_3 = 50 \quad (2)$$

Applying KVL in loop 3,

$$-8 + 4I_3 + 4(I_3 - I_2) + 4(I_3 - I_1) = 0$$

$$-8 + 4I_3 + 4I_3 - 4I_2 + 4I_3 - 4I_1 = 0$$

$$-4I_1 - 4I_2 + 12I_3 = 0 \quad (3)$$

Solving the equations,

$$\begin{bmatrix} 9 & -5 & -4 \\ -5 & 53 & -4 \\ -4 & -4 & 52 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -8 \\ 50 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 9 & -5 & -4 \\ -5 & 53 & -4 \\ -4 & -4 & 52 \end{vmatrix} = 9(556 - 56) + 5(-60 - 56) - 4(20 + 52) \\ = 9(500) + 5(-76) - 4(72) \\ = 1260 - 380 - 288 = 592$$

$$\det I_1 = \begin{vmatrix} -8 & -5 & -4 \\ 50 & 53 & -4 \\ 0 & -4 & 52 \end{vmatrix} = -8(556 - 56) + 5(520) - 4(-40) \\ = -8(500) + 600 + 160 \\ = -5320 + 600 + 160 = -360$$


$$I_1 = \frac{\det I_1}{\Delta} = \frac{-360}{592} = +0.60 A$$

$$\det I_2 = \begin{vmatrix} 9 & -8 & -4 \\ -5 & 50 & -4 \\ -4 & 0 & 52 \end{vmatrix} = 9(520) + 8(-60 - 56) - 4(40) \\ = 5080 + 8(-76) - 160 \\ = 5080 - 608 - 160 = 332$$

$$I_2 = \frac{\det I_2}{\Delta} = \frac{332}{592} = 0.527 A$$

$$\det I_3 = \begin{vmatrix} 9 & -5 & -8 \\ -5 & 53 & 50 \\ -4 & -4 & 0 \end{vmatrix} = 9(40) + 5(40) - 8(20 + 52) \\ = 360 + 200 - 8(72) \\ = 360 + 200 - 576 = -56$$
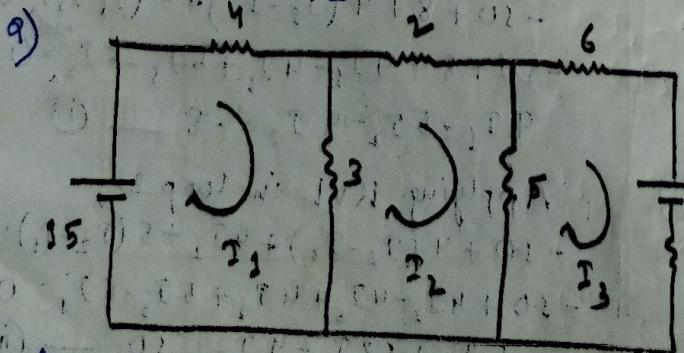
$$I_3 = \frac{\det I_3}{\Delta} = \frac{-56}{592} = 0.027 A$$



Applying KVL in loop 1:

$$-3(I_2 - I_1) + 2I_2 + 5(I_3 - I_2) = 0$$

$$-3I_2 + 3I_1 + 2I_2 + 5I_3 - 5I_2 = 0$$

$$3I_1 + 4I_3 - 5I_2 = 0$$

Applying KVL in loop 1,

$$-15 + 4I_1 + 3(I_1 - I_2) = 0$$

$$-15 + 4I_1 + 3I_1 - 3I_2 = 0$$

$$7I_1 - 3I_2 = 15 \quad \text{--- (1)}$$

Applying KVL in loop 3,

$$-52 + 3I_3 + 5(I_3 - I_2) + 6I_3 = 0$$

$$8I_3 + 15I_3 - 5I_2 + 6I_3 = 52$$

$$34I_3 - 5I_2 = 52 \quad \text{--- (1)}$$

Solving the equations,

$$\begin{bmatrix} 7 & -3 & 0 \\ 3 & 4 & -5 \\ 0 & -5 & 34 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 55 \\ 0 \\ 52 \end{bmatrix}$$

$$\det S = \Delta = \begin{vmatrix} 7 & -3 & 0 \\ 3 & 4 & -5 \\ 0 & -5 & 34 \end{vmatrix} = 7(56-25) + 3(42) \\ = 7(31) + 3(42) \\ = 257 + 326 = 343$$

$$\det S = \begin{vmatrix} 55 & -3 & 0 \\ 0 & 4 & -5 \\ 52 & -5 & 34 \end{vmatrix} = 55(56-25) + 3(60) \\ = 55(31) + 380 \\ = 465 + 380 = 645$$

$$I_1 = \frac{\det S}{\Delta} = \frac{645}{343} = 1.88 A$$

$$\det 2 = \begin{vmatrix} 7 & 55 & 0 \\ 3 & 0 & -5 \\ 0 & 52 & 34 \end{vmatrix} = 7(60) - 55(42) + 0 \\ = 420 - 630 \\ = -250$$

$$I_2 = \frac{\det 2}{\Delta} = \frac{-250}{343} = 0.632 A$$

$$\det 3 = \begin{vmatrix} 7 & -3 & 55 \\ 3 & 4 & 0 \\ 0 & -5 & 32 \end{vmatrix} = 7(48) + 3(86) + 55(-15) \\ = 336 + 258 - 225 \\ = 259$$

$$I_3 = \frac{\det 3}{\Delta} = \frac{259}{343} = 0.638 A$$


KCL :-

Current entering the node = Current leaving the node

Prerequisite assumption,

Current entering = -ve } Assumed by us

Current leaving = +ve

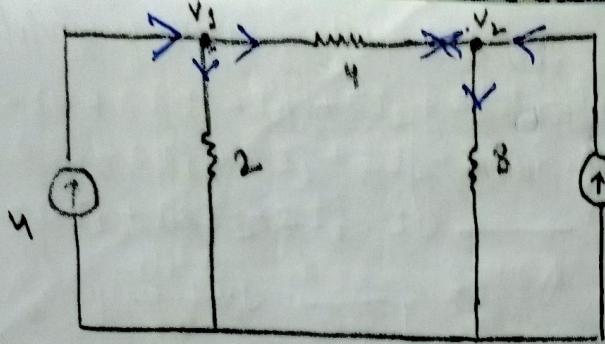

Solving eqn ① and ②,

$$\begin{aligned} 3V_3 - V_2 &= 36 \\ 2V_1 - V_2 &= 64 \end{aligned}$$

$$V_3 = -48 V$$

Applying KCL at node 1,

$$-4 + \frac{V_3 - 0}{2} + \frac{V_3 - V_2}{4} = 0$$

$$-4 + \frac{V_3}{2} + \frac{V_3}{4} - \frac{V_2}{4} = 0 \quad \text{--- (1)}$$

$$\frac{3V_3}{4} - \frac{V_2}{4} = 4 \Rightarrow 3V_3 - V_2 = 16 \quad \text{--- (1)}$$

Putting 'V3' in eqn ①,

$$3(-48) - V_2 = 16$$

$$-144 - V_2 = 16$$

$$V_2 = -160 V$$

Applying KCL at node 2,

$$-8 - \frac{(V_2 - V_3)}{4} + \frac{V_2 - 0}{8} = 0 \quad \text{--- (2)}$$

$$-8 - \frac{V_2}{4} + \frac{V_3}{4} + \frac{V_2}{8} = 0$$

$$-\frac{V_2}{8} + \frac{2V_3}{8} = 8 \Rightarrow 2V_3 - V_2 = 64 \quad \text{--- (2)}$$

$$5 \quad \text{--- (1) + (2)}$$

Applying KVL in loop 1,

$$-9 + 7 + 5(I_3 - I_2) + 8 + 6(I_3 - I_1) = 0$$

$$5I_3 - 5I_2 + 6I_3 - 6I_1 = -16$$

$$11I_3 - 6I_2 - 5I_1 = -16 \quad \text{--- (1)}$$

Applying KVL in loop 2,

$$-8 + 5(I_2 - I_3) + 3I_2 + 6(I_2 - I_1) = 0$$

$$5I_2 - 5I_3 + 3I_2 + 6I_2 - 6I_1 = 8$$

$$-6I_1 + 14I_2 - 5I_3 = 8 \quad \text{--- (2)}$$


Applying KVL in loop 3,

$$-7 + 5I_3 + 5(I_3 - I_2) + 5(I_3 - I_1) = 0$$

$$5I_3 + 5I_3 - 5I_2 + 5I_3 - 5I_1 = 7$$

$$-5I_1 - 5I_2 + 15I_3 = 7 \quad \text{--- (3)}$$

Solving the equations,

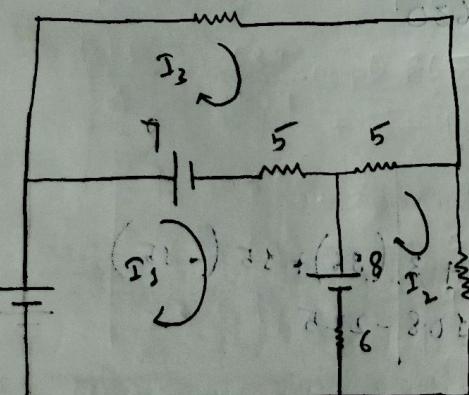

$$20 + 9I_3 = 7$$

20 + positive terminal
9I3 + positive terminal
9I3 + negative terminal

$$\left[\begin{array}{ccc} 11 & -6 & -5 \\ -6 & 14 & -5 \\ -5 & -5 & 15 \end{array} \right] \cdot \left[\begin{array}{c} I_1 \\ I_2 \\ I_3 \end{array} \right] = \left[\begin{array}{c} -6 \\ 8 \\ 7 \end{array} \right]$$

$$\Delta = \left| \begin{array}{ccc} 11 & -6 & -5 \\ -6 & 14 & -5 \\ -5 & -5 & 15 \end{array} \right| = 11(230+25) + 6(-90+25) - 5(30+70) \\ = 11(255) + 6(-65) - 5(100) \\ = 2035 - 690 - 500 = 845$$

$$\det 1 = \left| \begin{array}{ccc} -6 & -6 & -5 \\ 8 & 14 & -5 \\ 7 & -5 & 15 \end{array} \right| = -6(230+35) + 6(120+35) - 5(-40+98) \\ = -6(265) + 6(155) - 5(-58) \\ = -1590 + 930 + 290 = 510$$

$$I_1 = \frac{\det 1}{\Delta} = \frac{510}{845} = 0.60 A$$


$$\det 2 = \left| \begin{array}{ccc} 11 & -6 & -5 \\ -6 & 8 & -5 \\ 5 & 7 & 15 \end{array} \right| = 11(320+35) + 6(-90+25) - 5(-90+25) \\ = 11(355) + 6(-65) - 5(-65) \\ = 3705 - 390 + 325 = 3640$$

$$I_2 = \frac{\det 2}{\Delta} = \frac{3640}{845} = 4.31 A$$

$$\det 3 = \left| \begin{array}{ccc} 11 & -6 & -6 \\ -6 & 14 & 8 \\ 5 & -5 & 7 \end{array} \right| = 11(98+40) + 6(-42-40) - 6(30-70) \\ = 11(138) + 6(-82) - 6(-40) \\ = 1518 - 492 + 240 = 1266$$

$$I_3 = \frac{\det 3}{\Delta} = \frac{1266}{845} = 1.498 A$$

a)

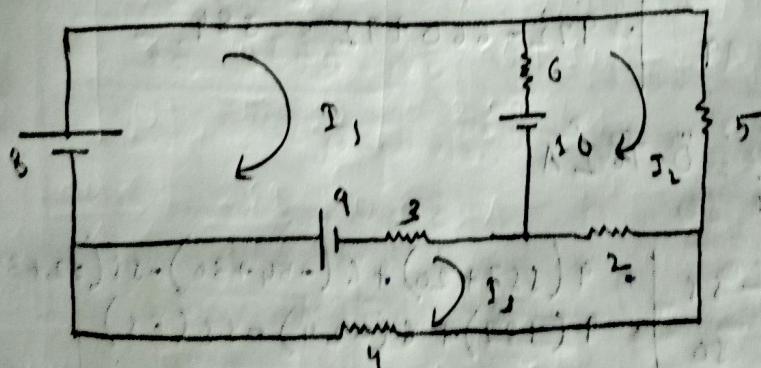

Applying KVL in loop 1,

$$-8 + 6(I_1 - I_2) + 50 + 3(I_1 - I_3) + 9 = 0$$

$$-8 + 6I_1 - 6I_2 + 50 + 3I_1 - 3I_3 + 9 = 0$$

$$9I_1 - 6I_2 - 3I_3 = -55 \quad \textcircled{1}$$

Applying KVL in loop 2,

$$\begin{aligned}-50 + 6(I_2 - I_1) + 5I_2 + 2(I_2 - I_3) &= 0 \\ 6I_2 - 6I_1 + 5I_2 + 2I_2 - 2I_3 &= 50 \\ -6I_3 + 13I_2 - 2I_3 &= 50 \quad \text{--- (II)}\end{aligned}$$

Applying KVL in loop 3,

$$\begin{aligned}-9 + 3(I_3 - I_1) + 2(I_3 - I_2) + 4I_3 &= 0 \\ 3I_3 - 3I_1 + 2I_3 - 2I_2 + 4I_3 &= 9 \\ -3I_1 - 2I_2 + 9I_3 &= 9 \quad \text{--- (III)}\end{aligned}$$

Solving the equations,

$$\begin{bmatrix} 9 & -6 & -3 \\ -6 & 13 & -2 \\ -3 & -2 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -50 \\ 10 \\ 9 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 9 & -6 & -3 \\ -6 & 13 & -2 \\ -3 & -2 & 9 \end{vmatrix} = 9(557 - 4) + 6(-54 - 6) - 3(32 + 39) \\ = 9(553) + 6(-60) - 3(51) \\ = 5057 - 360 - 153 = 504$$

$$\det 1 = \begin{vmatrix} -55 & -6 & -3 \\ 10 & 13 & -2 \\ 9 & -2 & 9 \end{vmatrix} = -55(+557 - 4) + 6(90 + 58) - 3(-20 - 55) \\ = -55(553) + 6(148) - 3(-75) \\ = -5243 + 888 + 225 = 1584 = 584$$


$$I_1 = \frac{\det 1}{\Delta} = \frac{584}{504} = 0.865 \text{ A}$$

$$\det 2 = \begin{vmatrix} 9 & -55 & -3 \\ -6 & 50 & -2 \\ -3 & 9 & 9 \end{vmatrix} = 9(90 + 58) + 55(-54 - 6) - 3(-54 + 36) \\ = 9(148) + 55(-60) - 3(-24) \\ = 972 - 330 + 72 = 384$$

$$I_2 = \frac{\det 2}{\Delta} = \frac{384}{504} = 0.762 \text{ A}$$

$$\det 3 = \begin{vmatrix} 9 & -6 & -55 \\ -6 & 13 & 50 \\ -3 & -2 & 9 \end{vmatrix} = 9(557 + 20) + 6(-54 + 30) - 55(32 + 39) \\ = 9(577) + 6(-24) - 55(53) \\ = 5233 - 144 - 2895 = 528$$
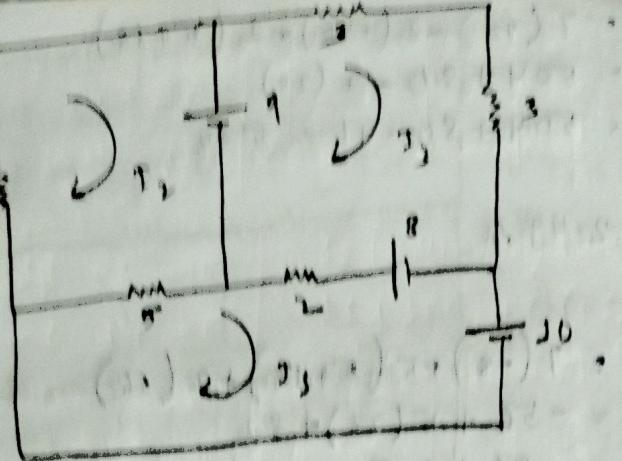
$$I_3 = \frac{\det 3}{\Delta} = \frac{528}{504} = 1.047 \text{ A}$$



Applying KVL in loop 1,

$$-10 + 5(T_1 - T_2) + 2(T_3 - T_1) + 8 = 0$$

$$5T_1 - 5T_2 + 2T_3 - 2T_1 = 2$$

$$7T_1 - 5T_2 - 2T_3 = 2 \quad \textcircled{1}$$

Applying KVL in loop 2,

$$-9 + 5(T_2 - T_3) + 3T_2 = 0$$

$$5T_2 - 5T_3 + 3T_2 = 9$$

$$-5T_3 + 8T_2 = 9 \quad \textcircled{2}$$

Applying KVL in loop 3,

$$-8 + 2(T_3 - T_1) + 9 + 3T_3 + 3T_1 = 0$$

$$2T_1 - 2T_3 + 3T_3 + 3T_1 = -5$$

$$-2T_3 + 8T_1 = -5 \quad \textcircled{3}$$

Solving the equations,

$$\begin{bmatrix} 7 & -5 & -2 \\ -5 & 8 & 0 \\ -2 & 0 & 8 \end{bmatrix} \begin{bmatrix} T_1 \\ T_2 \\ T_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 9 \\ -5 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 7 & -5 & -2 \\ -5 & 8 & 0 \\ -2 & 0 & 8 \end{vmatrix} = 7(64) + 5(-40) - 2(36) \\ = 448 - 200 - 72 \\ = 256$$

$$\det S = \begin{vmatrix} 2 & -5 & -2 \\ 9 & 8 & 0 \\ -5 & 0 & 8 \end{vmatrix} = 2(64) + 5(72) - 2(36) \\ = 128 + 360 - 72 \\ = 472$$

$$I_1 = \frac{\det S}{\Delta} = \frac{472}{256} = 2.85 A$$


$$\text{at } 2 : \begin{vmatrix} 7 & 2 & -2 \\ -5 & 9 & 0 \\ -2 & -1 & 8 \end{vmatrix} = 7(-12) - 2(-40) - 2(5 + 58) \\ = 504 + 80 - 2(63) \\ = 504 + 80 - 126 = 538$$

$$T_2 = \frac{\det 2}{\Delta} = \frac{538}{236} = 2.491$$

$$\det 3 : \begin{vmatrix} 7 & -5 & 2 \\ -5 & 8 & 9 \\ -2 & 0 & -1 \end{vmatrix} = 7(-8) + 5(5 + 58) + 2(56) \\ = -56 + 5(63) + 112 \\ = -56 + 315 + 112 = 371$$

$$T_3 = \frac{\det 3}{\Delta} = \frac{371}{236} = 0.428 A$$

Q)

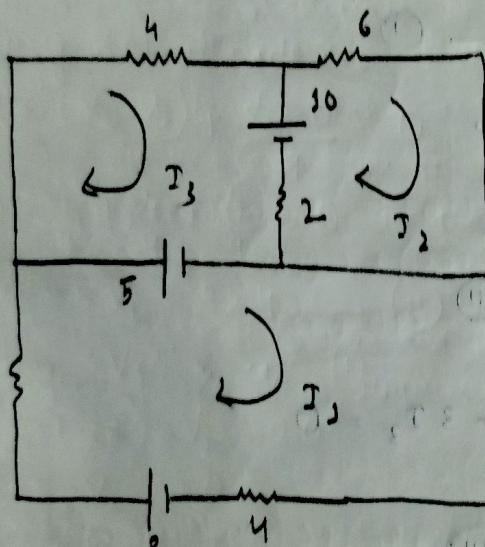

Applying KVL in loop 1,
 $-5 + 4I_1 + 8 + 3I_3 = 0$
 $7I_1 = -3 \Rightarrow I_1 = \frac{-3}{7} = -0.428$

Applying KVL in loop 2,
 $-50 + 6I_2 + 2(I_2 - I_3) = 0$
 $6I_2 + 2I_2 - 2I_3 = 50$
 $8I_2 - 2I_3 = 50 \quad \text{--- (1)}$

Applying KVL in loop 3, I_3
 $-50 + 2(I_3 - I_2) + 5 + 4I_3 = 0$
 $2I_3 - 2I_2 + 4I_3 = 5$
 $-2I_2 + 6I_3 = 5 \quad \text{--- (2)}$

Solving eqn (1) and (2)
 $(8I_2 - 2I_3 - 50) \times 3$
 $-2I_2 + 6I_3 = 5$
 $24I_2 - 6I_3 = 150$
 $-2I_2 + 6I_3 = 5$
 $22I_2 = 155$

$$I_2 = \frac{85}{22} = 3.86 A$$

Substituting (I_2) in eqn (2),
 $8(3.86) - 2I_3 = 50$


$$32.48 - 2I_3 = 50$$

$$-2I_3 = 17.52 \Rightarrow I_3 = \frac{17.52}{2} = 8.76 A$$

From eqn (1), $I_1 = \frac{3}{7} = 0.428 A$

And, $I_2 = 3.86 A$

$$I_3 = 8.76 A$$

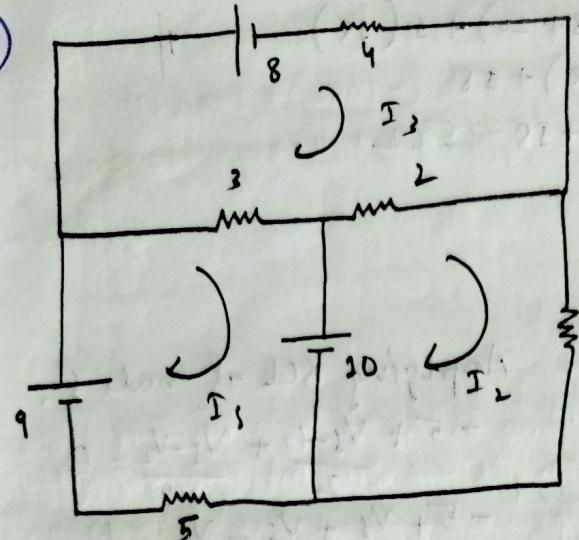

Applying KVL in loop 1,

$$-50 + 5I_1 + 9 + 3(I_1 - I_3) = 0$$

$$5I_1 + 3I_1 - 3I_3 = 1 \quad \text{--- (1)}$$

$$8I_1 - 3I_3 = 5$$

Applying KVL in loop 2,

$$-50 + 2(I_2 - I_1) + 4I_2 = 0$$

$$-50 + 2I_2 - 2I_1 + 4I_2 = 0 \quad \text{--- (2)}$$

$$6I_2 - 2I_1 = 50 \quad \text{--- (2)}$$

Applying KVL in loop 3,

$$-8 + 4I_3 + 2(I_3 - I_2) + 3(I_3 - I_1) = 0$$

$$4I_3 + 2I_3 - 2I_2 + 3I_3 - 3I_1 = 8 \quad \text{--- (3)}$$

$$-3I_1 - 2I_2 + 9I_3 = 8 \quad \text{--- (3)}$$

Solving the equations,

$$\begin{bmatrix} 8 & 0 & -3 \\ 0 & 6 & -2 \\ -3 & -2 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 50 \\ 8 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 & 0 & -3 \\ 0 & 6 & -2 \\ -3 & -2 & 9 \end{vmatrix} = 8(54 - 4) - 3(58) \\ = 8(50) - 3(58) \\ = 400 - 54 = 346$$

$$\det 1 = \begin{vmatrix} 5 & 0 & -3 \\ 10 & 6 & -2 \\ 8 & -2 & 9 \end{vmatrix} = 5(54 - 4) - 3(-20 - 48) \\ = 50 - 3(-68) \\ = 50 + 204 = 254$$


$$I_1 = \frac{\det 1}{\Delta} = \frac{254}{346} = 0.734 \text{ A}$$

$$\det 2 = \begin{vmatrix} 8 & 5 & -3 \\ 0 & 10 & -2 \\ -3 & 8 & 9 \end{vmatrix} = 8(90 + 56) - 5(-8) - 3(30) \\ = 8(146) + 40 - 90 \\ = 840 + 40 - 90 = 756$$

$$I_2 = \frac{\det 2}{\Delta} = \frac{756}{346} = 2.185 \text{ A}$$

$$.3 = \begin{vmatrix} 8 & 0 & 3 \\ 0 & 6 & 30 \\ -3 & -2 & 8 \end{vmatrix} = 8(48+20) + 3(-58) \\ = 8(68) + 3(-58) \\ = 544 + 38 = 562$$
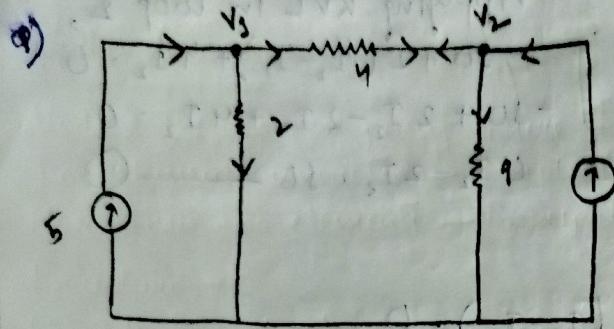
$$I_3 = \frac{\text{det } 3}{\Delta} = \frac{562}{346} = 1.624 A$$



Applying KCL at node 1,

$$-5 + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{4} = 0$$

$$-5 + \frac{V_1}{2} + \frac{V_1}{4} - \frac{V_2}{4} = 0$$

$$3V_1 - V_2 = 20 \quad \text{--- (1)}$$

Applying KCL at node 2,

Solving eq $\frac{V_1}{(1)}$ and $\frac{V_2}{(1)}$,

$$-9 - \frac{(V_2 - V_1)}{4} + \frac{V_2 - 0}{9} = 0$$

$$15V_1 - 15V_2 = 500$$

$$-9 - \frac{V_2}{4} + \frac{V_1}{4} + \frac{V_2}{9} = 0$$

$$9V_1 - 6V_2 = 824$$

$$9V_1 - 5V_2 = 824 \quad \text{--- (11)}$$

$$6V_1 = -224$$

Putting ' V_1 ' in eq $\frac{V_2}{(1)}$


$$V_1 = -\frac{224}{6} = -37.33 V$$

$$3(-37.33) - V_2 = 20$$

$$-112 - V_2 = 20 \quad (\text{--- (2)})$$

$$V_2 = -132 V$$

9)

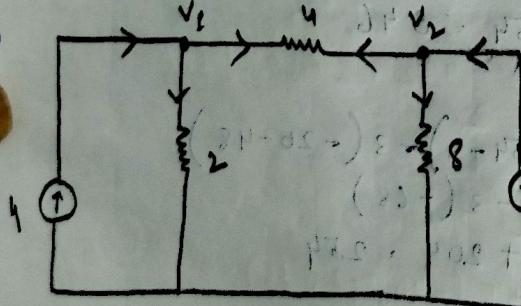

Applying KCL at node 1,

$$-4 + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{4} = 0$$

$$-4 + \frac{V_1}{2} + \frac{V_1}{4} - \frac{V_2}{4} = 0$$

$$3V_1 - V_2 = 16 \quad \text{--- (1)}$$

Applying KCL at node 2,

Solving eq $\frac{V_1}{(1)}$ and $\frac{V_2}{(1)}$,

$$-6 - \frac{(V_2 - V_1)}{4} + \frac{V_2 - 0}{8} = 0$$

$$3V_1 - V_2 = 16$$

$$-6 - \frac{V_2}{4} + \frac{V_1}{4} + \frac{V_2}{8} = 0$$

$$2V_1 - V_2 = 48$$

$$2V_1 - V_2 = 48 \quad \text{--- (11)}$$


$$V_1 = -32 V$$

Putting ' V_1 ' in eq $\frac{V_2}{(1)}$,

$$3(-32) - V_2 = 16$$

$$-96 - V_2 = 16$$

$$V_2 = -112 V$$

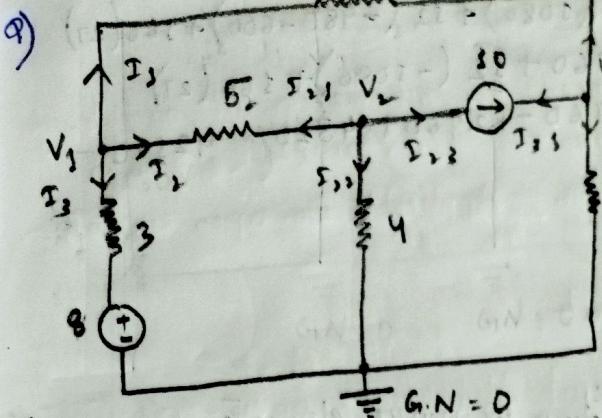

Applying KCL at node 5,

$$I_1 + I_2 + I_3 = 0 \quad \text{--- (i)}$$

$$\frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{5} + \frac{V_1 - V_2}{3} = 0$$

$$\frac{V_1 - V_3}{4} - \frac{V_2 - V_3}{5} + \frac{V_1 - V_2}{3} = \frac{8}{3}$$

$$47V_1 - 52V_2 - 55V_3 = 860 \quad \text{--- (ii)}$$

Applying KCL at node 2,

$$I_{12} + I_{23} + I_{31} = 0$$

Applying KCL at node 3,

$$I_{31} + I_{23} + I_{12} = 0$$

$$-30 + \frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{3} = 0$$

$$\frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{3} = 50 \quad \text{--- (iii)}$$

$$-3V_1 + 7V_3 = 320 \quad \text{--- (iv)}$$

$$-4V_3 + 9V_2 = -200 \quad \text{--- (v)}$$

Solving the equations, we will get

$$\begin{bmatrix} 47 & -52 & -55 \\ -4 & 9 & 0 \\ -3 & 0 & 7 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 860 \\ -200 \\ 320 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 47 & -52 & -55 \\ -4 & 9 & 0 \\ -3 & 0 & 7 \end{vmatrix} = 47(63) + 52(-28) - 55(27) \\ = 2963 - 336 - 405 \\ = 2220$$

$$\text{det } S = \begin{vmatrix} 360 & -52 & -55 \\ -200 & 9 & 0 \\ 120 & 0 & 7 \end{vmatrix} = 360(63) + 52(-3400) - 55(-3080) \\ = 10080 - 18800 + 16200 \\ = 9480$$

$$V_1 = \frac{\text{det } S}{\Delta} = \frac{9480}{2220} = 4.27 \text{ V}$$

$$\text{det } 2 = \begin{vmatrix} 47 & 360 & -55 \\ -4 & -200 & 0 \\ -3 & 120 & 7 \end{vmatrix} = (47(-3400) - 360(-28) - 55(-480 - 600)) \\ = -65800 + 4480 - 55(-3080) \\ = -65800 + 4480 + 16200 = -45320$$

$$V_2 = \frac{\text{det } 2}{\Delta} = \frac{-45320}{2220} = -20.324 \text{ V}$$

$$\det 3 = \begin{vmatrix} 47 & -52 & 560 \\ -4 & 9 & -200 \\ -3 & 0 & 520 \end{vmatrix} = 47(5080) + 52(-480-600) + 560(27) \\ = 50760 + 52(-5080) + 560(27) \\ = 50760 - 52960 + 4320 = 42320$$

$$V_3 = \frac{\det 3}{4} = \frac{42320}{2220} = 18.972 \text{ V}$$

Nodal Analysis :-

Node : The common point where two or more elements are connected.
 Two elements connected — Simple node \rightarrow Current Division
 More than two elements — Principal node \rightarrow Current Division


Procedure :-

- (i) Identify the total number of nodes.
- (ii) Assign the voltage at each node. One node is taken as reference node (datum), potential taken as 0V.
- (iii) Develop the KCL equations for each non-reference node.
- (iv) Solve the KCL equations to get the node voltage.

NOTE :-

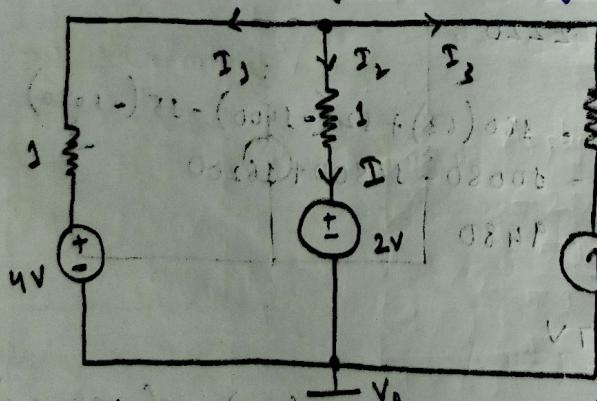- (i) Applicable for both planar and non-planar networks.
- (ii) Number of equations required to solve an electrical network is $e = N - 1$.

Q) Find the value of current I using nodal analysis.



Applying KCL in node V :

$$I_1 + I_2 + I_3 = 0 \\ \frac{(V-0)-4}{1} + \frac{(V-0)-2}{1} - 2 = 0$$

$$V - 4 + V - 2 - 2 = 0$$

$$2V = 8$$

$$V = \frac{8}{2} = 4V$$

$$I = I_2 = \frac{V-2}{1}$$

$$I = 4 - 2 = 2 \text{ A (Ans)}$$

No. of nodes = 2

V_0 = Reference node = 0V

V = Non-Reference node

Important cases for finding current directly:-


Applying KVL,

$$V_x - IR - V_y = V_y$$

$$I = (V_x - V_y)/R$$

Applying KVL,

$$I = (V_x - V_y)/R$$

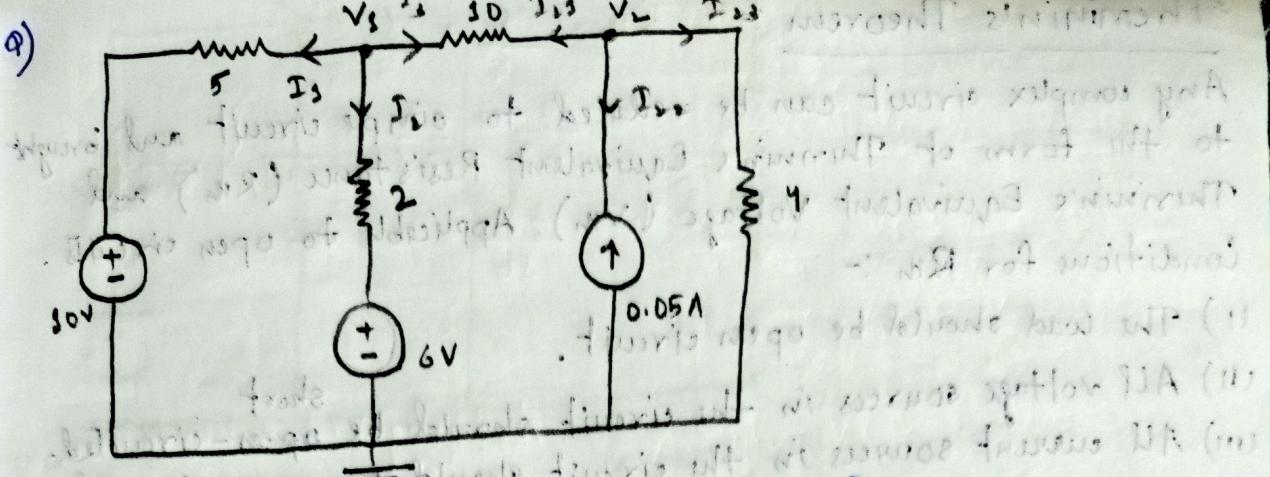

Applying KCL in node 1, $[I_1 + I_2 + I_3 = 0]$

$$\frac{(V_3 - 0)}{5} + \frac{(V_3 - 0)}{2} + \frac{(V_3 - V_2)}{50}$$

$$\frac{V_3}{5} - 2 + \frac{V_3}{2} - 3 + \frac{V_3}{50} - \frac{V_2}{50} = 0$$

$$8V_3 - V_2 = 50 \quad \textcircled{1}$$

Applying KCL in node 2, $[I_{21} + I_{22} + I_{23} = 0]$

$$\frac{(V_2 - V_3)}{10} + \frac{(V_2 - 0)}{4} - 0.05 = 0$$

$$\frac{V_2 - V_3}{10} + \frac{V_2}{4} = 0.05$$

$$-2V_3 + 7V_2 = 1 \quad \textcircled{11}$$

Solving eq $\textcircled{1}$ and $\textcircled{11}$,

$$8V_3 - V_2 = 50$$

$$-8V_3 + 28V_2 = 40$$

$$27V_2 = 54$$

$$V_2 = \frac{54}{27} = 2V$$

Putting ' V_2 ' in eq $\textcircled{11}$,

$$-2V_3 + 7(2) = 1$$

$$-2V_3 = -13$$

$$V_3 = \frac{-13}{2} = 6.5V$$

$$G.P.E = \frac{V_2}{R_2} = \frac{2}{2 \times 10} = 0.1A$$


$$\frac{(AV)}{R_2} = 0.1A$$

Theminin's Theorem :-


Any complex circuit can be reduced to simple circuit and to the form of Theminin's Equivalent Resistance (R_{th}) and Theminin's Equivalent Voltage (V_{th}). Applicable to open circuit.

Conditions for R_{th} :-

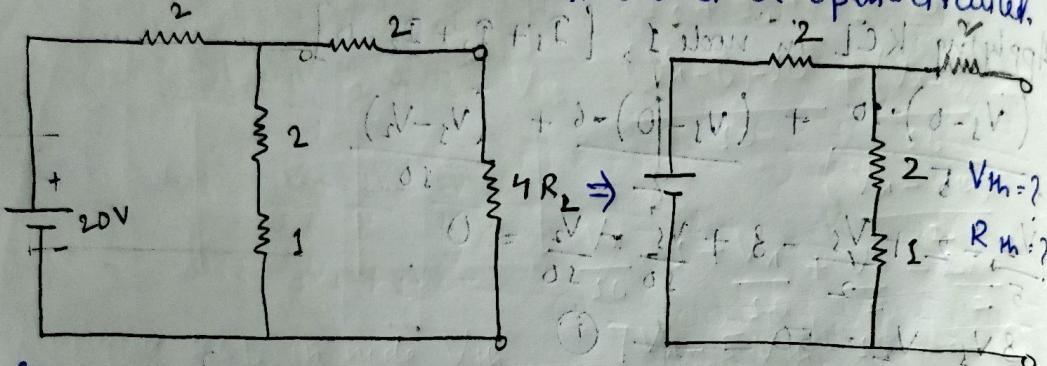
- (i) The load should be open circuit.
- (ii) All voltage sources in the circuit should be short-circuited.
- (iii) All current sources in the circuit should be open-circuited.




Step - I : Find R_{th} ?

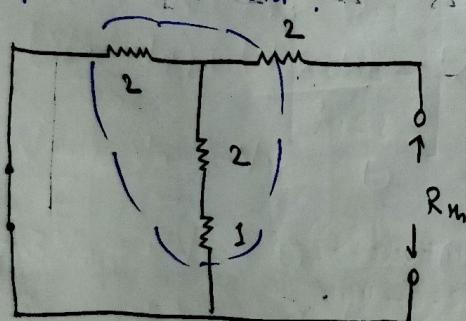
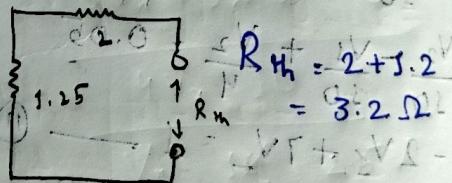
$$R_{th} = 2 \left(\frac{2 \times 3}{2+3} \right) = \frac{6}{5} = 1.2 \Omega$$



Step - II : Calculate V_{th} ?

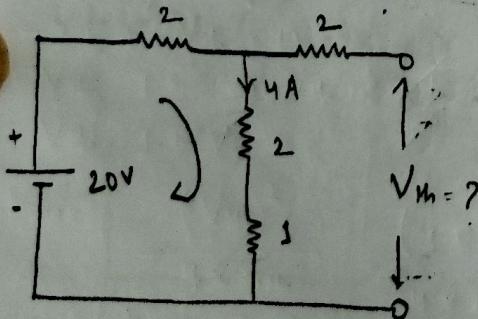

In 3 Ω Resistor,

$$V = IR$$

$$V_{th} = 4 \times 3 = 12V$$


Applying KVL in loop,

$$-20 + 2I + 2I + I = 0$$

$$5I - 20 = 0$$

$$5I = 20$$

$$I = \frac{20}{5} = 4A$$




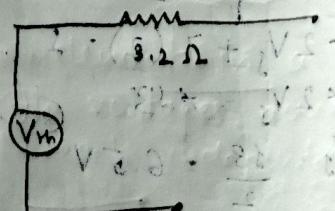


Step - III : Theminin's Equivalent eq. n


$$P_{max} = \frac{(V_{th})^2}{4 \times R_{th}}$$

↑ Max power transferred to circuit
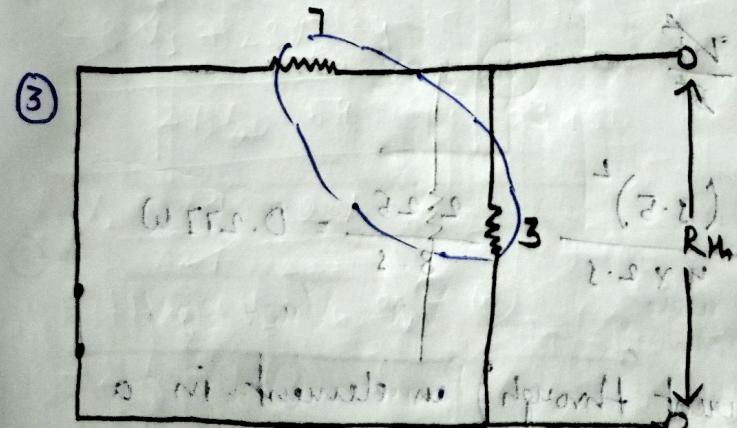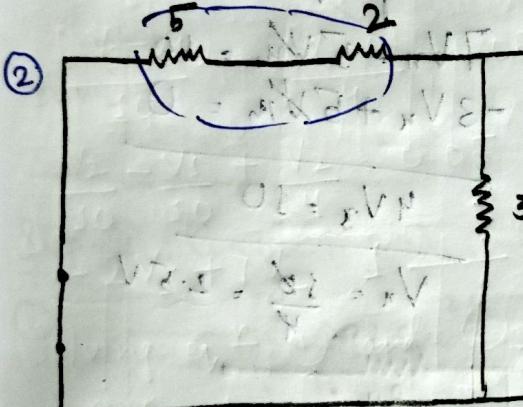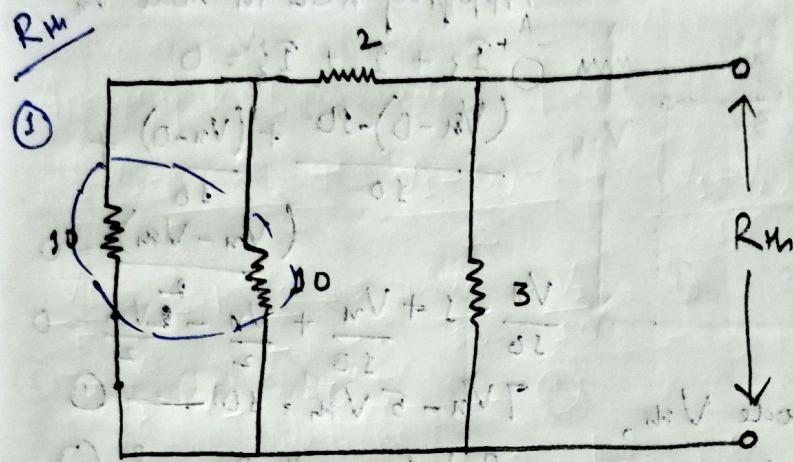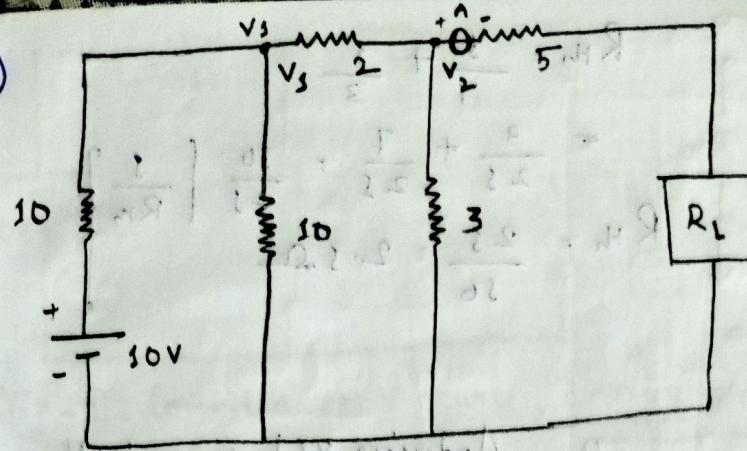
$$P_{max} = \frac{144}{4 \times 1.2} = 33.2W$$




(4)

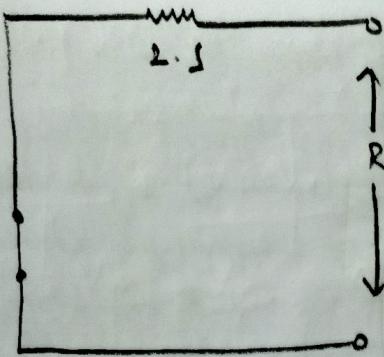

$$R_{Hn} = \frac{3}{7} + \frac{5}{3}$$

$$= \frac{3}{25} + \frac{7}{25} = \frac{50}{25} \left(\frac{1}{R_{Hn}} \right)$$

$$R_{Hn} = \frac{25}{50} = 2.5 \Omega$$

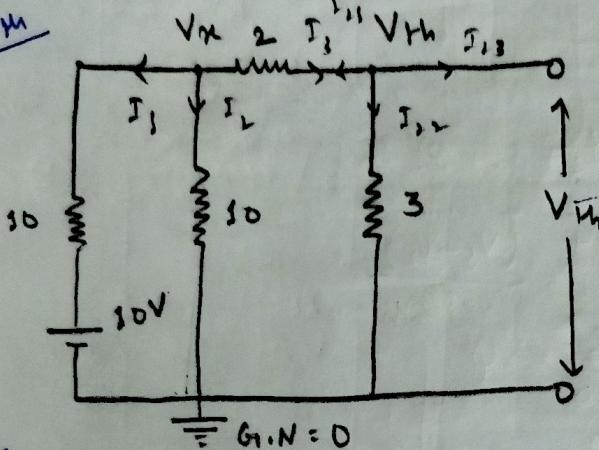V_HnApplying KCL in node V_Hn ,

$$I_{2s} + I_{22} + I_{23} = 0$$

$$\frac{(V_Hn - V_x)}{2} + \frac{(V_Hn - 0)}{3} = 0$$

$$\frac{V_Hn}{2} - \frac{V_x}{2} + \frac{V_Hn}{3} = 0$$

$$-3V_x + 5V_Hn = 0 \quad \textcircled{ii}$$

Putting ' V_x ' in eq \textcircled{ii} ,

$$-3(2.5) + 5V_Hn = 0$$

$$-7.5 + 5V_Hn = 0$$

$$5V_Hn = 7.5 \Rightarrow V_Hn = \frac{7.5}{5}$$

$$V_Hn = 1.5V$$

$$P_{max} = \frac{(V_Hn)^2}{4 \times R_{Hn}} = \frac{(1.5)^2}{4 \times 2.5} = \frac{2.25}{8 \times 2.5} = 0.277W$$

Superposition Theorem :-

The voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.

Minimum two sources are required.

Applying KCL in node V_n ,

$$I_1 + I_2 + I_3 = 0$$

$$\frac{(V_n - 0) - 50}{50} + \frac{(V_n - 0)}{50} +$$

$$\frac{(V_n - V_Hn)}{2} = 0$$

$$\frac{V_n}{50} - 1 + \frac{V_n}{50} + \frac{V_n}{2} - \frac{V_Hn}{2} = 0$$

$$7V_n - 5V_Hn = 50 \quad \textcircled{1}$$



Solving eq $\textcircled{1}$ and \textcircled{ii} ,


$$7V_n - 5V_Hn = 50$$

$$-3V_n + 5V_Hn = 0$$


$$4V_n = 50$$

$$V_n = \frac{50}{4} = 2.5V$$

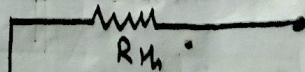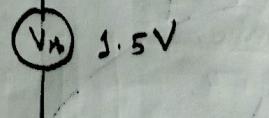 $V_Hn = 1.5V$ 

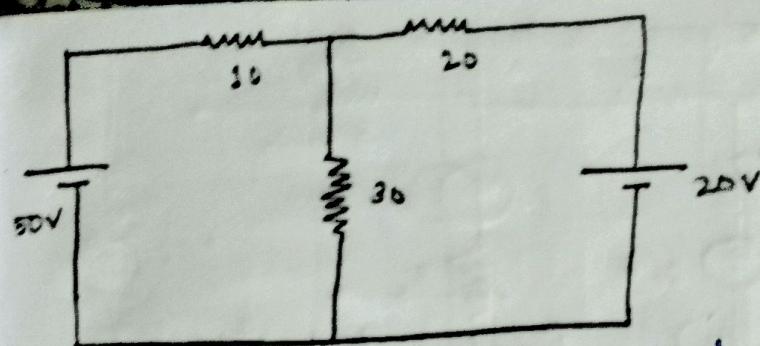

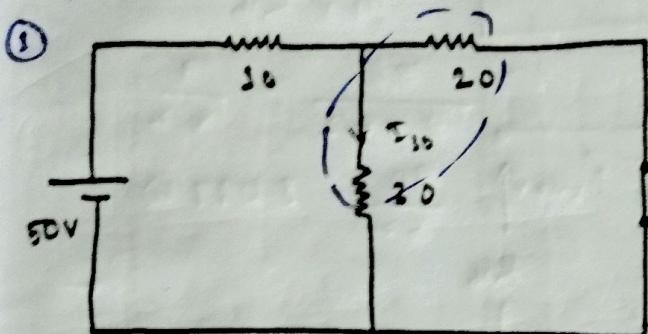Step-I: Consider 50V source, short-circuiting 20V source.





$$V = 50V; R_{eq} = 22\Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{50}{22} = 2.27A$$
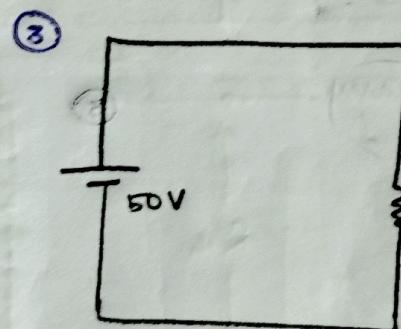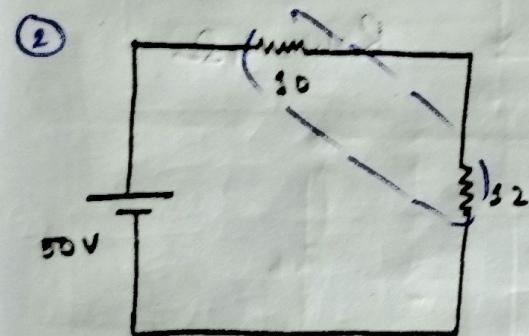
$$I_{30} = 2.27 \times \frac{20}{50} = 0.908A$$



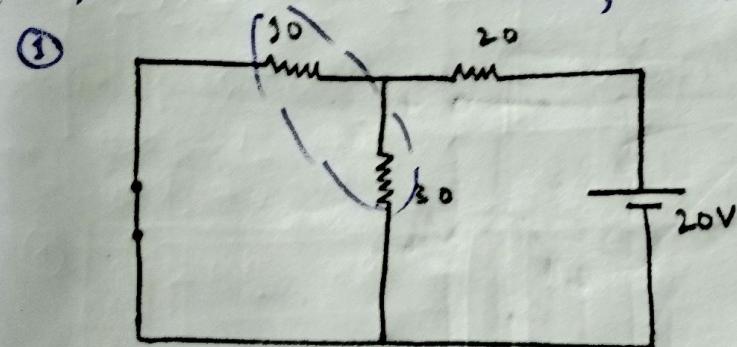Step-II: Consider 20V source, short-circuiting 50V source.





$$V = 20V; R_{eq} = 27.5\Omega$$

$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{20}{27.5} = 0.72A$$

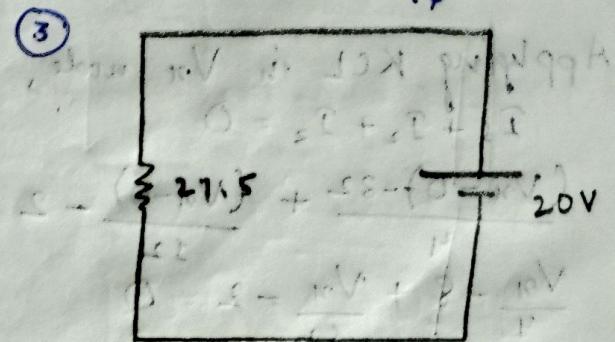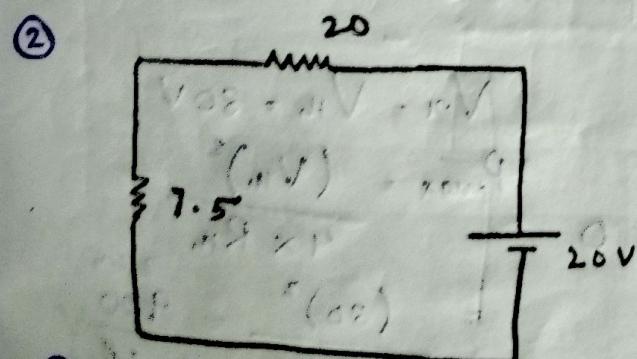
$$I_{30} = 0.72 \times \frac{30}{40} = 0.58A$$



$$\begin{aligned} I_{Total(30)} &= I_{30}(50V) + I_{30}(20V) \\ &= 0.908 + 0.58 \\ &= 1.488A \end{aligned}$$


H.W (4)

Q)

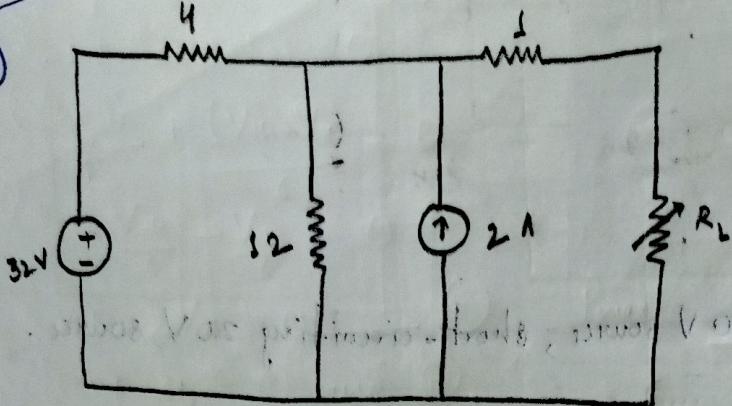


R_m

(1)

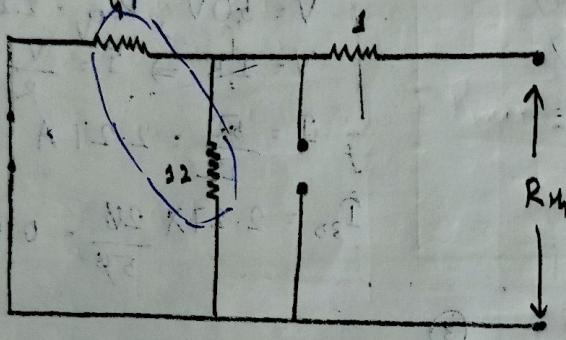


$$R_m = 4 \Omega$$


(2)

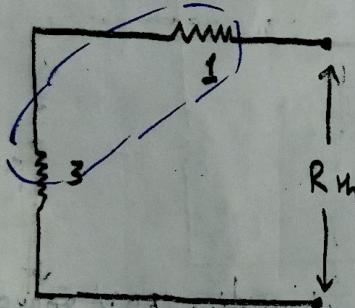

(3)

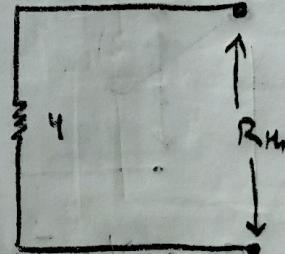

V_m

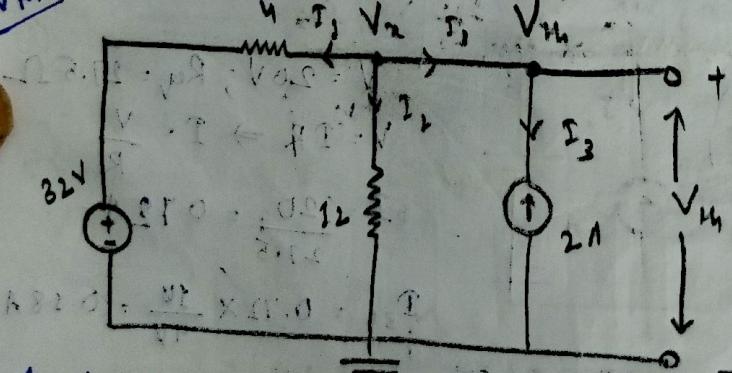

Applying KCL in V_m node,
 $I_1 + I_2 + I_3 = 0$

$$\frac{(V_m - 0)}{4} + \frac{(V_m - 0)}{12} - 2 = 0$$

$$\frac{V_m}{4} - 8 + \frac{V_m}{12} - 2 = 0$$





$$\frac{4V_m}{12} = 10 \Rightarrow 4V_m = 120 \quad (1) \quad + (V_m) \cdot \frac{4 \times 4}{4 \times 4 - (12)} \quad (2)$$

$$V_m = \frac{120}{4} = 30V$$

$$V_m = V_m = 30V$$

$$P_{max} = \frac{(V_m)^2}{4 \times R_m}$$
$$= \frac{(30)^2}{4 \times 4} = \frac{225}{16} = 14.0625W$$

$$14.0625W$$

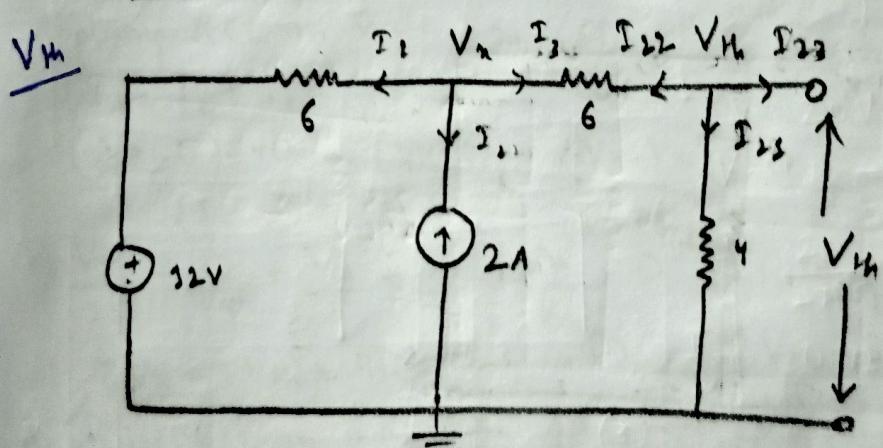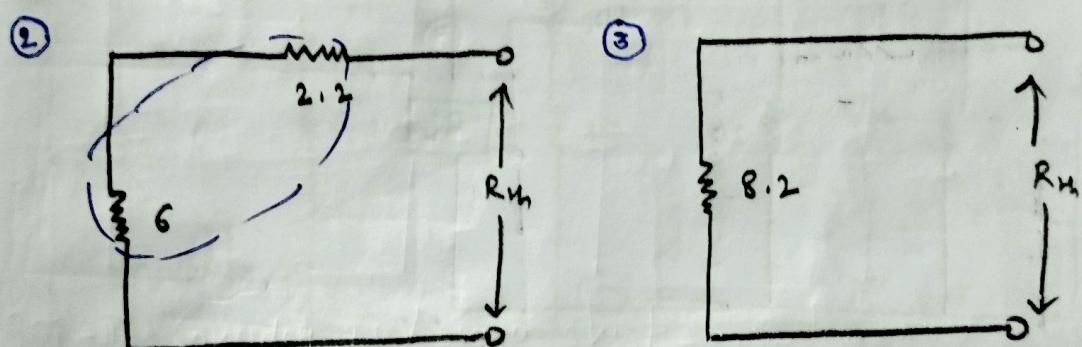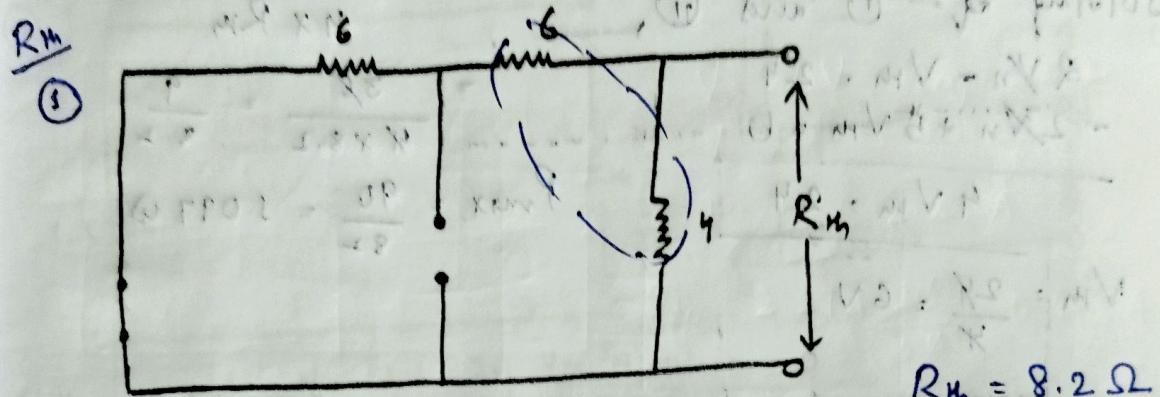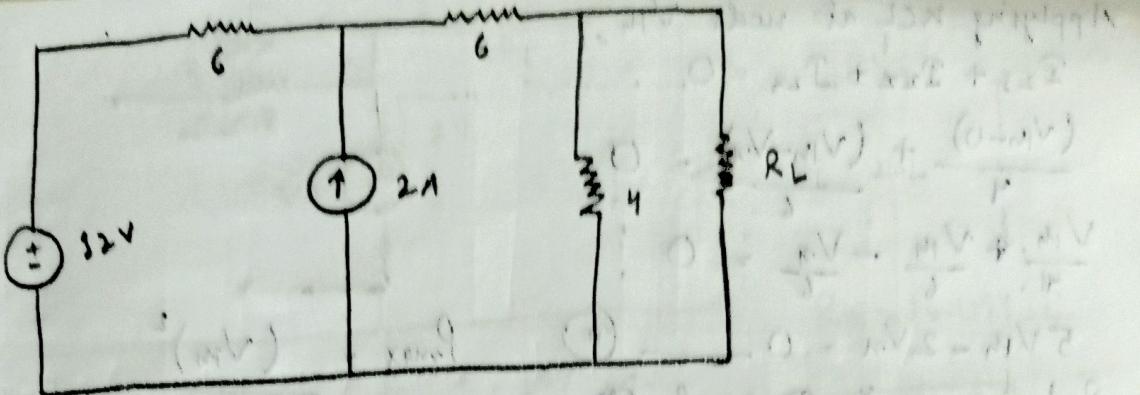

Applying KCL at node V_N ,

$$I_1 + I_2 + I_3 = 0$$

$$\frac{(V_N - 0)}{6} - 32 - 2 + \frac{(V_N - V_H)}{6} = 0$$

$$\frac{V_N}{6} - 2 - 2 + \frac{V_N}{6} - \frac{V_H}{6} = 0$$

$$\frac{2V_N - V_H}{6} = 0 \quad \text{--- (1)}$$

Applying KCL at node V_M ,

$$I_{21} + I_{22} + I_{23} = 0$$

$$\frac{(V_M - 0)}{4} + \frac{(V_M - V_x)}{6} = 0$$


$$\frac{V_M}{4} + \frac{V_M}{6} - \frac{V_x}{6} = 0$$

$$5V_M - 2V_x = 0 \quad \textcircled{1}$$

Solving eq $\textcircled{1}$ and $\textcircled{11}$,

$$\begin{aligned} 2V_x - V_M &= 24 \\ -2V_x + 5V_M &= 0 \\ \hline 4V_M &= 24 \end{aligned}$$


$$V_M = \frac{24}{4} = 6V$$

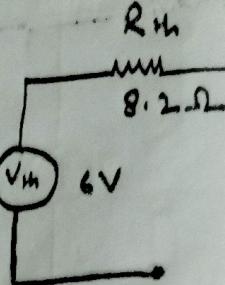

$$P_{\max} = \frac{(V_M)^2}{4 \times R_M}$$


$$= \frac{36}{4 \times 8.2} = \frac{9}{8.2}$$
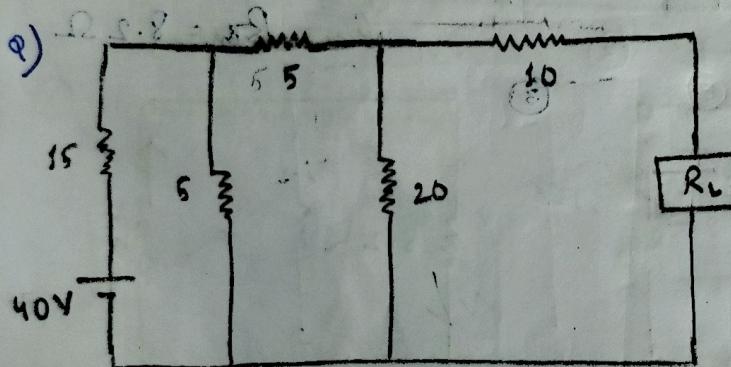
$$P_{\max} = \frac{90}{82} = 1.097 \text{ W}$$





R_M

①



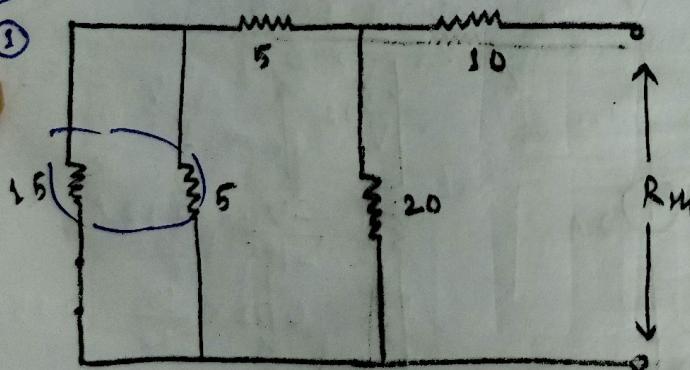


②

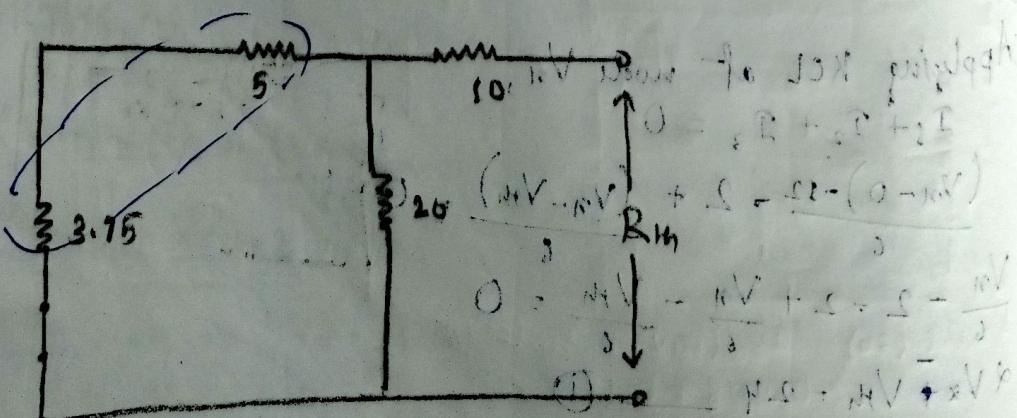

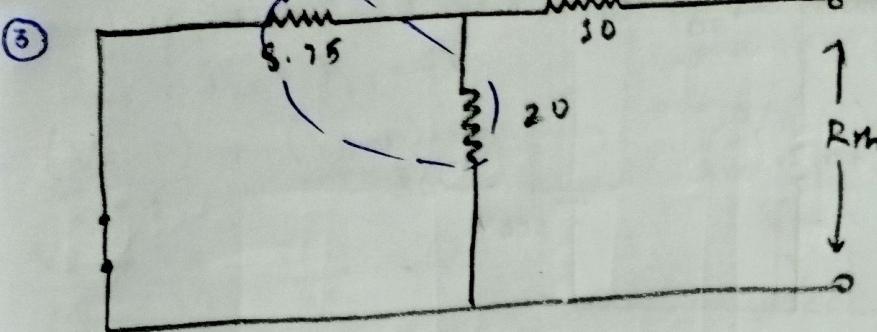

$$R_m = 16.097 \Omega$$

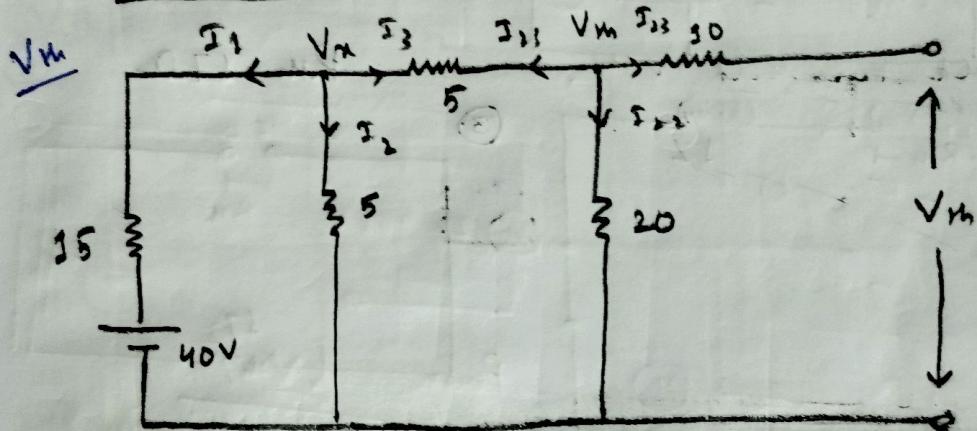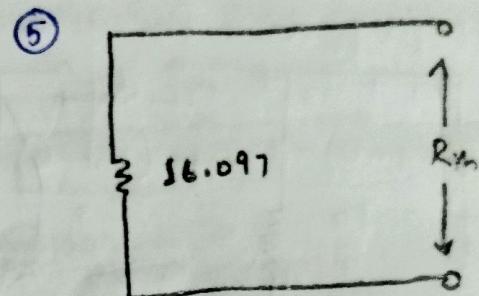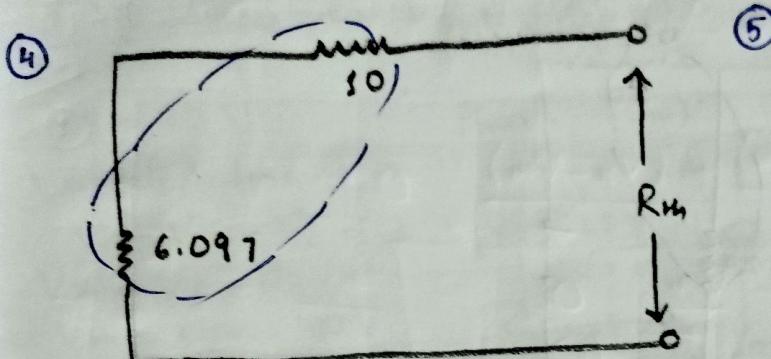

Applying KCL in node V_x ,

$$I_3 + I_2 + I_1 = 0$$

$$\frac{(V_x - 0) - 40}{15} + \frac{(V_x - 0)}{5} + \frac{(V_x - V_m)}{5} = 0$$

$$\frac{V_x}{15} - \frac{40}{15} + \frac{V_x}{5} + \frac{V_x}{5} - \frac{V_m}{5} = 0$$

$$7V_x - 3V_m = 40$$

Putting eq. ⑪ in ①,

$$7V_m - 3V_m = 40$$

$$4V_m = 40$$

$$V_m = \frac{40}{4} = 10V$$

Applying KCL in node V_{H_m} ,


$$I_{23} + I_{22} + I_{21} = 0$$

$$\frac{(V_m - V_x)}{5} + \frac{(V_m - 0)}{20} = 0$$

$$\frac{V_m}{5} - \frac{V_x}{5} + \frac{V_m}{20} = 0$$




$$V_m - V_x = 0$$

$$V_m = V_x \quad \text{--- ⑪}$$


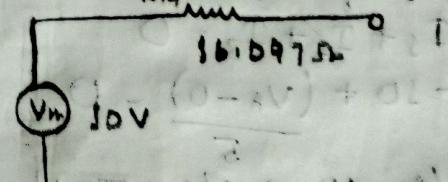


$$P_{max} = \frac{(V_m)^2}{4 \times R_m} = \frac{100}{4 \times 16.097}$$

$$P_{max} = 1.553 W$$

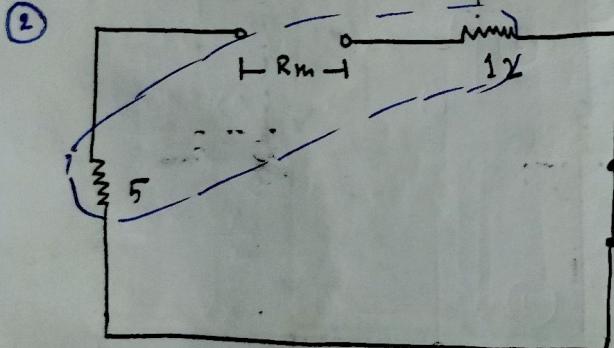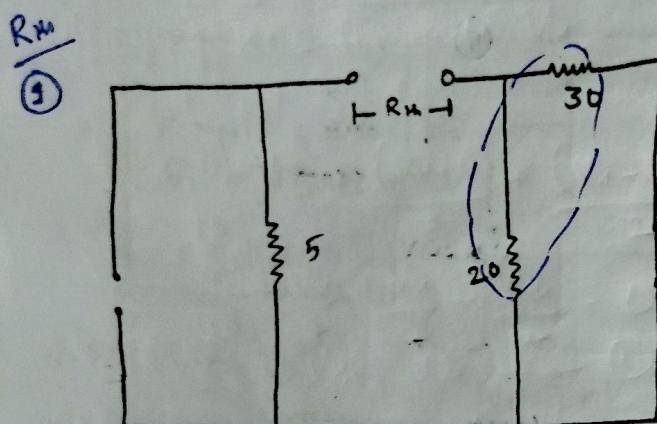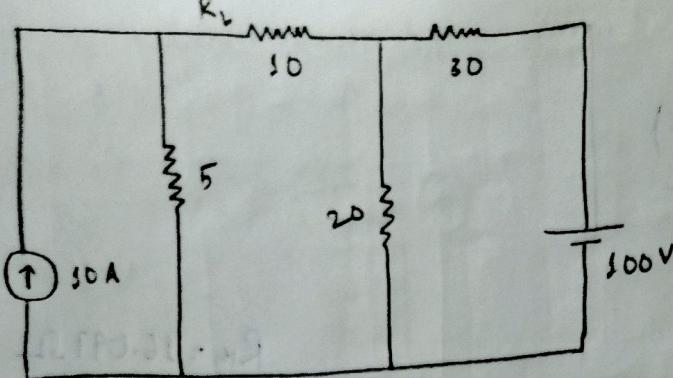

$$R_{th} = 57\Omega$$

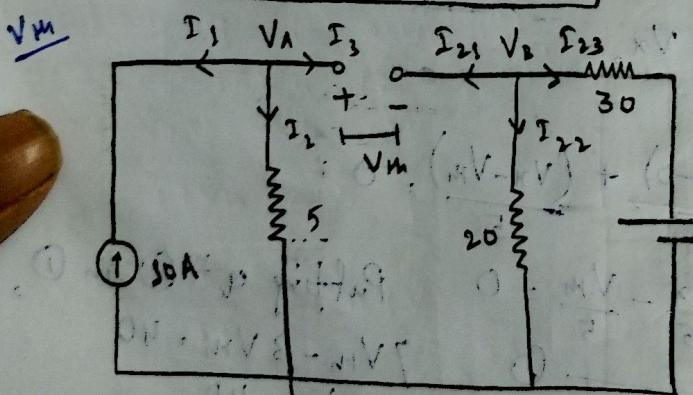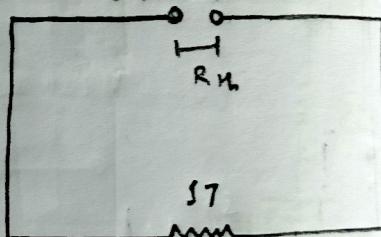

Applying KCL for node V_A

$$T_1 + T_2 + T_3 = 0$$

$$-50 + (V_A - 0) = 0$$

$$\underline{V_A} = 10 \Rightarrow V_A = 50V$$

Applying KCL for node V_B ,

$$I_{21} + I_{23} + I_{32} = 0$$

$$\frac{(V_B - 0)}{20} + \frac{(V_B - 0) - 50V}{30} = 0$$

$$\frac{V_B}{20} + \frac{V_B}{30} - \frac{500}{80} = 0$$

$$\frac{5V_B}{60} + \frac{500}{80} \Rightarrow V_B = \frac{500}{80} \times \frac{60}{5}$$

$$V_B = 40V$$

V_M calculation :-

$$V_A - V_M - V_B = 0$$

$$V_M = V_A - V_B$$

$$V_M = 50V - 40V$$

$$V_M = 10V$$

$$P_{max} = \frac{(V_M)^2}{4 \times R_M}$$

$$= \frac{100}{4 \times 57}$$

$$= 5.47W$$

V_M calculation :-
(Second node V_B)

$$V_B + V_M - V_A = 0$$

$$V_M = V_A - V_B$$

$$V_M = 50V - 40V$$


$$V_M = 10V$$

R_M


17Ω

V_M 10V


Q)

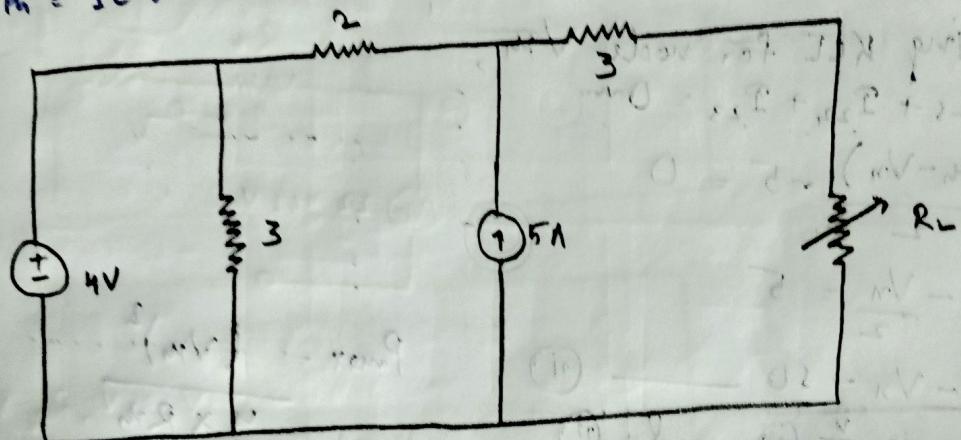


$\frac{R_M}{R_L}$

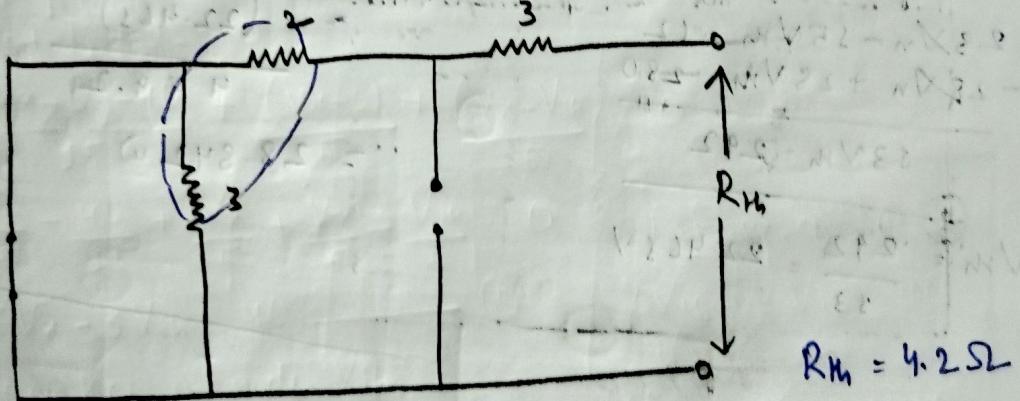


②

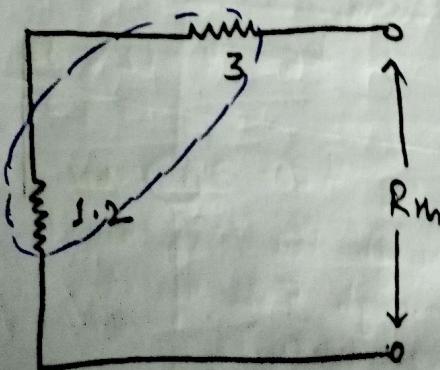

③

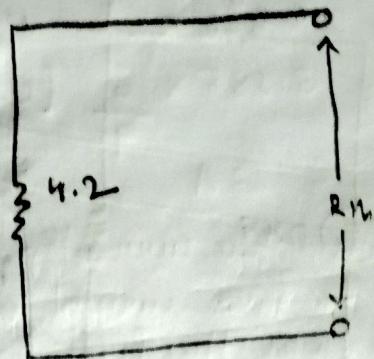

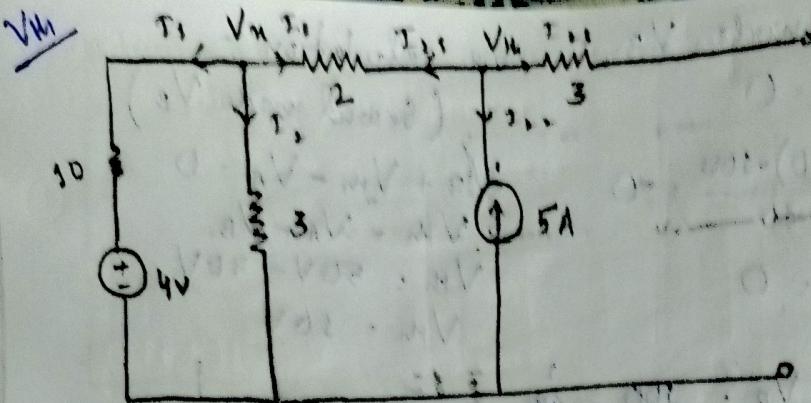

Applying KCL for node V_x ,

$$I_3 + I_2 + I_1 = 0$$

$$\frac{(V_x - 0) - 4}{10} + \frac{(V_m - 0)}{3} + \frac{(V_x - V_m)}{2} = 0$$

$$\frac{V_x}{10} - \frac{4}{10} + \frac{V_x}{3} + \frac{V_x}{2} - \frac{V_m}{2} = 0$$

$$28V_x - 55V_m + 52 = 0 \quad (1)$$

Applying KCL for node V_m ,

$$I_{23} + I_{22} + I_{21} = 0$$

$$\frac{(V_m - V_x)}{2} - 5 = 0$$

$$\frac{V_m}{2} - \frac{V_x}{2} = 5$$

$$V_m - V_x = 10 \quad (2)$$


Solving eq $\frac{1}{(1)}$ and (2) ,

$$28V_m - 55V_m = 52$$

$$-28V_m + 28V_m = 280$$


$$53V_m = 292$$
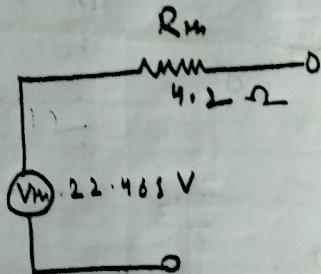
$$V_m = \frac{292}{53} = 22.465 \text{ V}$$




$$\begin{aligned} P_{\max} &= \frac{(V_m)^2}{4 \times R_{11}} \\ &= \frac{(22.465)^2}{4 \times 4.2} \\ &= 28.842 \text{ W} \end{aligned}$$

Q)

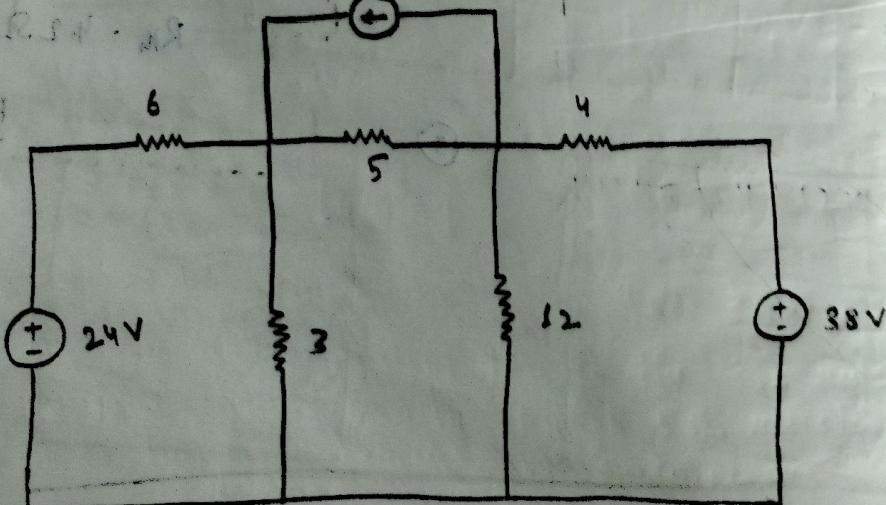


Considering 24V source, open-circuiting 4A source, and short-circuiting 88V.


①

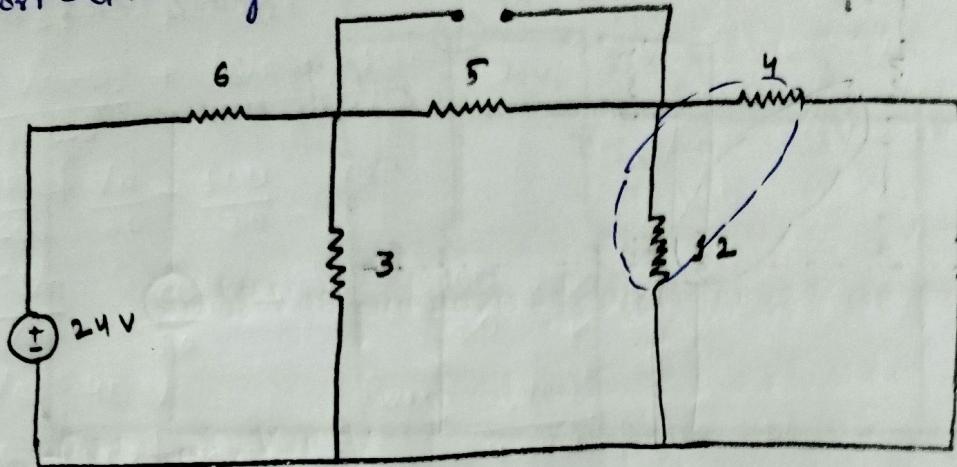

②

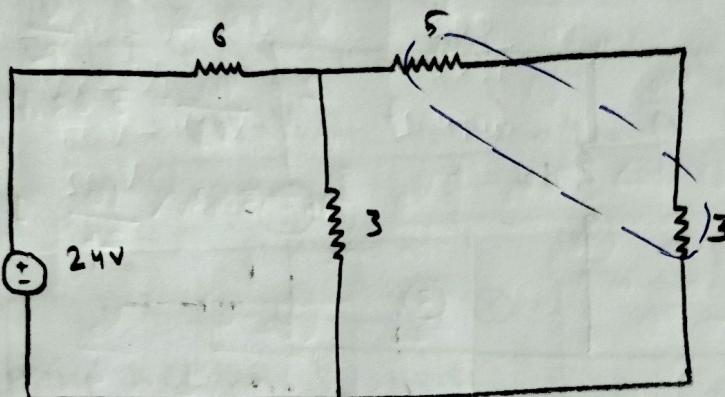

③

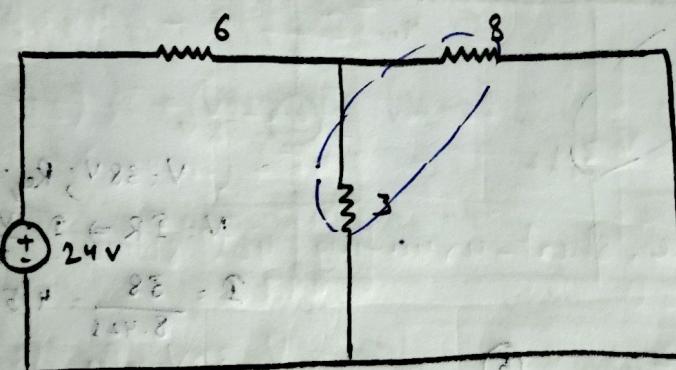


$$V = 24V; R_{eq} = 8.58\Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{24}{8.58} = 2.93A$$

④

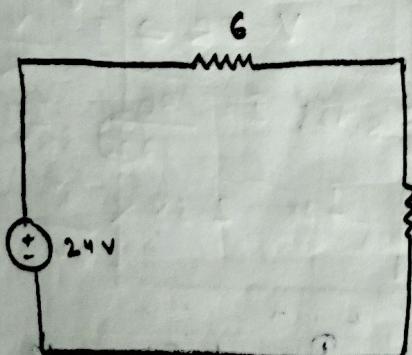

⑤

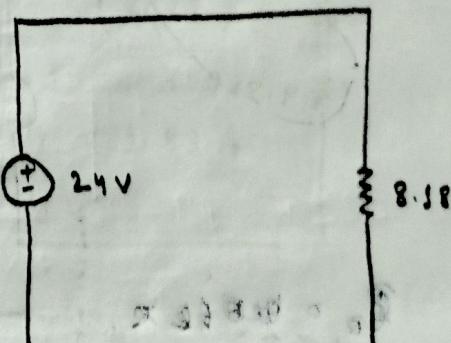


$$I_3 = 2.93 * \frac{5}{8} \quad [Current-Division Rule]$$

$$I_3 = 1.83325A$$


[I_3 = Current flowing through 3Ω resistor] with current flowing from left to right of bolt

Considering 38V source, open-circuiting 4A source and short circuiting 24V source.

①

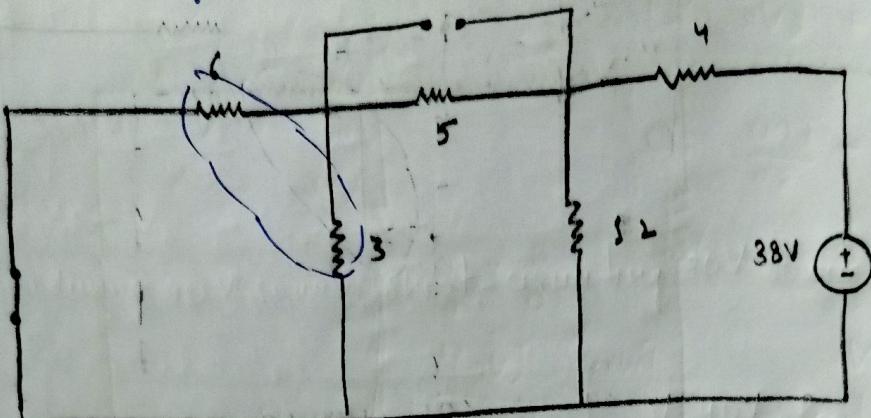


②

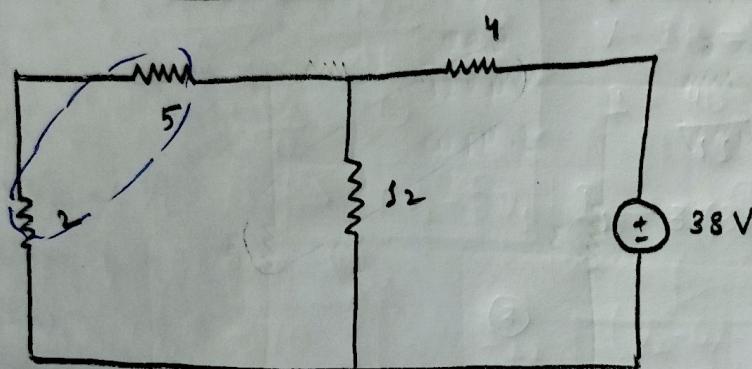


③


~~Δ 8.425~~

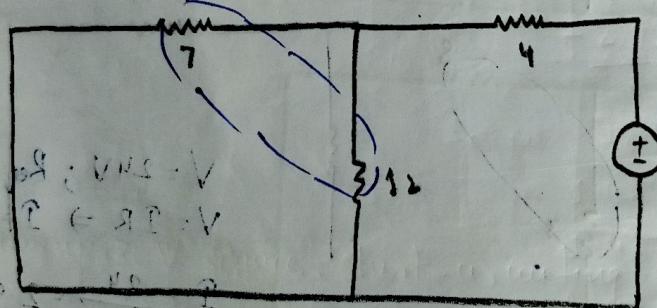

④

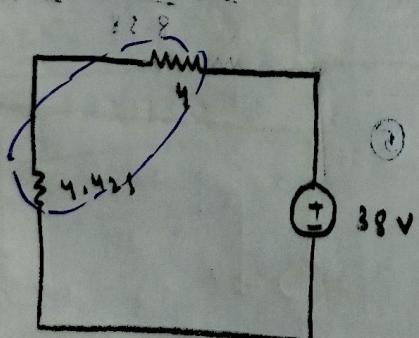

⑤

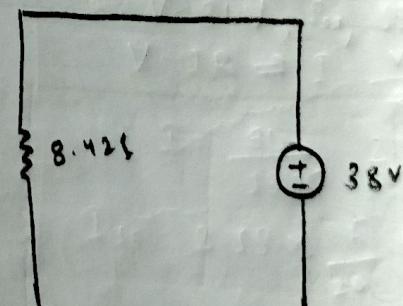

$$R_{eq} = 8.425 \Omega$$

$$I_3 = 3.585 \times \frac{6}{9} [C, D, R]$$


$$I_3 = 2.523 A$$

$$I_5 = 4.552 \times \frac{32}{57}$$

$$I_5 = 3.585 A$$

* Found the current passing through the 8Ω resistor.
Had to find current passing through 5Ω resistor because that was the first branch from source.

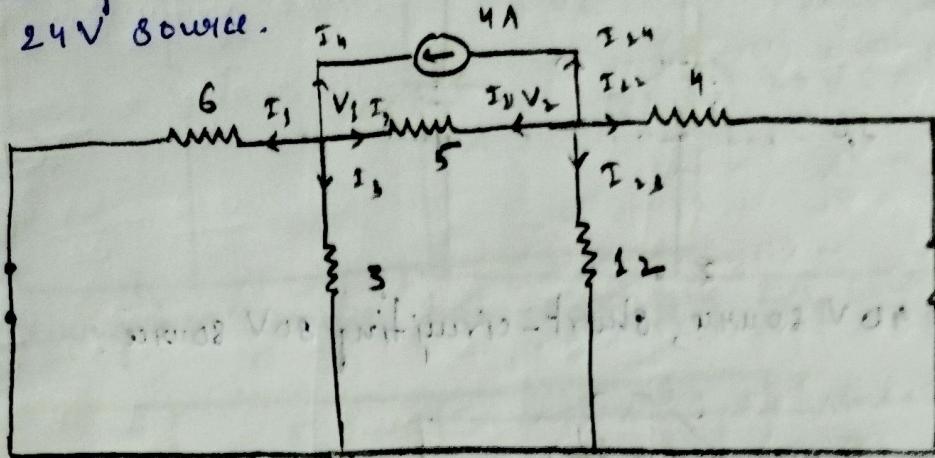Considering the 4A source and short-circuiting the 38V and 24V source.



Applying KCL in V_3 node,

$$I_3 + I_2 + I_3 + I_4 = 0$$

$$\frac{(V_3 - 0)}{6} + \frac{(V_3 - V_2)}{5} + \frac{(V_3 - 0)}{3} - 4 = 0$$

$$\frac{V_3}{6} + \frac{V_3}{5} - \frac{V_2}{5} + \frac{V_3}{3} = 4$$

$$7V_3 - 2V_2 = 40 \quad \textcircled{1}$$

Applying KCL in V_2 node,

$$I_{23} + I_{22} + I_{23} + I_{24} = 0$$

$$\frac{(V_2 - V_3)}{5} + \frac{(V_2 - 0)}{4} + \frac{(V_2 - 0)}{12} + 4 = 0$$

$$\frac{V_2}{5} - \frac{V_3}{5} + \frac{V_2}{4} + \frac{V_2}{12} = -4$$

$$8V_2 - 3V_3 = -60 \quad \textcircled{11}$$

Solving eq's $\textcircled{1}$ and $\textcircled{11}$,

$$28V_3 - 8V_2 = 360$$

$$-3V_3 + 8V_2 = -60$$

$$25V_3 = 300$$

$$V_3 = \frac{300}{25} = 4V$$


Thus,

$$\begin{aligned} I_3 (\text{Total}) &= I_3 (24V) + I_3 (38V) + I_3 (4A) \\ &= 3.83 \times 25 + 2.523 + 5.33 \\ &= 5.28425 A \end{aligned}$$


Now,

$$I_3 = \frac{(V_3 - 0)}{3} = \frac{V_3}{3}$$

$$I_3 = \frac{4}{3} = 1.33 A$$

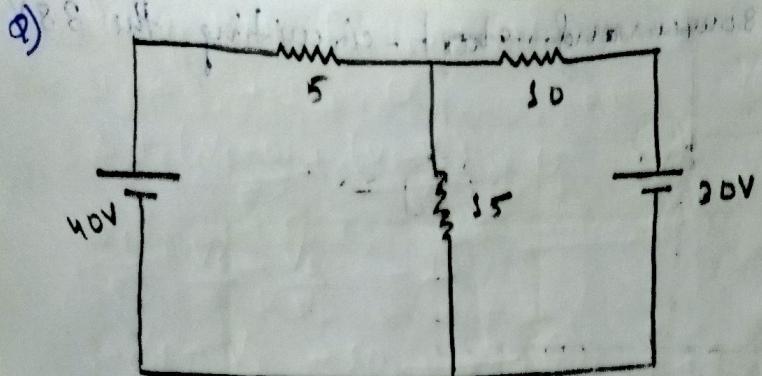

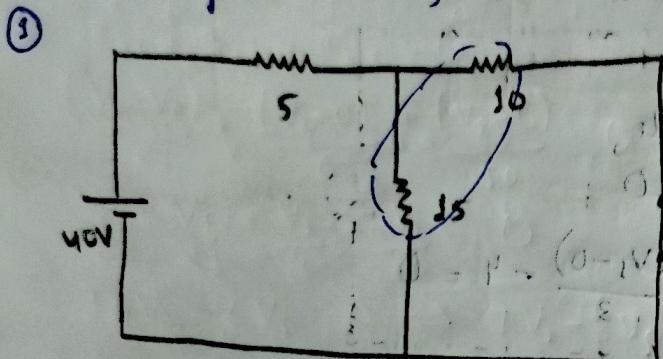Considering 40V source, short-circuiting 30V source.





$$V = 40V; R_{eq} = 5\Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{40}{5} = 8A$$
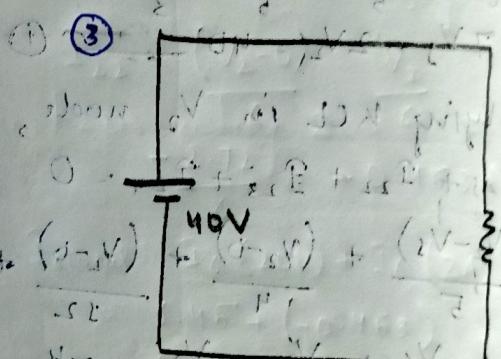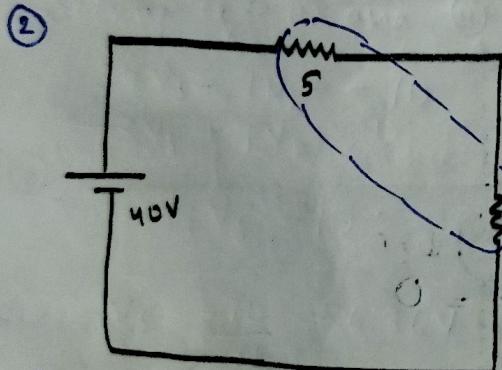
$$I_{35} = 8A \times \frac{10}{25} = 3.2A$$



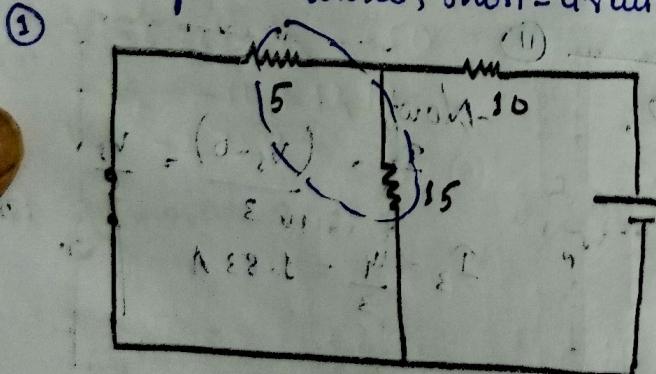Considering 30V source, short-circuiting 40V source.





$$V = 30V; R_{eq} = 5\Omega$$


$$V = IR \Rightarrow I = \frac{V}{R}$$

$$30V \quad I = \frac{30}{5} = 6A$$


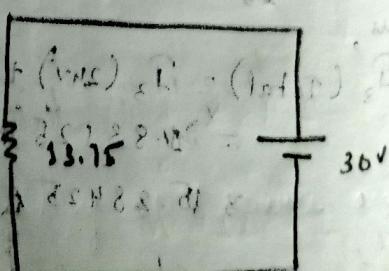
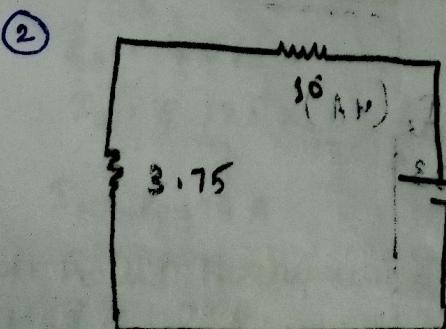
$$I_{35} = 6A \times \frac{5}{25} = 1.2A$$



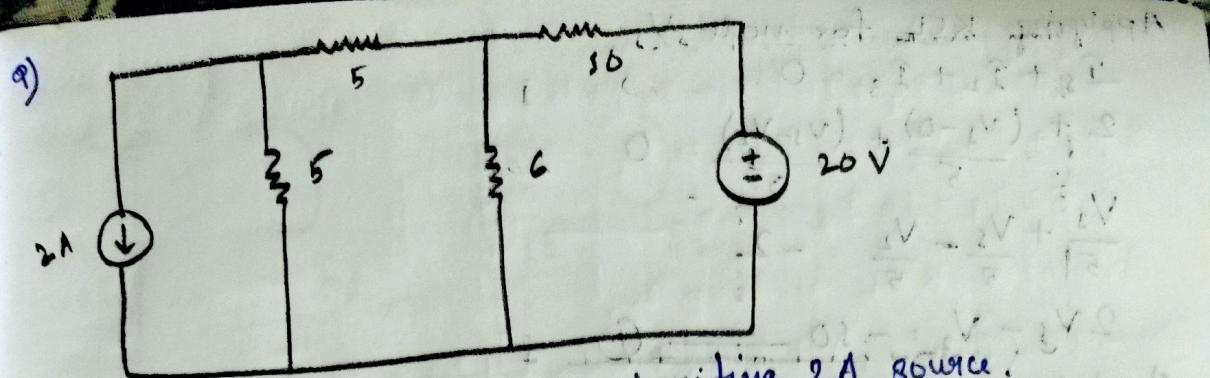
$$I_{35} (\text{Total}) = I_{35} (40V) + I_{35} (30V) = 1.452 + 0.545 = 1.997A$$



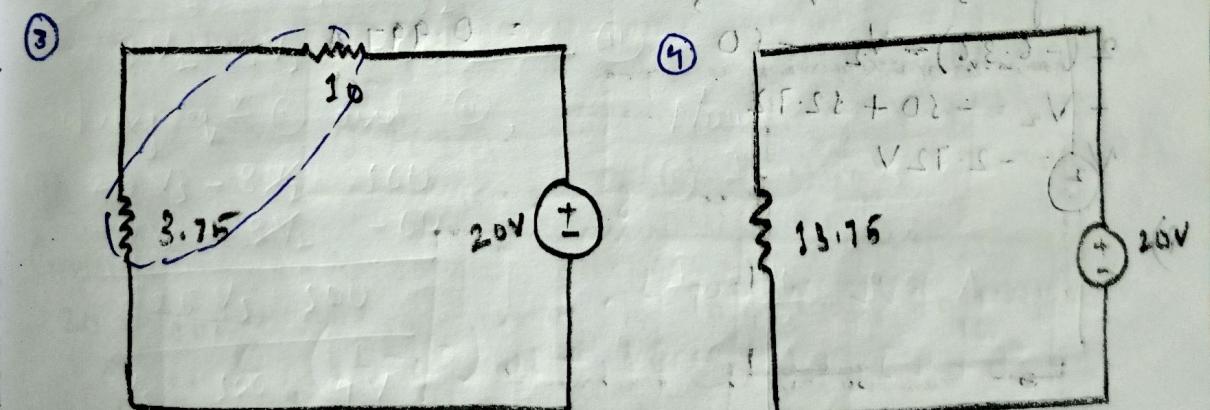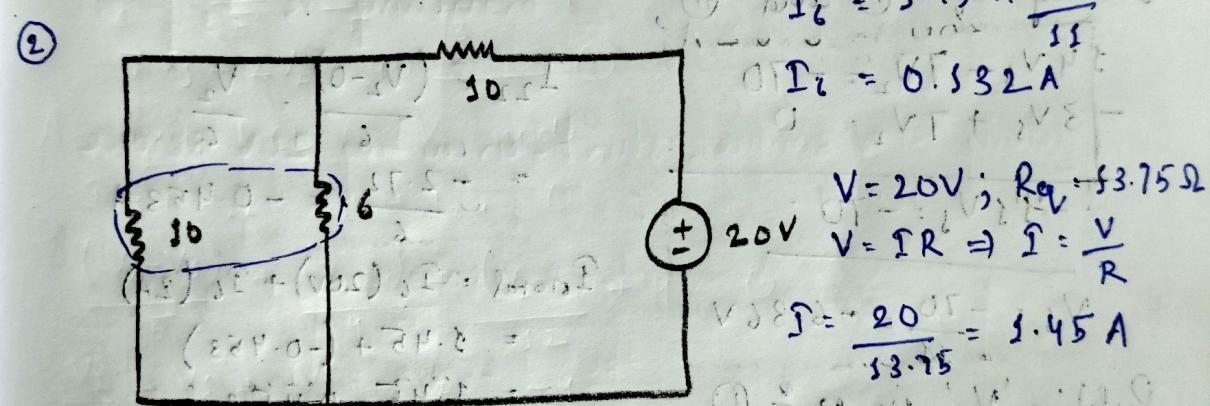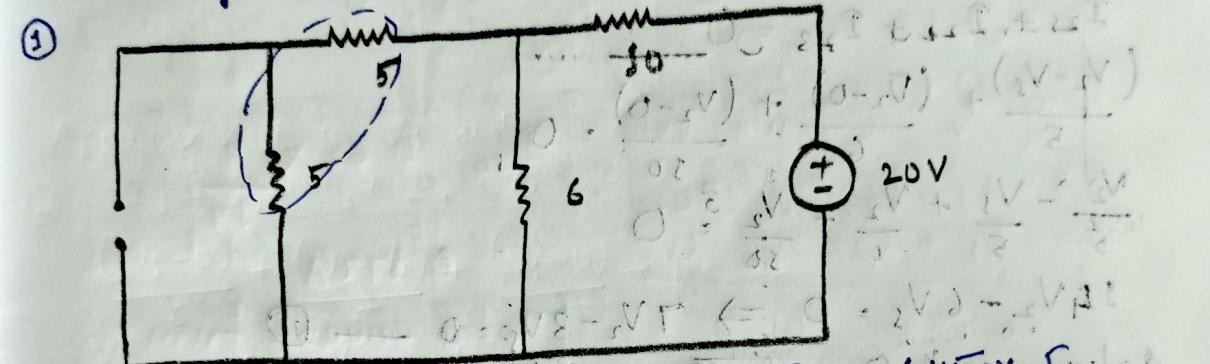Considering 20V source, open-circuiting 2A source.



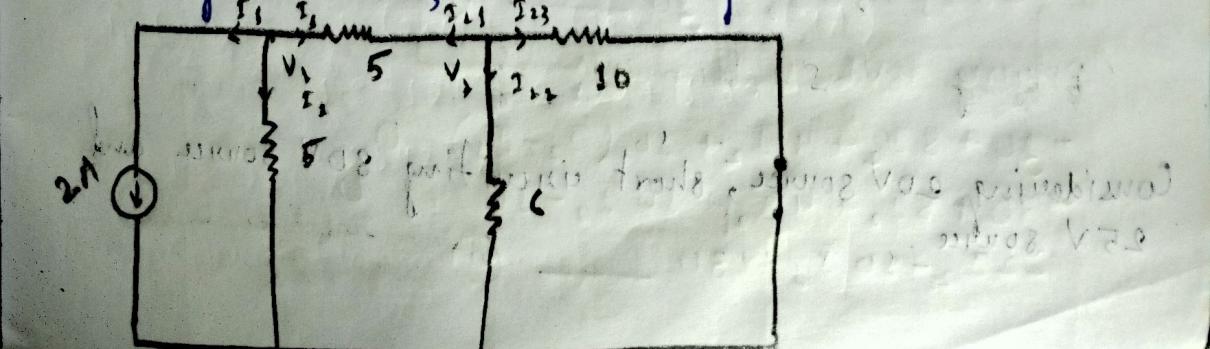Considering 2A source, short-circuiting 20V source.



Applying KCL for node V_3 ,

$$I_1 + I_2 + I_3 = 0$$

$$2 + \frac{(V_3 - 0)}{5} + \frac{(V_3 - V_2)}{5} = 0$$

$$\frac{V_3}{5} + \frac{V_3}{5} - \frac{V_2}{5} = -2$$

$$2V_3 - V_2 = -50 \quad \text{--- } ①$$

Applying KCL for node V_2 ,

$$I_{21} + I_{22} + I_{23} = 0$$

$$\left(\frac{V_2 - V_3}{5}\right) + \left(\frac{V_2 - 0}{6}\right) + \left(\frac{V_2 - 0}{50}\right) = 0$$

$$\frac{V_2}{5} - \frac{V_3}{5} + \frac{V_2}{6} + \frac{V_2}{50} = 0$$

$$14V_2 - 6V_3 = 0 \Rightarrow 7V_2 - 3V_3 = 0 \quad \text{--- } ⑪$$

Solving eq $\cong ①$ and $⑪$,

$$\begin{aligned} 14V_3 - 7V_2 &= -70 \\ -3V_3 + 7V_2 &= 0 \end{aligned}$$

$$\underline{\underline{35V_3 = -70}}$$

$$V_3 = \frac{-70}{35} = -2 \cdot 72 \text{ V}$$

Putting ' V_3 ' in eq $\cong ①$,

$$2(-2.72) - V_2 = -50$$


$$-V_2 = -50 + 5.44$$

$$V_2 = -2.72 \text{ V}$$


$$\begin{aligned} I_{22} &= \frac{(V_2 - 0)}{6} = \frac{V_2}{6} \\ &= \frac{-2.72}{6} = -0.453 \text{ A} \end{aligned}$$

$$\begin{aligned} I_{\text{total}} &= I_6(20V) + I_6(2A) \\ &= 1.45 + (-0.453) \\ &= 1.45 - 0.453 \\ &= 0.997 \text{ A} \end{aligned}$$

(a)

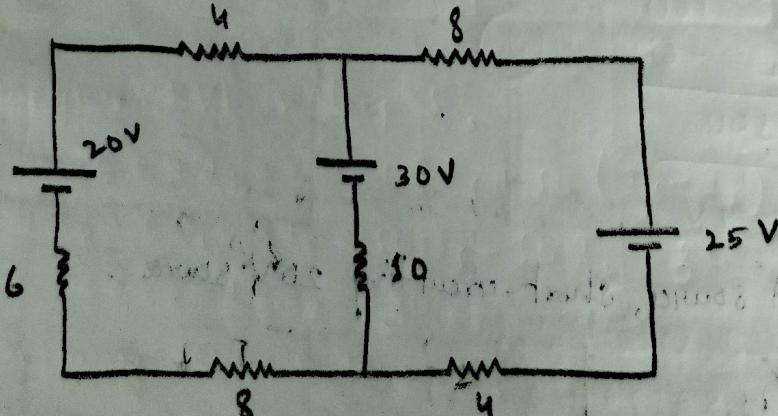

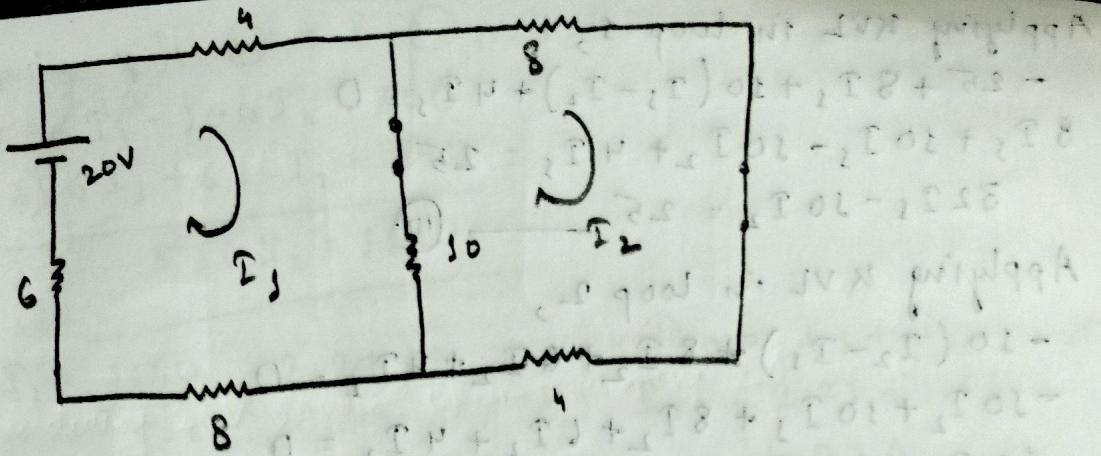Considering 20V source, short circuiting 30V source and 25V source.



Applying KVL in loop 1,

$$-20 + 4I_3 + 50(I_3 - I_2) + 8I_3 + 6I_3 = 0$$

$$4I_3 + 50I_3 - 50I_2 + 8I_3 + 6I_3 = 20$$

$$28I_3 - 50I_2 = 20$$

$$14I_3 - 25I_2 = 10 \quad \text{--- (1)}$$

Applying KVL in loop 2,

$$-8I_2 + 4I_2 + 50(I_2 - I_3) = 0$$

$$-8I_2 + 4I_2 + 50I_2 - 50I_3 = 0$$

$$6I_2 - 50I_3 = 0 \quad \text{--- (2)}$$

Solving eq 1 and 2,

$$84I_3 - 30I_2 = 60$$

$$-50I_3 + 30I_2 = 0$$

$$\underline{34I_3 = 60}$$


$$I_3 = \frac{60}{34} = 1.764 \text{ A}$$

$$I_{50} = 1.764 \times \frac{8}{58}$$

$$= 0.784 \text{ A}$$

I_3 = Total current from source of 20V getting divided into 50Ω and 8Ω resistor.

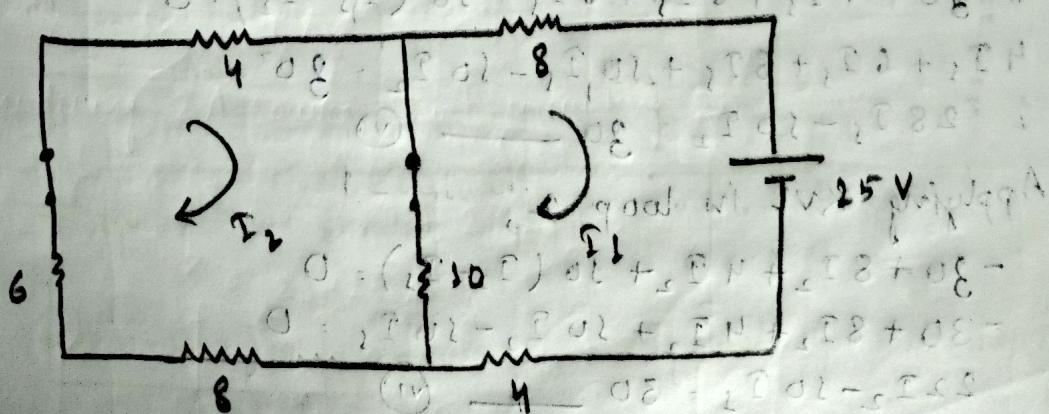Considering 25V source, short circuiting 30V and 20V source. [Again we've to take loops for KVL].



Applying KVL in loop 3,

$$-25 + 8I_3 + 50(I_3 - I_2) + 4I_3 = 0$$

$$8I_3 + 50I_3 - 50I_2 + 4I_3 = 25$$

$$32I_3 - 50I_2 = 25 \quad \text{--- (III)}$$

Applying KVL in loop 2,

$$-50(I_2 - I_3) + 8I_2 + 6I_2 + 4I_2 = 0$$

$$-50I_2 + 50I_3 + 8I_2 + 6I_2 + 4I_2 = 0$$

$$32I_2 + 50I_3 = 0 \quad \text{--- (IV)}$$

Solving eq $\frac{v}{=}$ (III) and (IV), $I_{30} = 0.62 \times \frac{4}{54}$

$$884I_3 - 520I_2 = 300$$


$$500I_3 + 520I_2 = 0$$

$$\underline{484I_3 = 300}$$

[Total current from branching is I_3]

$$I_3 = \frac{300}{484} = 0.62 \text{ A}$$

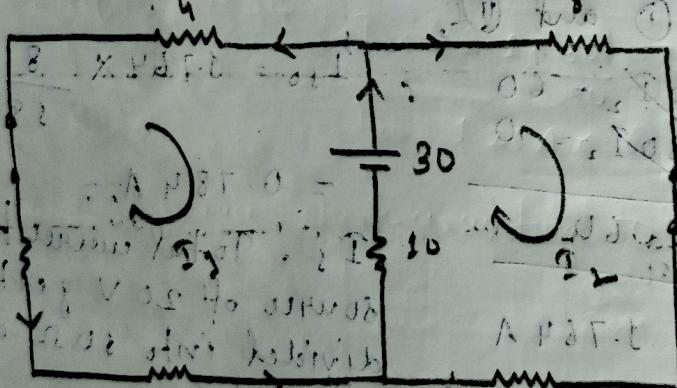Considering 80V source, short-circuiting 20V source and 25V source.



Applying KVL in loop 1,

$$-30 + 4I_3 + 6I_3 + 8I_3 + 50(I_3 - I_2) = 0$$

$$4I_3 + 6I_3 + 8I_3 + 50I_3 - 50I_2 = 30$$

$$28I_3 - 50I_2 = 30 \quad \text{--- (V)}$$

Applying KVL in loop 2,

$$-30 + 8I_2 + 4I_2 + 50(I_2 - I_3) = 0$$

$$-30 + 8I_2 + 4I_2 + 50I_2 - 50I_3 = 0$$

$$22I_2 - 50I_3 = 30 \quad \text{--- (VI)}$$

Solving eq $\textcircled{1}$ and $\textcircled{6}$,

$$\begin{aligned} 28I_3 - 500I_2 &= 800 \\ -286I_3 + 636I_2 &= 840 \\ \hline 536I_2 &= 5540 \end{aligned}$$

$$I_2 = \frac{5540}{536} = 2.25 \text{ A}$$

Putting ' I_2 ' in eq $\textcircled{1}$,

$$28I_3 - 50(2.25) = 80$$

$$28I_3 - 22.5 = 80$$

$$28I_3 = 52.5$$

$$I_3 = \frac{52.5}{28} = 1.86 \text{ A}$$

$$I_{\text{so}} = I_3 + I_2$$


$$I_{\text{so}} = 2.25 + 1.86 = 4.07 \text{ A}$$

$$I_{\text{so}} (\text{Total}) = I_{\text{so}} (20V) + I_{\text{so}} (25V) + I_{\text{so}} (30V)$$

$$I_{\text{so}} (\text{Total}) = 0.784 + 0.62 + 4.07$$


$$I_{\text{so}} (\text{Total}) = 5.474 \text{ A}$$

a)

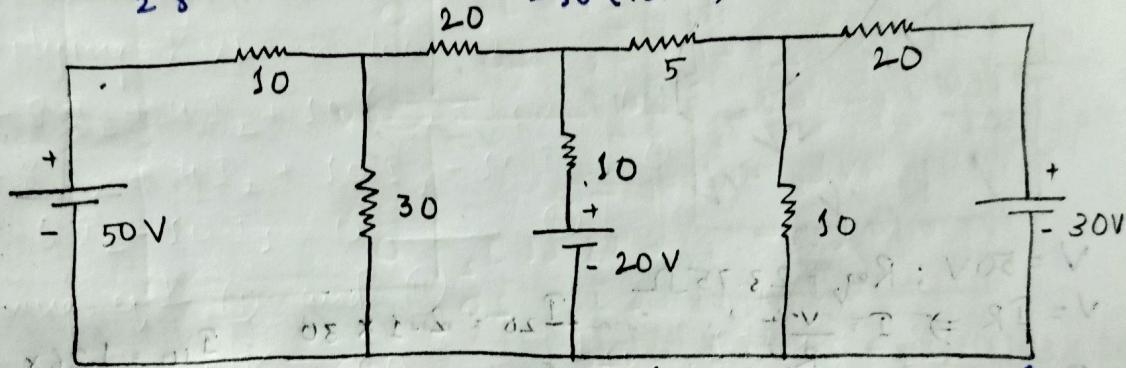







Considering 50V source, short-circuiting 20V source and 30V source.

①

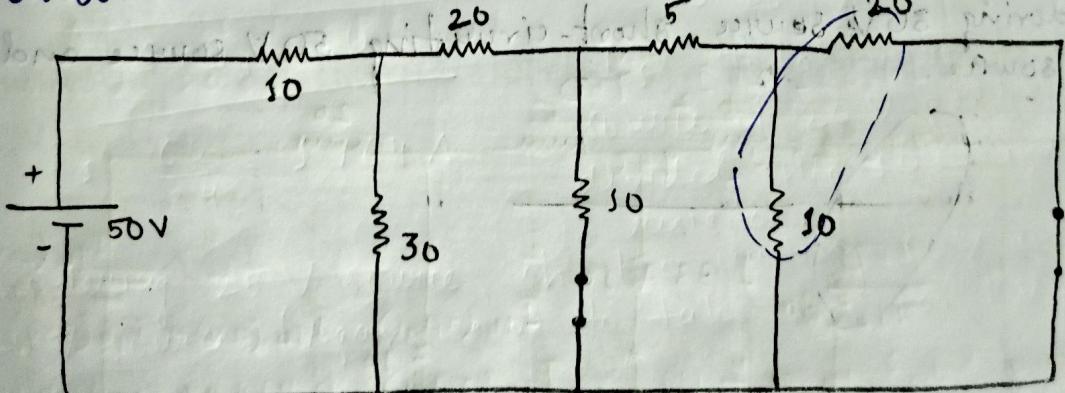

②

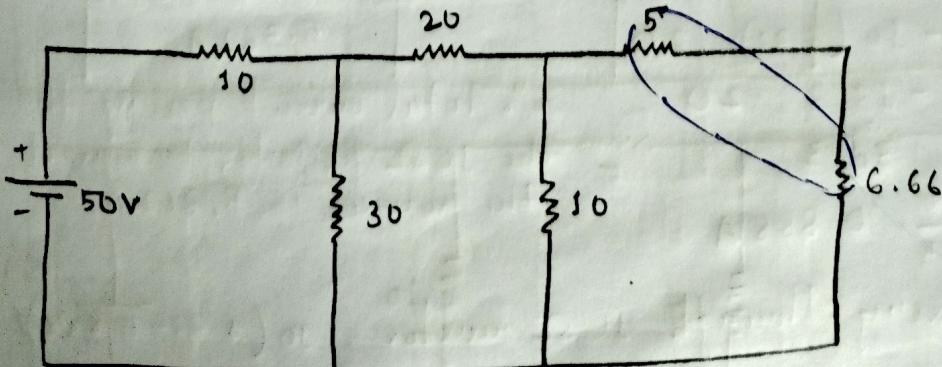

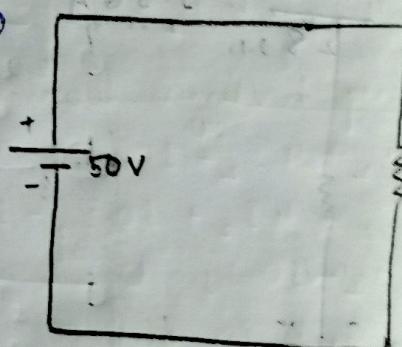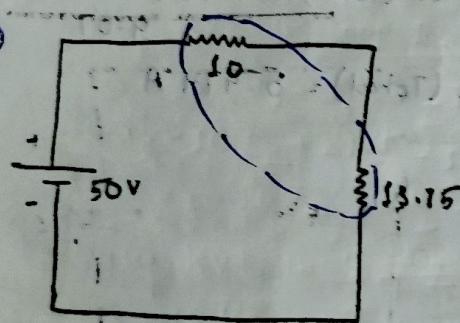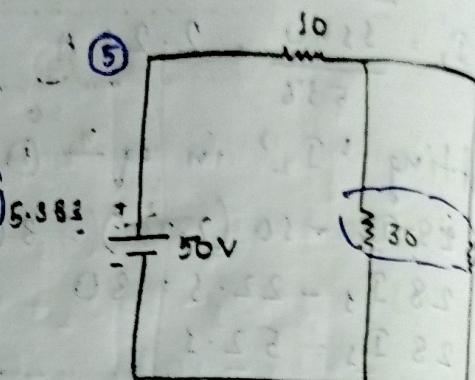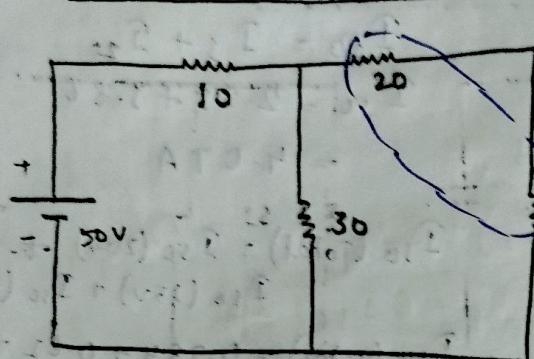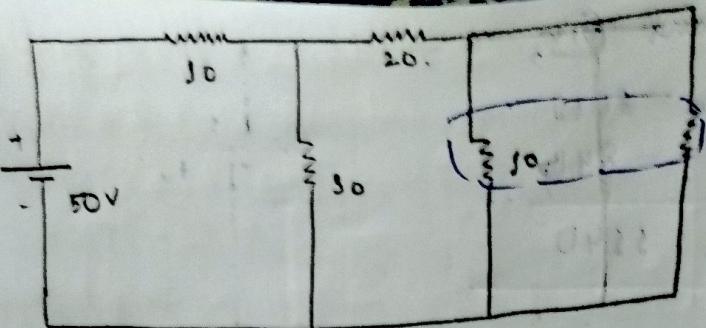

$$V = 50V; R_{eq} = 23.75\Omega$$

$$V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{50}{23.75} = 2.1A$$



$$I_{20} = 2.1 \times \frac{30}{50}$$

$$I_{20} = 1.26A$$


$$I_{30} = 3.26 \times \frac{8}{15}$$

$$I_{30} = 0.42A$$

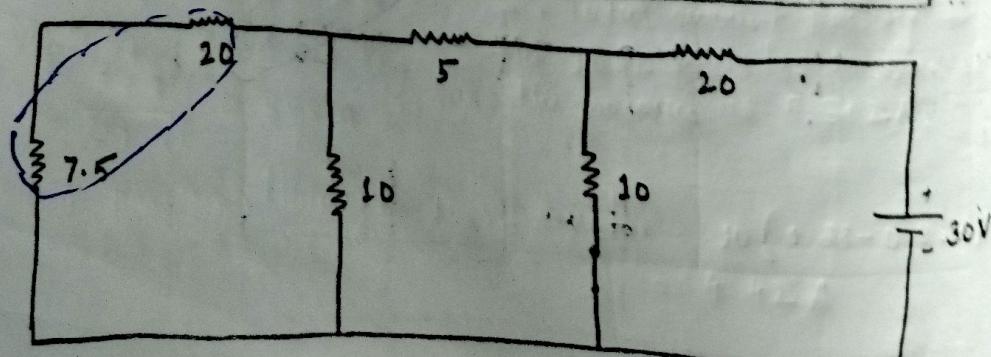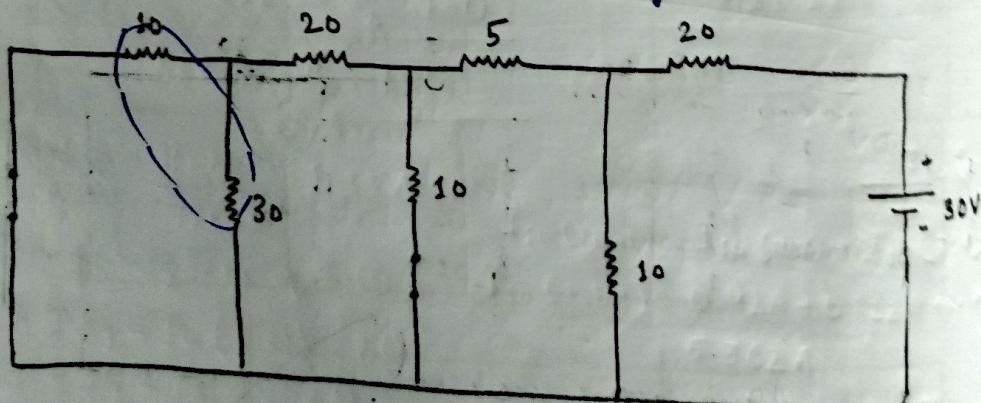
Considering 30V source, short-circuiting 50V source and 20V source.




③

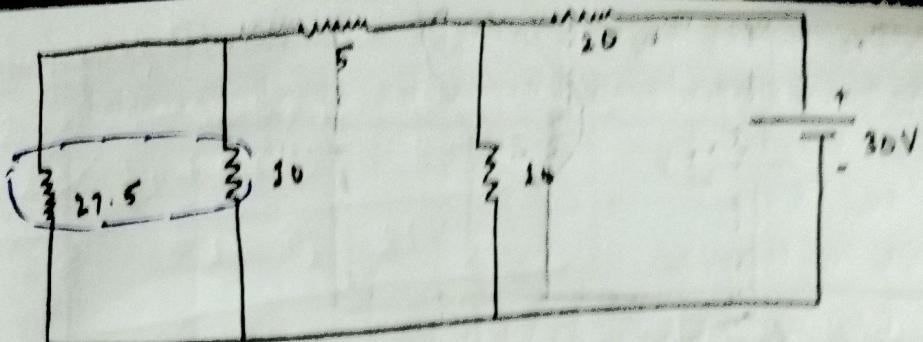


④

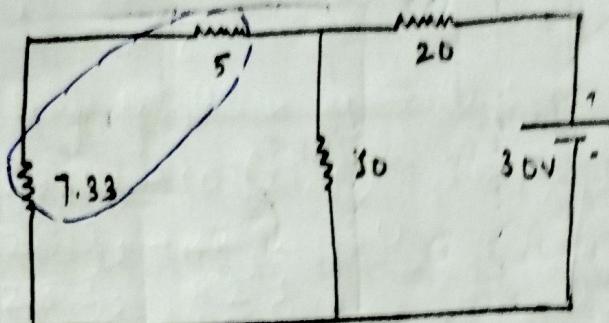


⑤

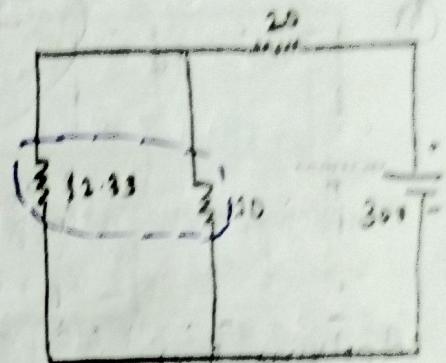

⑥

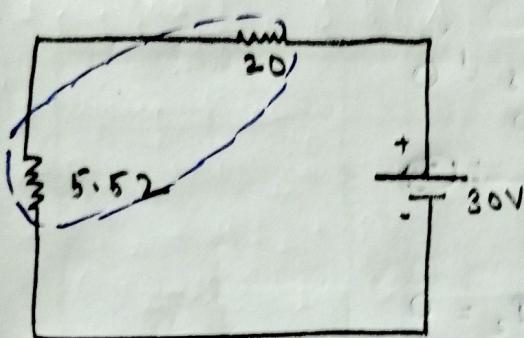

⑦

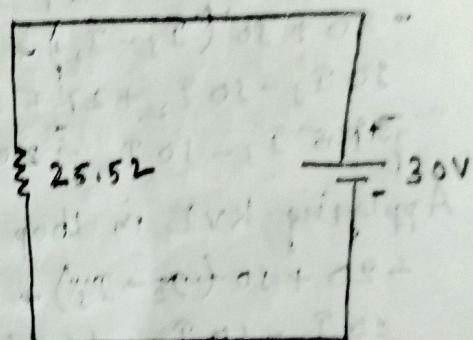

$$V = 30V; R_{eq} = 25.52\Omega$$

$$V = IR \rightarrow I = \frac{V}{R}$$


$$I = \frac{30}{25.52} = 1.175A$$

$$I_5 = 1.175 \times \frac{10}{35} \quad I_{30} = 0.783 \times \frac{20}{30}$$


$$I_5 = 0.783A \quad I_{30} = 0.522A$$




Considering 20V source, short-circuiting 50V source and 30V source.

①

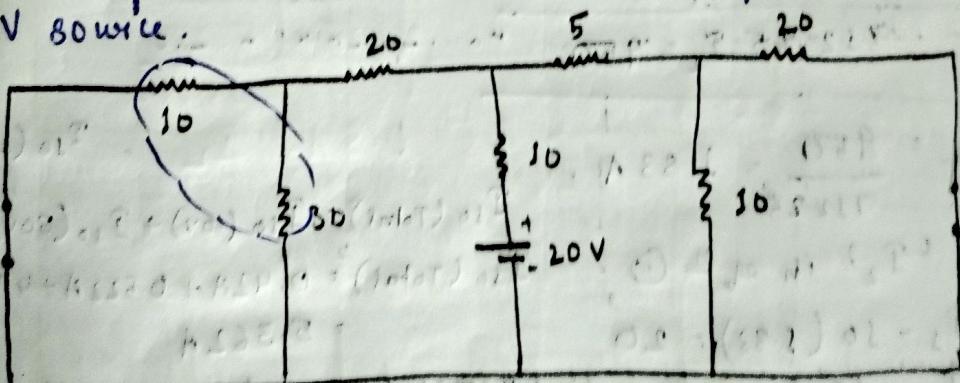

②

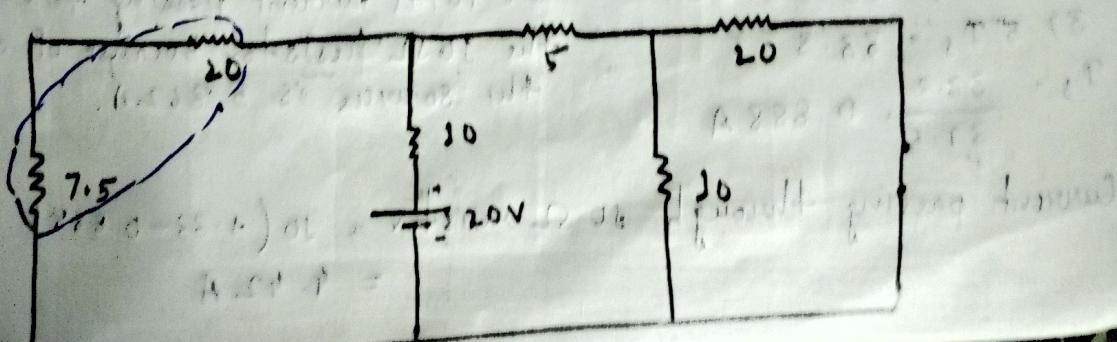

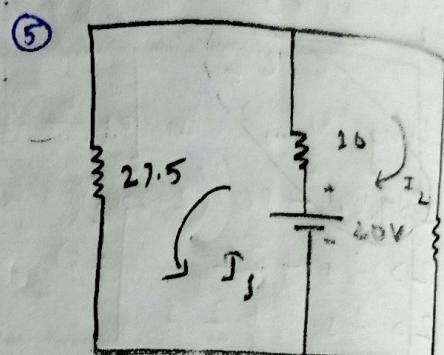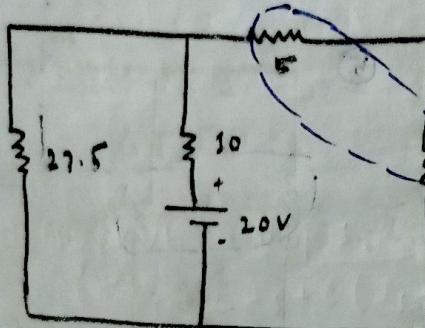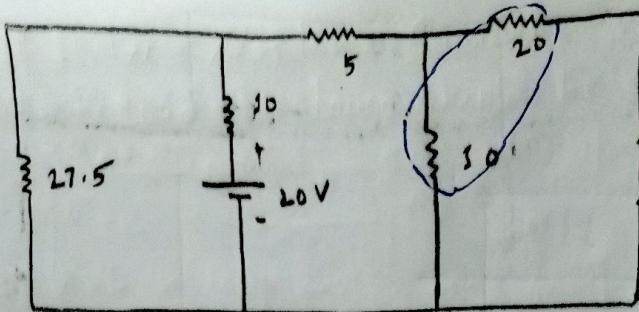

Applying KVL in loop 1,

$$-20 + 50(I_2 - I_1) + 27.5 I_1 = 0 \\ 50 I_2 - 50 I_1 + 27.5 I_1 = 20 \\ 37.5 I_1 - 50 I_2 = 20 \quad \textcircled{1}$$

Applying KVL in loop 2,

$$-20 + 50(I_1 - I_2) + 11.66 I_2 = 0 \\ 50 I_1 - 50 I_2 + 11.66 I_2 = 20 \\ -50 I_2 + 21.66 I_2 = 20 \quad \textcircled{11}$$

Solving eq n ① and ⑪,

$$\begin{aligned} 37.5 I_1 - 500 I_2 &= 200 \\ -37.5 I_1 + 83.33 I_2 &= 150 \\ \hline 750 I_2 &= 950 \end{aligned}$$

$$I_2 = \frac{950}{750} = 1.33 \text{ A}$$

Putting I_2 in eq n ①,

$$37.5 I_1 - 50(1.33) = 20$$

$$37.5 I_1 - 66.5 = 20$$


$$37.5 I_1 = 86.5$$

$$I_1 = \frac{86.5}{37.5} = 0.888 \text{ A}$$

$$\begin{aligned} I_{\text{Total}}(\text{Total}) &= I_{50}(50V) + I_{50}(30V) \\ I_{50}(\text{Total}) &= 0.42A + 0.522A + 4.42 \\ &= 5.362 \text{ A} \end{aligned}$$

∴ Total current passing through the 50Ω resistor because of all the sources is 5.362 A .
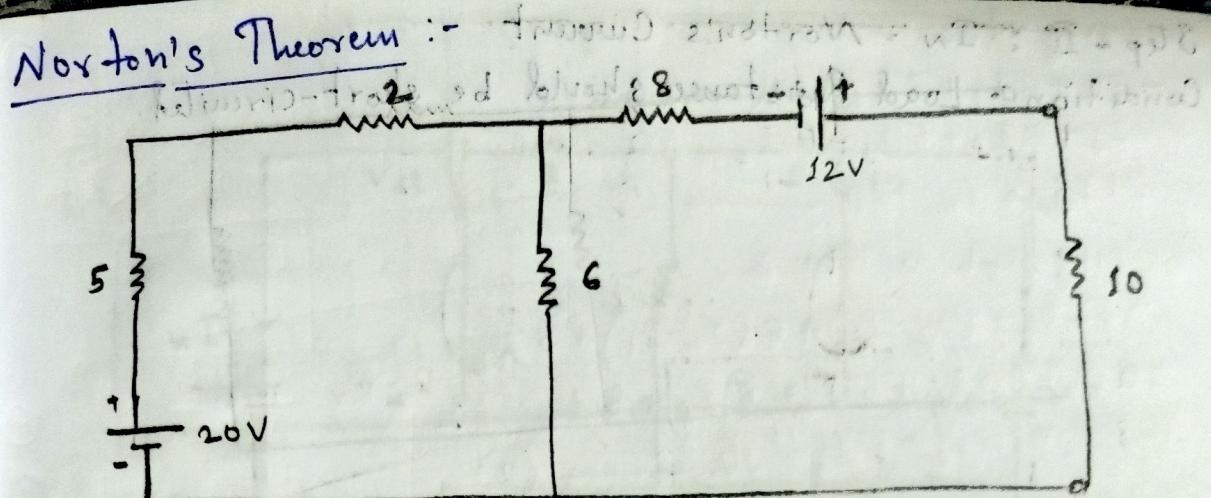
$$\begin{aligned} \text{Current passing through } 50\Omega \text{ resistor} &= 50(1.33 - 0.888) \\ &= 4.42 \text{ A} \end{aligned}$$




Step - I : R_N = Norton's Resistance

Conditions :-

- Load resistance should be open-circuited.
- Voltage source should be short-circuited.


①

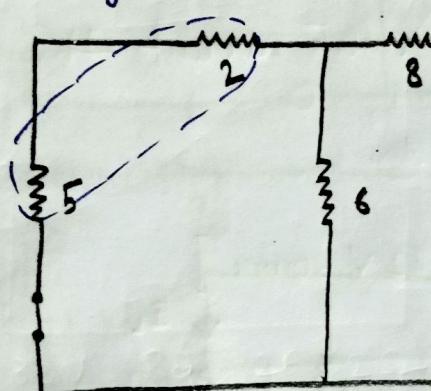

(1) R_N = $\frac{V_{oc}}{I_s}$

$$R_N = \frac{12}{2} = 6\Omega$$


②

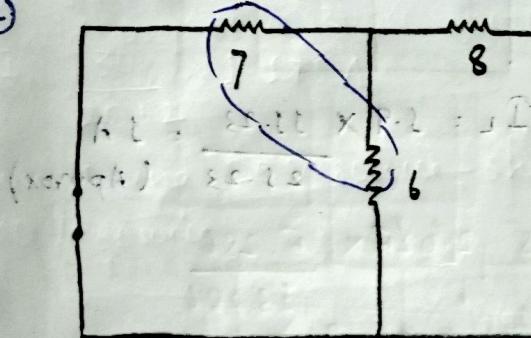


(2) R_N = $\frac{V_{oc}}{I_s}$

$$R_N = \frac{12}{2} = 6\Omega$$

③

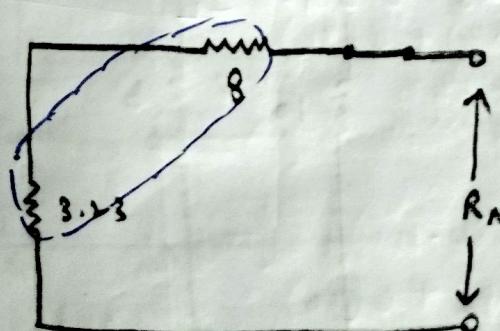


④

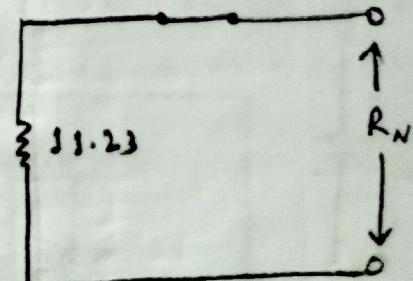

$$\text{Norton's Resistance} = R_N = 5.23\Omega$$

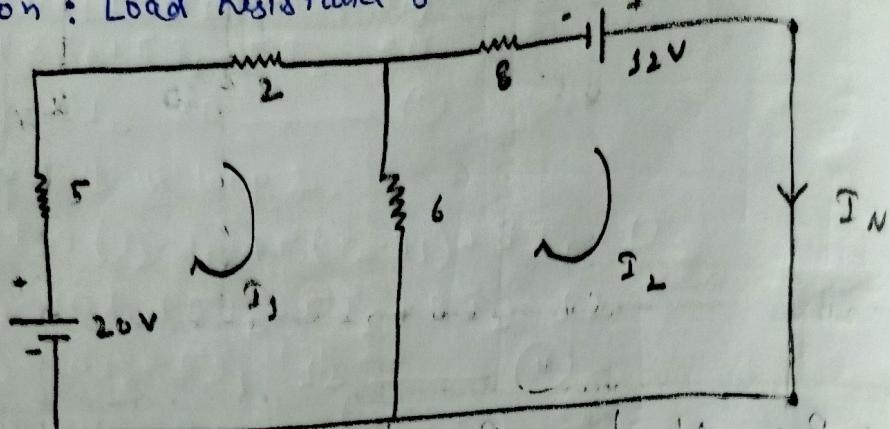Step - II : I_N = Norton's Current
Condition : Load Resistance should be short-circuited.



Applying KVL in loop 1,

$$\begin{aligned} -20 + 5I_1 + 2I_1 + 6(I_3 - I_2) &= 0 \\ 5I_1 + 2I_1 + 6I_3 - 6I_2 &= 20 \\ 13I_1 - 6I_2 &= 20 \quad \text{--- (1)} \end{aligned}$$


Applying KVL in loop 2,

$$\begin{aligned} -32 + 6(I_2 - I_1) + 8I_2 &= 0 \\ 6I_2 - 6I_1 + 8I_2 &= 32 \\ 14I_2 - 6I_1 &= 32 \quad \text{--- (2)} \end{aligned}$$


Solving eqn (1) and (2),







$$\begin{aligned} 78I_1 - 36I_2 &= 120 \\ -78I_1 + 582I_2 &= 556 \\ 546I_2 &= 276 \end{aligned}$$

$$I_2 = \frac{276}{546} = 0.5A = I_N$$

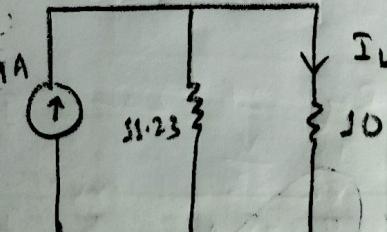
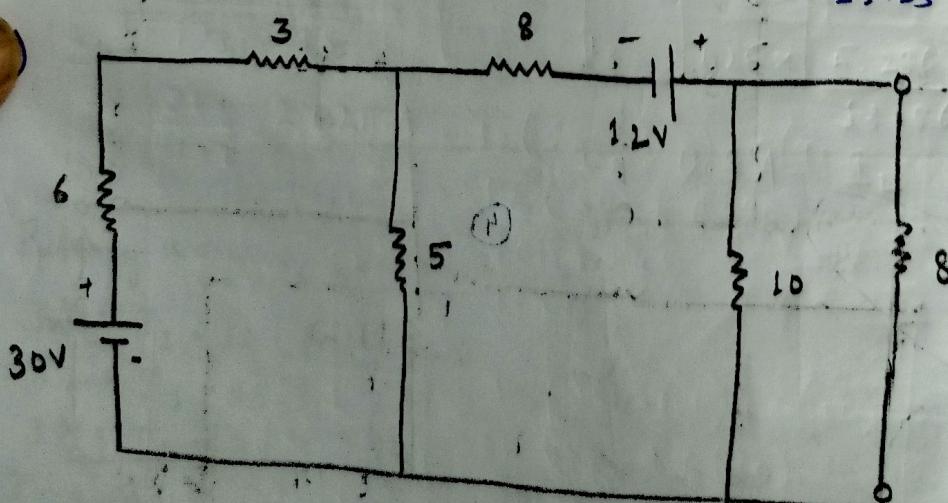
$$I_L = 0.5 \times \frac{10}{1+10} = 0.45A \approx 0.5A \quad (\text{Approx})$$



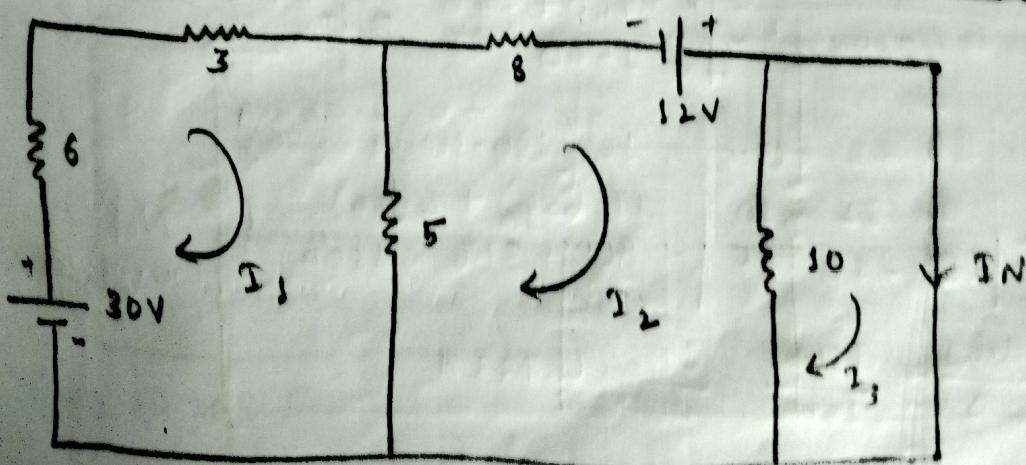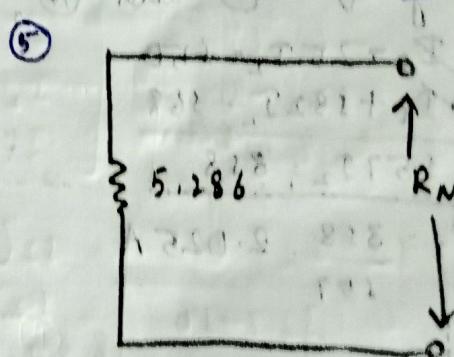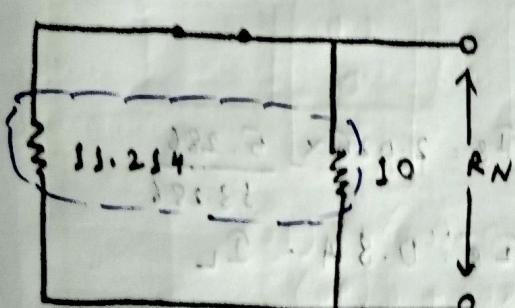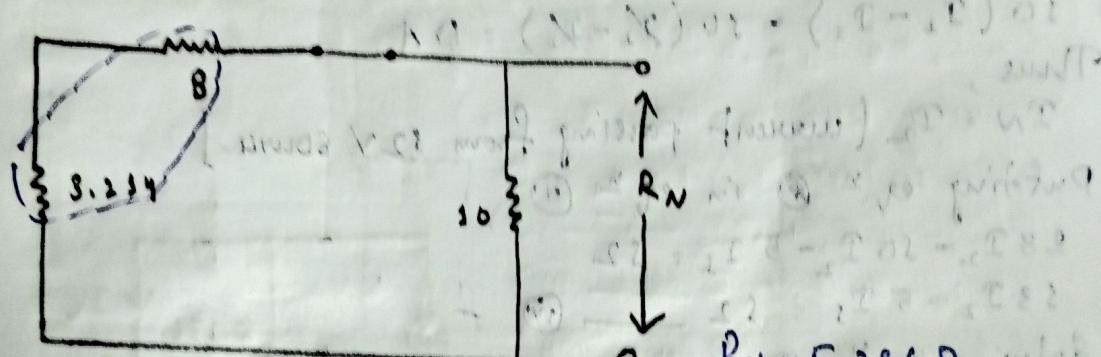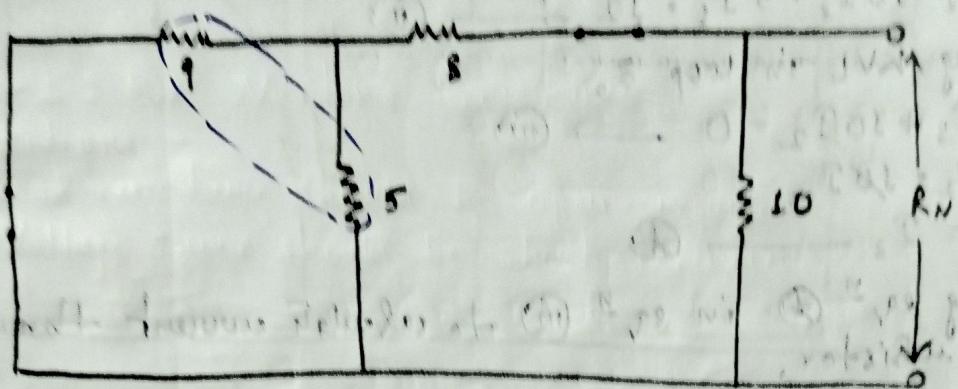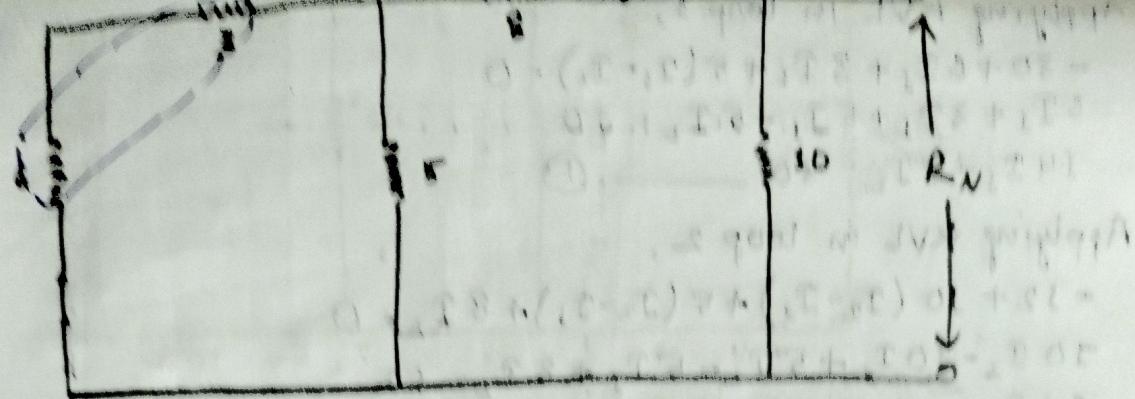

Applying KVL in loop 1,

$$-30 + 6I_1 + 3I_2 + 5(I_3 - I_2) = 0$$
$$6I_1 + 3I_2 + 5I_3 - 5I_2 = 30$$
$$14I_3 - 5I_2 = 30 \quad \textcircled{1}$$

Applying KVL in loop 2,

$$-12 + 10(I_2 - I_3) + 5(I_2 - I_1) + 8I_2 = 0$$
$$10I_2 - 10I_3 + 5I_2 - 5I_1 + 8I_2 = 12$$
$$23I_2 - 10I_3 - 5I_1 = 12 \quad \textcircled{2}$$

Applying KVL in loop 3,

$$-10I_3 + 10I_2 = 0 \quad \textcircled{3}$$
$$I_2 = I_3 \quad \textcircled{4}$$

Putting eq $\textcircled{4}$ in eq $\textcircled{3}$ to calculate current through 50Ω resistor,

$$= 10(I_2 - I_3) = 10(2I_2 - I_2) = 10A$$

Thus,

$I_N = I_2$ [current passing from $52V$ source]

Putting eq $\textcircled{4}$ in eq $\textcircled{2}$,

$$23I_2 - 50I_2 - 5I_3 = 12$$

$$53I_2 - 5I_3 = 12 \quad \textcircled{4}$$


Solving eq $\textcircled{1}$ and $\textcircled{4}$,

$$10I_3 - 25I_2 = 150$$

$$-70I_3 + 182I_2 = 168$$

$$\underline{157I_2 = 358}$$

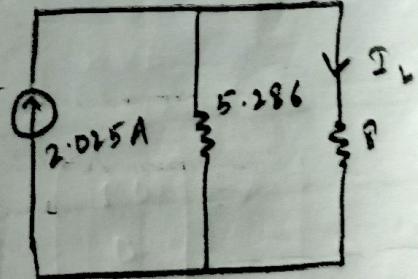
$$\overline{I_2 = \frac{358}{157} = 2.25A}$$








$$I_L = 2.25 \times \frac{5.286}{53.286}$$


$$I_L = 0.8A$$

H.W. $\textcircled{6}$

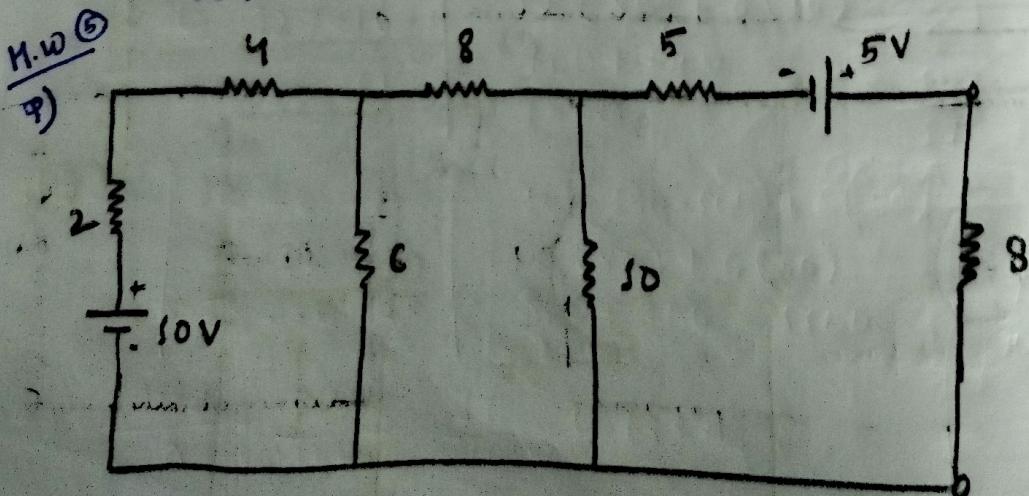

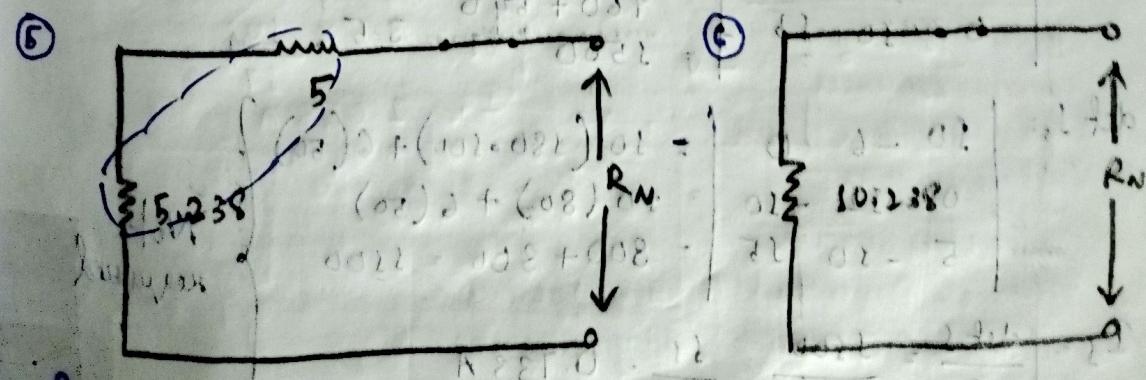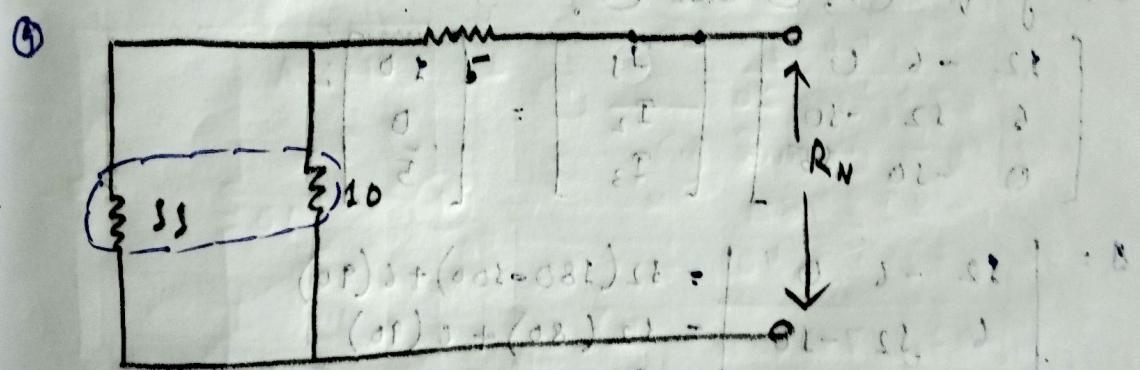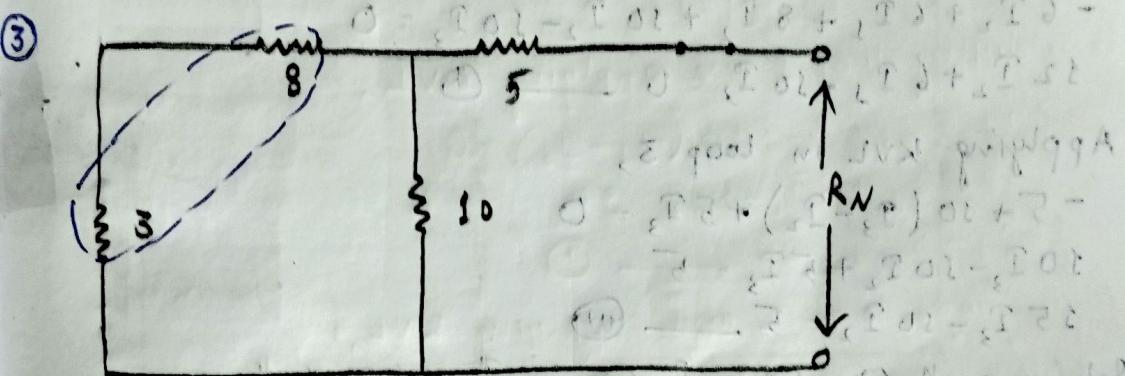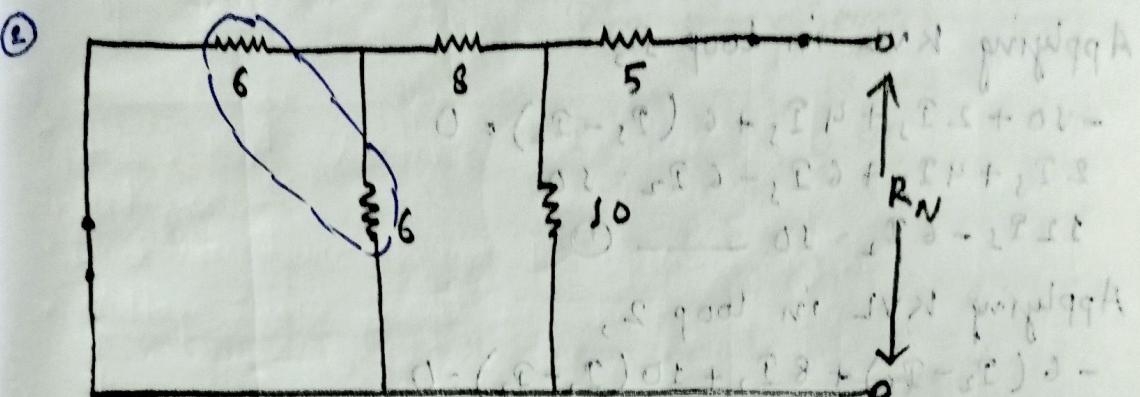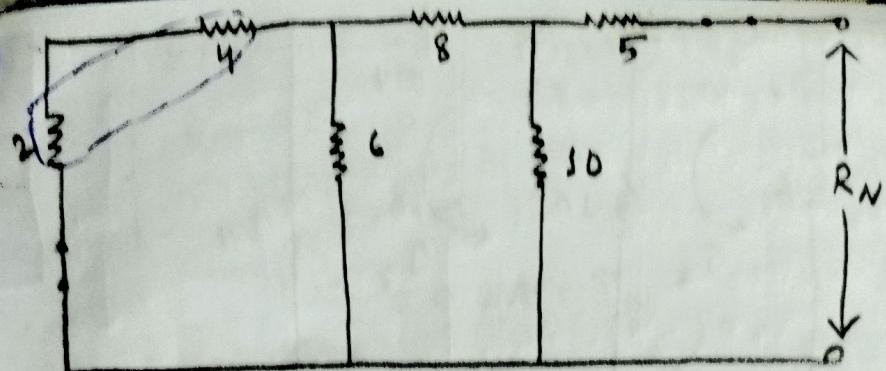

$$R_N = 10.238 \Omega$$

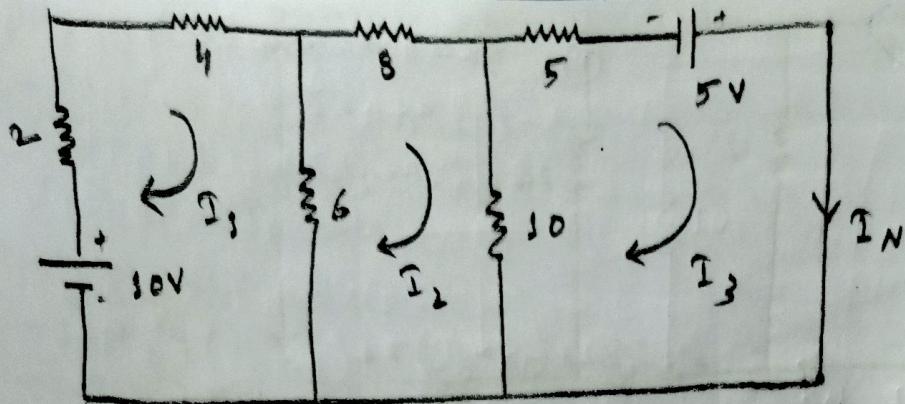

Applying KVL in loop 1,

$$-50 + 2I_3 + 4I_3 + 6(I_3 - I_2) = 0$$

$$2I_3 + 4I_3 + 6I_3 - 6I_2 = 50$$

$$12I_3 - 6I_2 = 50 \quad \textcircled{1}$$

Applying KVL in loop 2,

$$-6(I_2 - I_3) + 8I_2 + 10(I_2 - I_3) = 0$$

$$-6I_2 + 6I_3 + 8I_2 + 10I_2 - 10I_3 = 0$$

$$12I_2 + 6I_3 - 10I_3 = 0 \quad \textcircled{2}$$

Applying KVL in loop 3,

$$-5 + 10(I_3 - I_2) + 5I_3 = 0$$

$$10I_3 - 10I_2 + 5I_3 = 5$$

$$15I_3 - 10I_2 = 5 \quad \textcircled{3}$$

Solving eq n $\textcircled{1}$, $\textcircled{2}$ and $\textcircled{3}$,

$$\begin{bmatrix} 12 & -6 & 0 \\ 6 & 12 & -10 \\ 0 & -10 & 15 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \\ 5 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 12 & -6 & 0 \\ 6 & 12 & -10 \\ 0 & -10 & 15 \end{vmatrix} = 12(180 - 500) + 6(90) \\ = 12(80) + 6(90) \\ = 960 + 540 \\ = 1500$$


$$\text{det } S = \begin{vmatrix} 50 & -6 & 0 \\ 0 & 12 & -10 \\ 5 & -10 & 15 \end{vmatrix} = 50(180 - 500) + 6(50) \\ = 10(80) + 6(50) \\ = 800 + 300 = 1100$$

$$I_3 = \frac{\text{det } S}{\Delta} = \frac{1100}{1500} = \frac{11}{15} = 0.733 \text{ A}$$

Not required

$$\text{det. 3} = \begin{vmatrix} 32 & -6 & 50 \\ 6 & 32 & 0 \\ 0 & -50 & 5 \end{vmatrix} = 32(50) + 6(0) + 50(-60) \\ = 720 + 0 - 300 \\ = 300$$



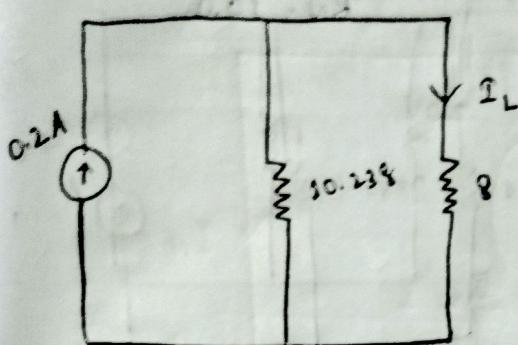
$$I_3 = \frac{\text{det. 3}}{3} = \frac{300}{3500} = 0.2 \text{ A} = I_N$$





$$I_3 = 0.2 \times \frac{30.238}{38.238}$$

$$I_8 = \frac{2}{50} \times 0.56$$


$$I_L = 0.552 \text{ A}$$

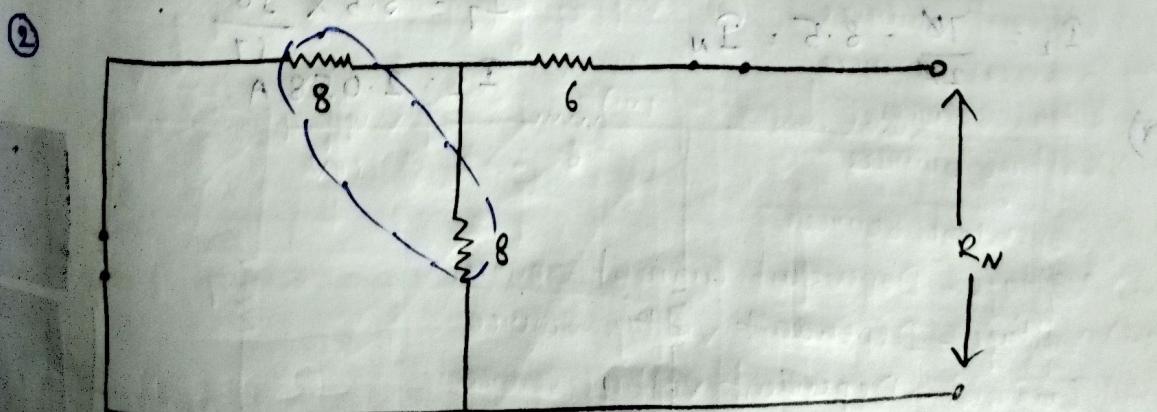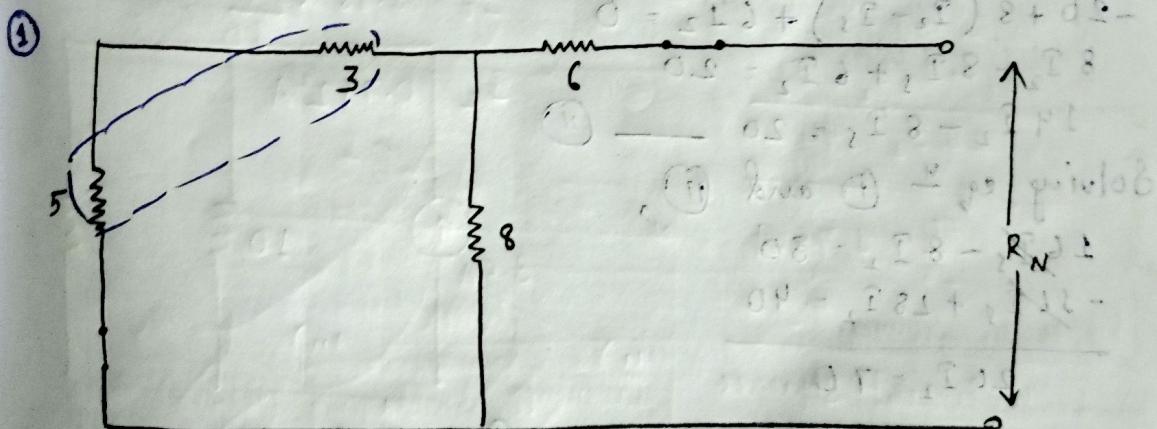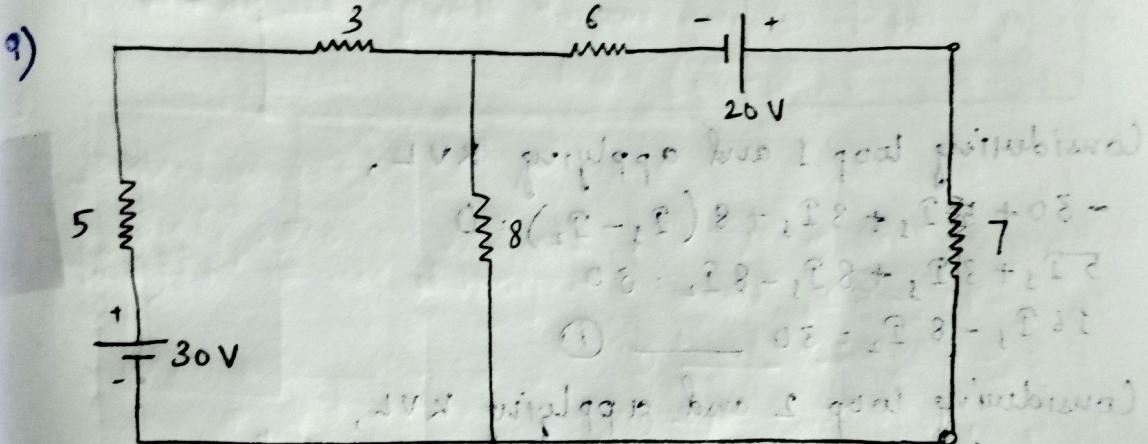

③

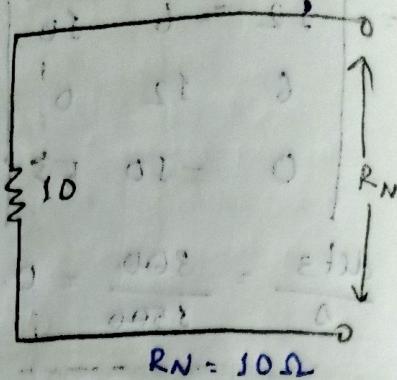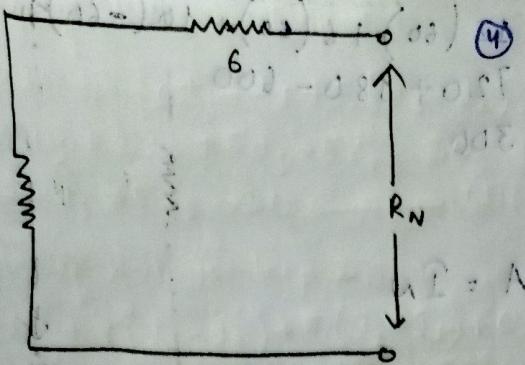

$$R_N = 10\Omega$$

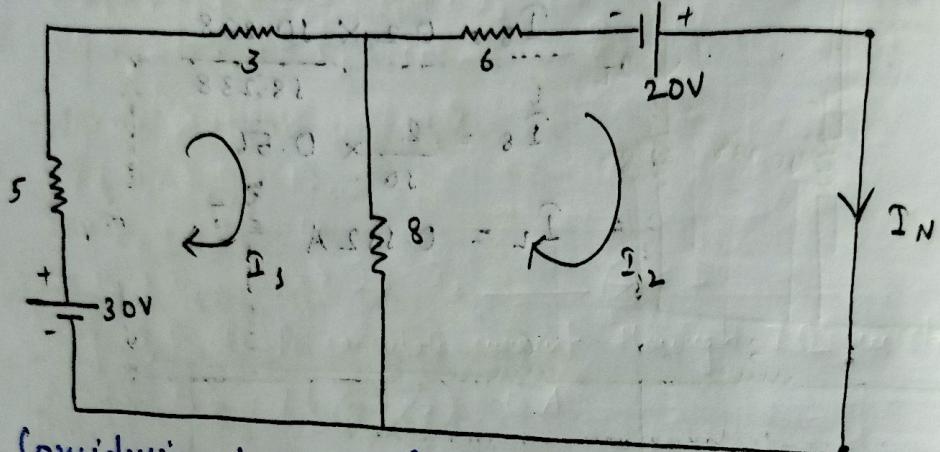

Considering loop 1 and applying KVL,

$$-30 + 5I_1 + 3I_1 + 8(I_1 - I_2) = 0$$

$$5I_1 + 3I_1 + 8I_1 - 8I_2 = 30$$

$$16I_1 - 8I_2 = 30 \quad \text{--- (1)}$$

Considering loop 2 and applying KVL,

$$-20 + 8(I_2 - I_1) + 6I_2 = 0$$

$$8I_2 - 8I_1 + 6I_2 = 20$$

$$14I_2 - 8I_1 = 20 \quad \text{--- (11)}$$


Solving eq $\frac{1}{(1)} \text{ and } (11)$,

$$16I_1 - 8I_2 = 30$$

$$-32I_1 + 28I_2 = 60$$


$$20I_2 = 70$$






$$I_2 = \frac{70}{20} = 3.5 = I_N$$

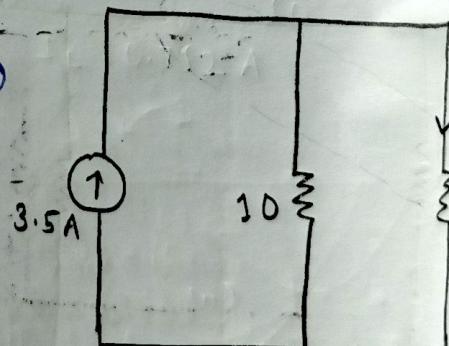

$$I_N = 3.5 \times \frac{10}{17}$$

$$I_L = 2.058 \text{ A}$$

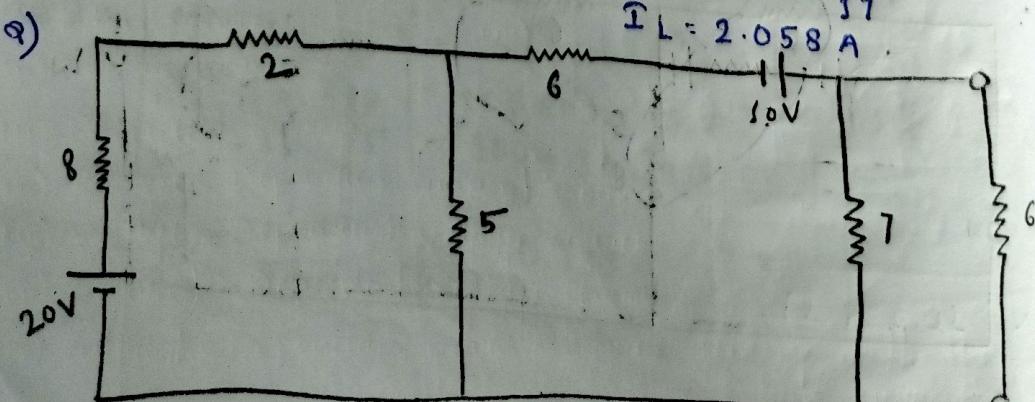

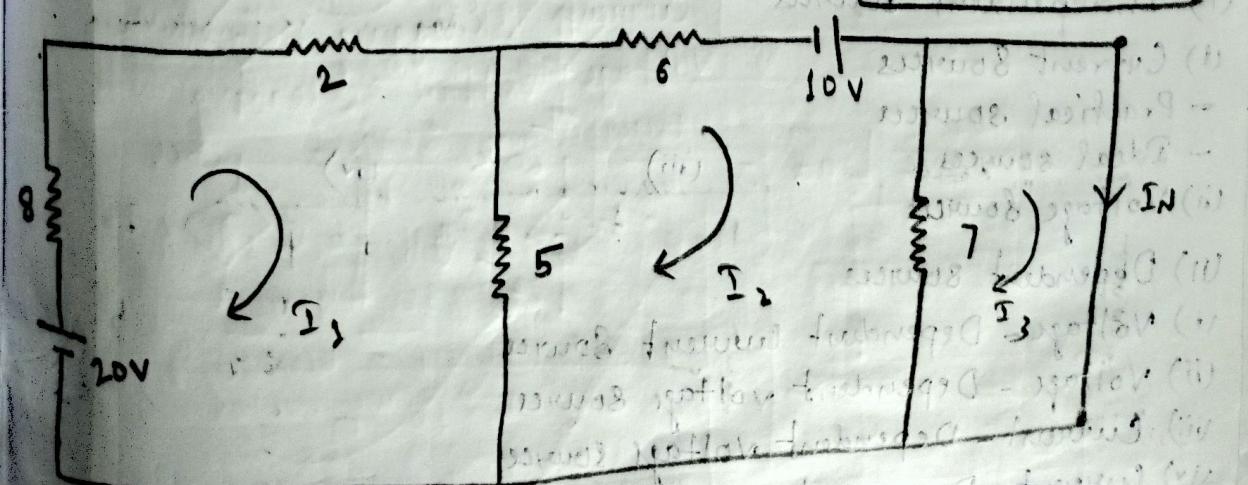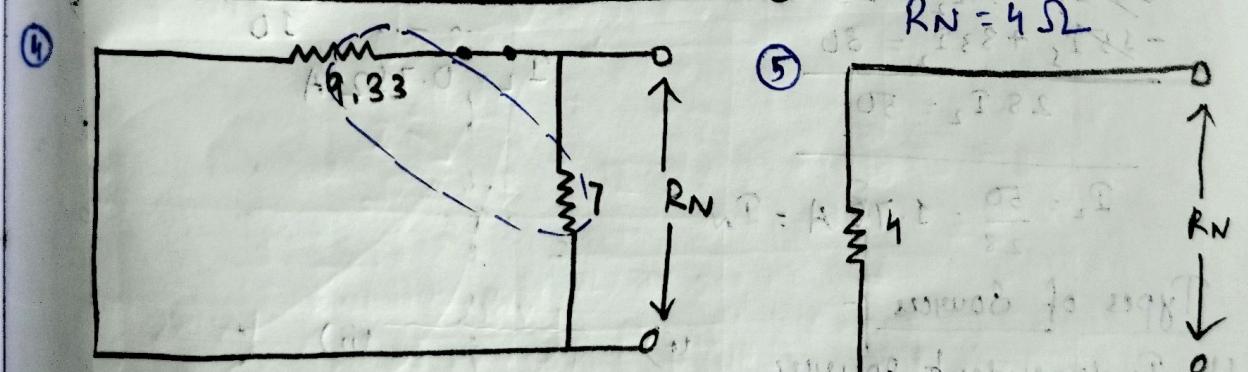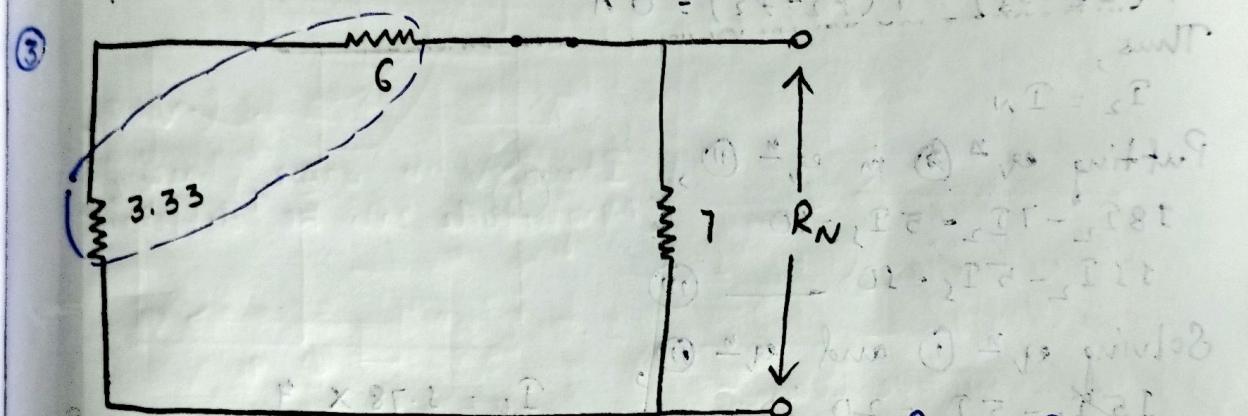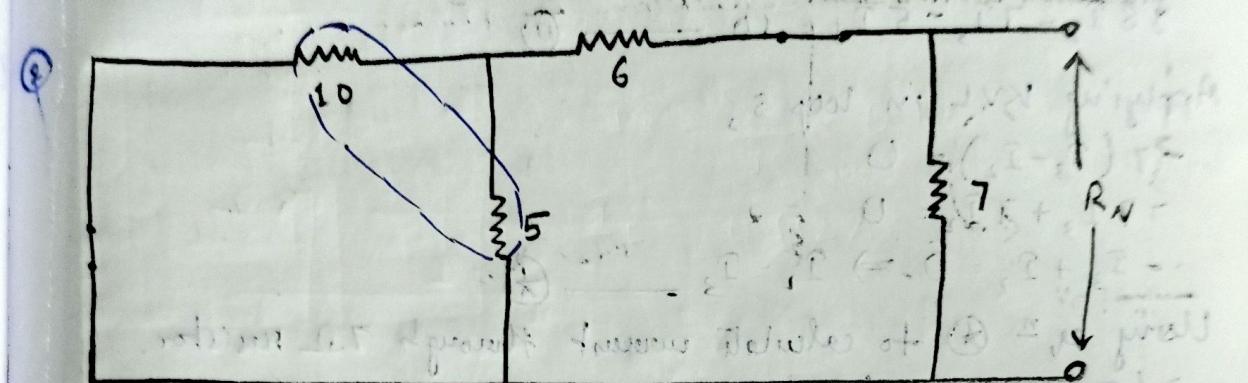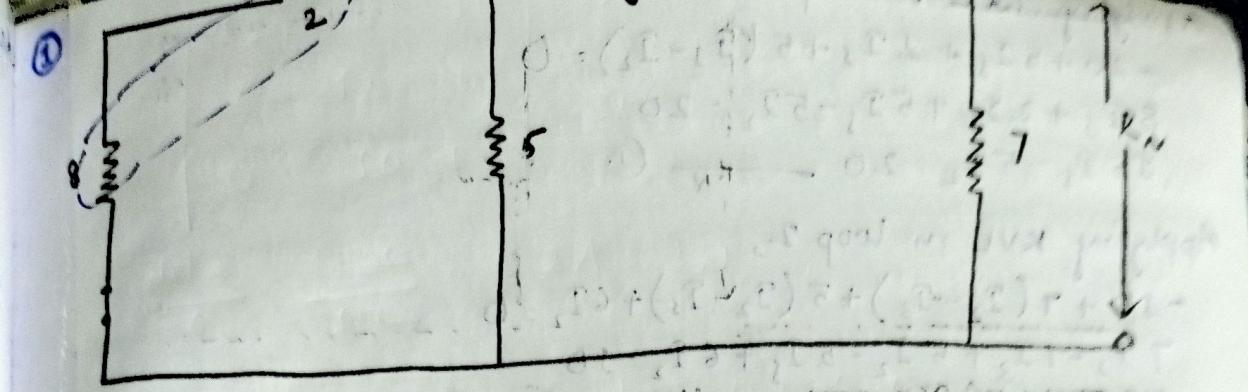

Applying KVL in loop 1,

$$-20 + 8I_3 + 2I_3 + 5(I_3 - I_2) = 0$$

$$8I_3 + 2I_3 + 5I_3 - 5I_2 = 20$$

$$15I_3 - 5I_2 = 20 \quad \textcircled{1}$$

Applying KVL in loop 2,

$$-10 + 7(I_2 - I_3) + 5(I_2 - I_3) + 6I_2 = 0$$

$$7I_2 - 7I_3 + 5I_2 - 5I_3 + 6I_2 = 10$$

$$18I_2 - 12I_3 = 10 \quad \textcircled{2}$$

Applying KVL in loop 3,

$$-7(I_3 - I_2) = 0$$

$$-7I_3 + 7I_2 = 0$$

$$-I_3 + I_2 = 0 \Rightarrow I_2 = I_3 \quad \textcircled{3}$$

Using eq $\textcircled{2}$ to calculate current through 7Ω resistor.

$$= 7(I_2 - I_3) = 7(7I_2 - 7I_2) = 0A$$

Thus,

$$I_2 = I_N$$

Putting eq $\textcircled{3}$ in eq $\textcircled{1}$,

$$18I_2 - 7I_2 - 5I_3 = 10$$

$$11I_2 - 5I_3 = 10 \quad \textcircled{3}$$

Solving eq $\textcircled{1}$ and eq $\textcircled{3}$,

$$15I_3 - 5I_2 = 20$$

$$-15I_3 + 33I_2 = 30$$

$$\frac{28I_2 = 50}{28I_2 = 50}$$

$$\overline{I_2 = \frac{50}{28} = 1.78 A = I_N}$$

Types of Sources :-

(i) Independent sources

(ii) Current sources

- Practical sources

- Ideal sources

(iii) Voltage source


(iv) Dependent sources

(i) Voltage - Dependent current source

(ii) Voltage - Dependent voltage source


(iii) Current - Dependent voltage source

(iv) Current - Dependent current source

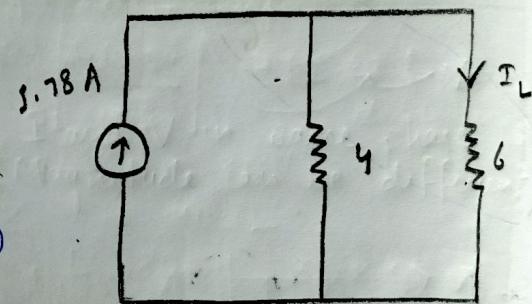


$$I_6 = 5.78 \times \frac{4}{50}$$


$$I_L = 0.732 A$$

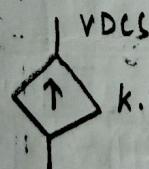

iii)

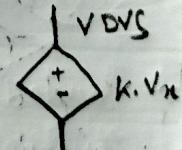

iii)

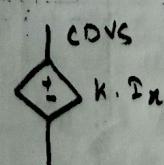

iv)

