

SEMICONDUCTOR DEVICES

* Topics:

1. Pn junction diode: symbolic representation,
Internal structure, modes of operation, characteristics
2. Half and Full wave rectifier circuits,
3. ~~Zinade~~ Zener diode: Symbolic representation, internal structure, mode of operation, characteristic, zener voltage regulator
4. BJT (Bipolar Junction transistor): symbolic representation, internal structure, types of configurations, characteristic.

* Introduction to semiconductors:


Semiconductors are the materials which have conductivity between conductors and non-conductors (or insulators).

• Types of semiconductor device:

1. pn-junction
2. zener diode.
3. FET (Field effect transistor)
4. MOSFET (Metal oxide semiconductor field effect transistor)
5. BJT (Bipolar Junction transistor)
6. SCRT (Silicon Control rectifier circuit)


* P-N-Junction diode

• Symbolic representation:

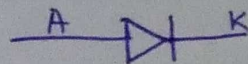

A is anode, K is cathode.


• Internal structure:

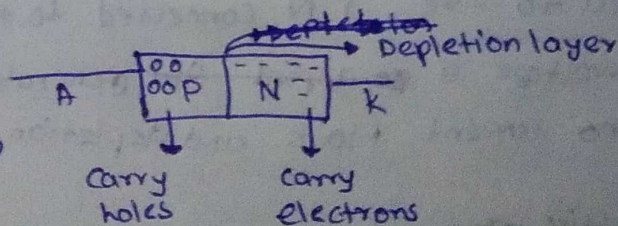

① How depletion layer is formed?

Access e from N & Access

hole from P form depletion layer.

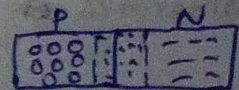


② Width of depletion layer depends on doping (adding impurities) \Rightarrow width imp. for current generation

③ When heavily doped \Rightarrow thin depletion layer \Rightarrow forward direction of I
When lightly doped \Rightarrow thick depletion layer \Rightarrow No current.

Types of modes in pn junction:

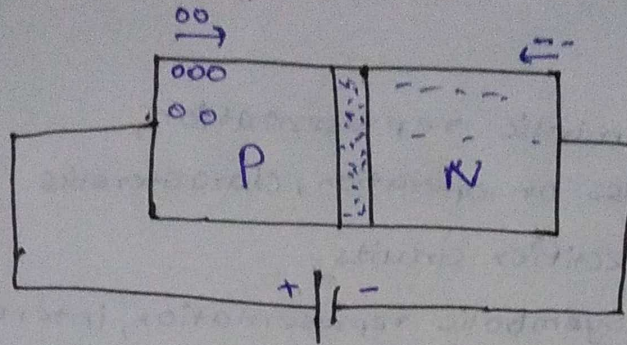1. Forward conduction mode / Forward biased:




$I_F \rightarrow$
Circuit representation of PN junction F.B

Positive terminal of battery is connected to p and negative terminal of battery is connected to n.

In forward biased mode, applied voltage, ~~applied emf~~ and generated are in opposite direction then depletion layer becomes thinner. Then current will flow in forward direction and maximum current is generated.

$$I_F \rightarrow I_D$$

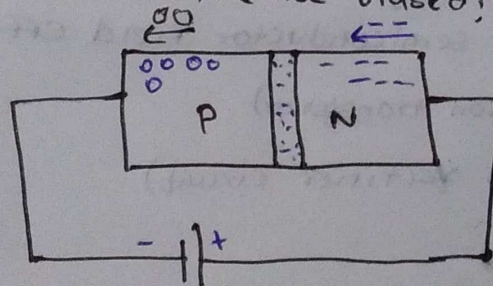2. Reverse conduction mode / Reverse biased:




$I_R \rightarrow$
Circuit representation of pn junction R.B.


P connected to -ve, N connected to +ve.

Applied voltage & ~~applied emf~~ generated voltage in opposite direction. Hence no current flows and depletion layer gets thicker.

Characteristics :

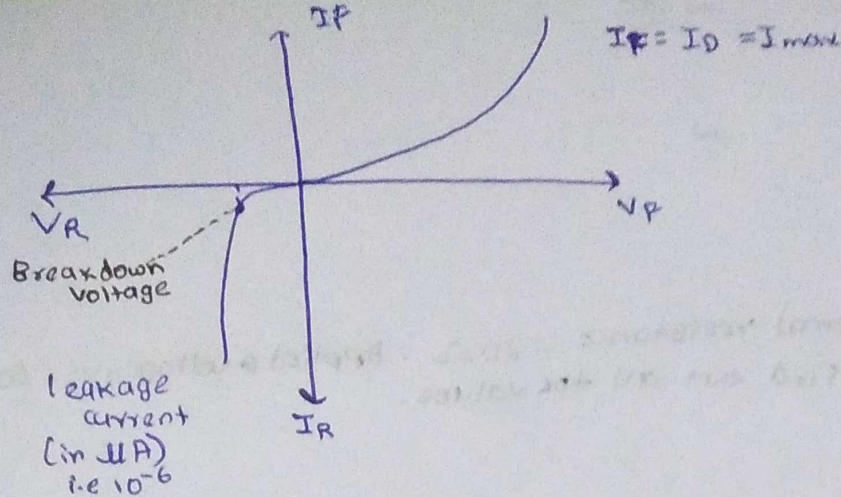



★ Half and Full wave Rectifier circuit:

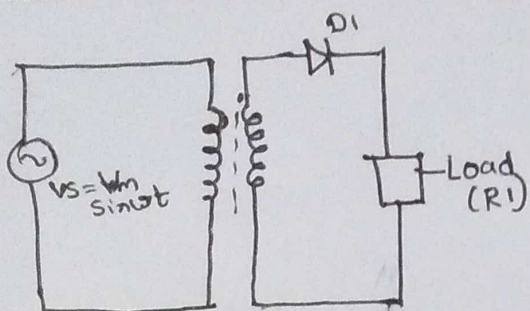

Using rectifier we can convert AC to DC.

⇒ Uncontrollable diode ~~half~~ wave circuit.

Half wave rectifier circuit

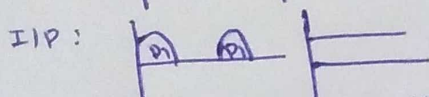
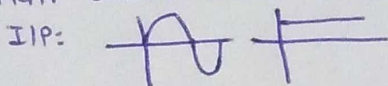


Efficiency:

Full wave is better than Half wave

Costly:

Full wave more costly than Half wave

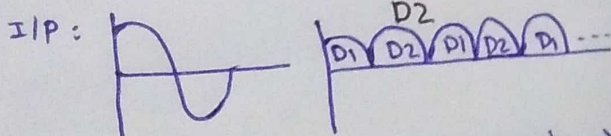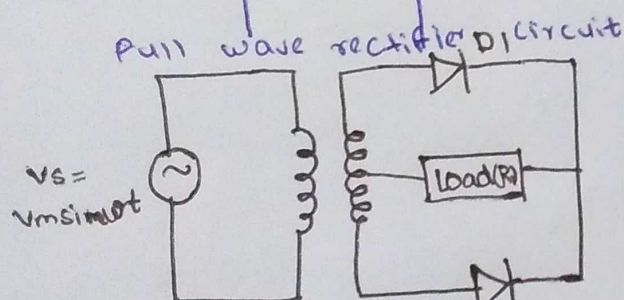

No interruption ⇒ Continuous Power supply

Half wave

Full wave

- ① Circuit representation
- ② Efficiency: 40.6
- ③ Peak inverse voltage = V_{max}
- ④ Ripple factor = 1.21
- ⑤ Form factor = 1.57
- ⑥ Peak factor = 2
- ⑦ I_{DC} or $I_{avg} = I_{max}/\pi$
- ⑧ $I_{rms} = I_m/2$
- ⑨ AC Power input = $I_{rms}^2 \times R_T$
- ⑩ DC Power output = $I_{DC}^2 \times R_L$

- ① Circuit representation
- ② Efficiency: 81.2
- ③ Peak inverse voltage = $2 \times V_{max}$
- ④ Ripple factor = 0.482
- ⑤ Form factor = 1.11
- ⑥ Peak factor = 1.414
- ⑦ I_{DC} or $I_{avg} = 2 I_{max}/\pi$
- ⑧ $I_{rms} = I_m/\sqrt{2}$
- ⑨ AC Power input = $I_{rms}^2 \times R_T$
- ⑩ DC Power output = $I_{DC}^2 \times R_L$

⑪ DC ~~Power~~ output voltage
 $I_{DC} \times R_L$

⑫ Efficiency = $\frac{\text{DC O/P Power}}{\text{AC I/P Power}}$

Q.1) Crystal diode having internal resistance = 20Ω . Applied voltage, $V_s = 50 \sin \omega t$
 Load resistance, $R_L = 800\Omega$. Find out all the values.

